

Chapter 7










Digital Design and Computer Architecture: ARM[®] Edition

Sarah L. Harris and David Money Harris

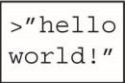

Chapter 7 :: Topics

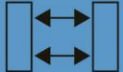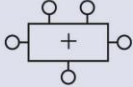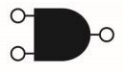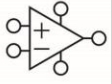
- **Introduction**
- **Performance Analysis**
- **Single-Cycle Processor**
- **Multicycle Processor**
- **Pipelined Processor**
- **Advanced Microarchitecture**

Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	



Introduction

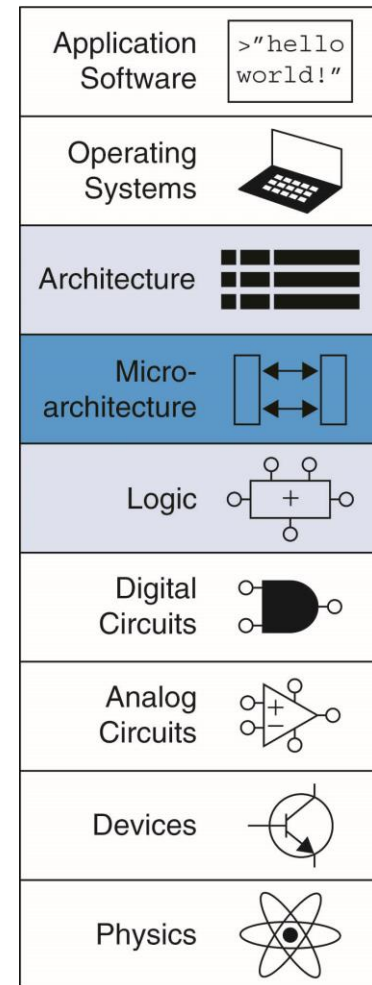- **Microarchitecture:** how to implement an architecture in hardware
- Processor:
 - **Datapath:** functional blocks
 - **Control:** control signals



Microarchitecture

- Multiple implementations for a single architecture:
 - **Single-cycle:** Each instruction executes in a single cycle
 - **Multicycle:** Each instruction is broken up into series of shorter steps
 - **Pipelined:** Each instruction broken up into series of steps & multiple instructions execute at once



Processor Performance

- **Program execution time**

Execution Time = (#instructions)(cycles/instruction)(seconds/cycle)

- **Definitions:**

- CPI: Cycles/instruction
- clock period: seconds/cycle
- IPC: instructions/cycle = IPC

- **Challenge is to satisfy constraints of:**

- Cost
- Power
- Performance



ARM Processor

- Consider **subset** of ARM instructions:
 - **Data-processing instructions:**
 - **ADD, SUB, AND, ORR**
 - with register and immediate Src2, but **no shifts**
 - **Memory instructions:**
 - **LDR, STR**
 - with **positive immediate offset**
 - **Branch instructions:**
 - **B**




Architectural State Elements

Determines everything about a processor:

- Architectural state:
 - 16 registers (including PC)
 - Status register
- Memory



ARM Architectural State Elements

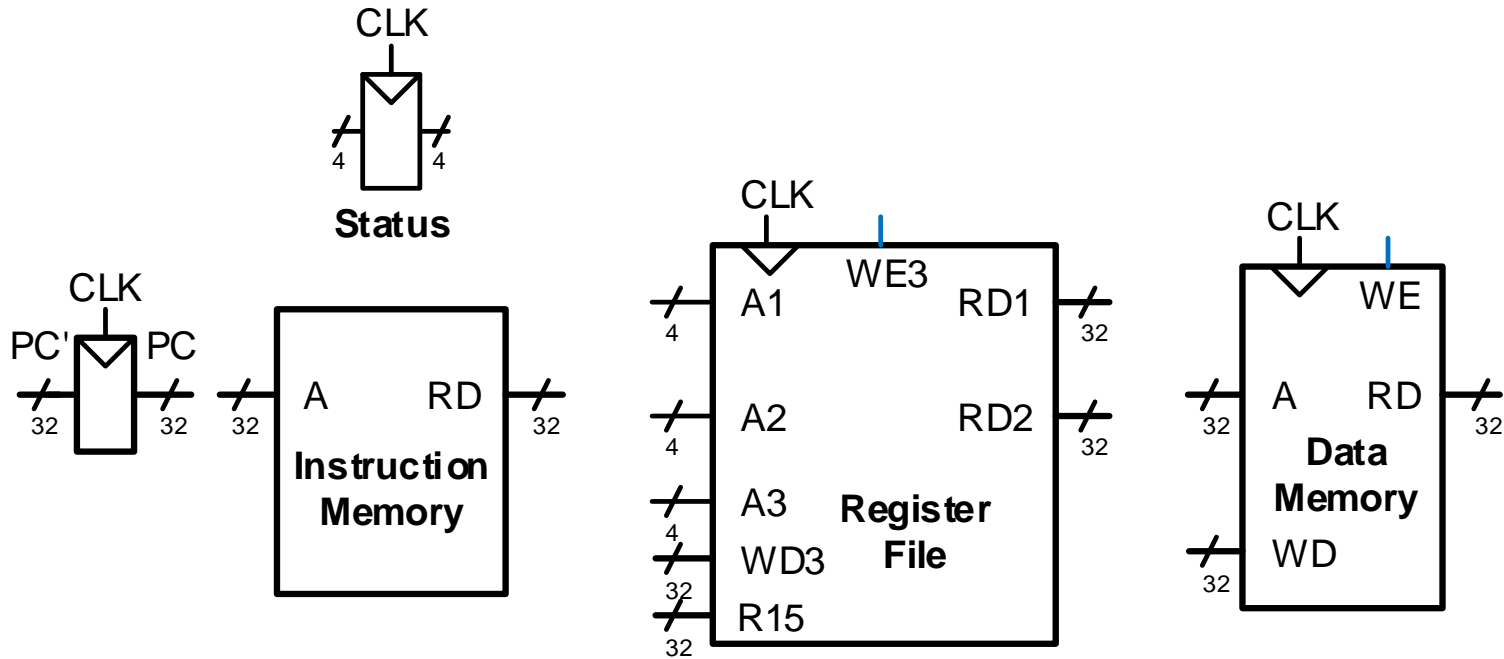

Single-Cycle ARM Processor

- Datapath
- Control




Single-Cycle ARM Processor

- **Datapath**
- Control




Single-Cycle ARM Processor

 - **Datapath:** start with LDR instruction
- **Example:** LDR R1, [R2, #5]
LDR Rd, [Rn, imm12]





Single-Cycle Datapath: LDR fetch

STEP 1: Fetch instruction

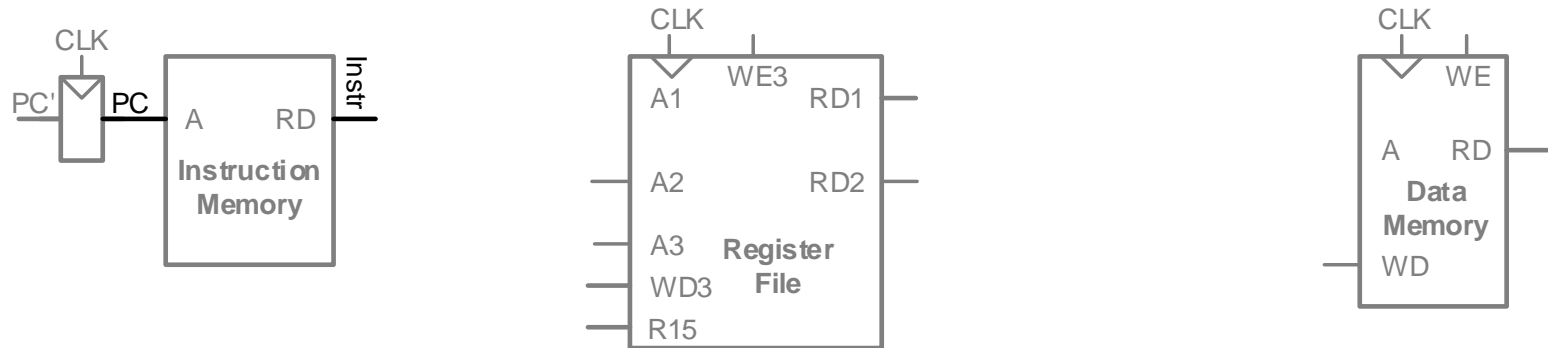



Single-Cycle Datapath: LDR Reg Read

STEP 2: Read source operands from RF

 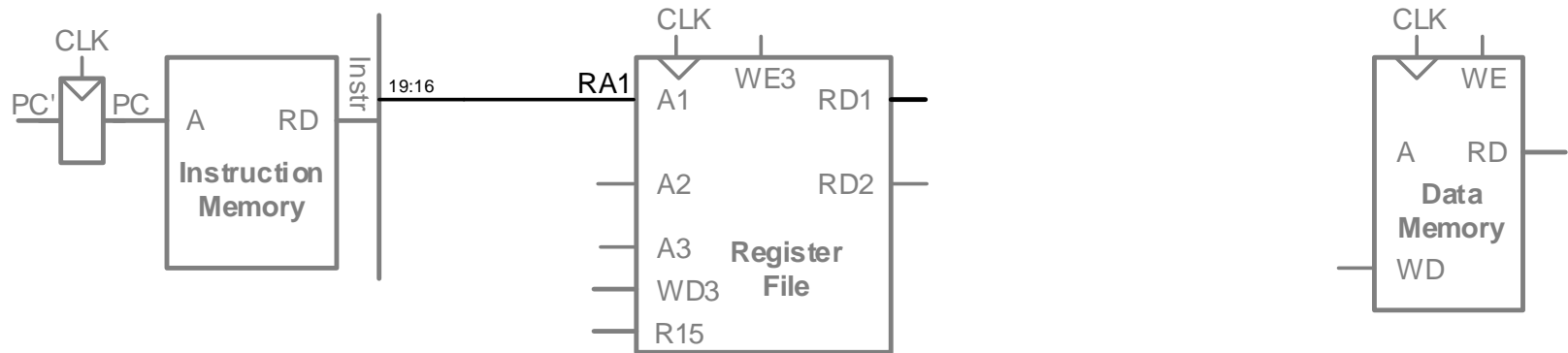



Single-Cycle Datapath: LDR Immed.

STEP 3: Extend the immediate

 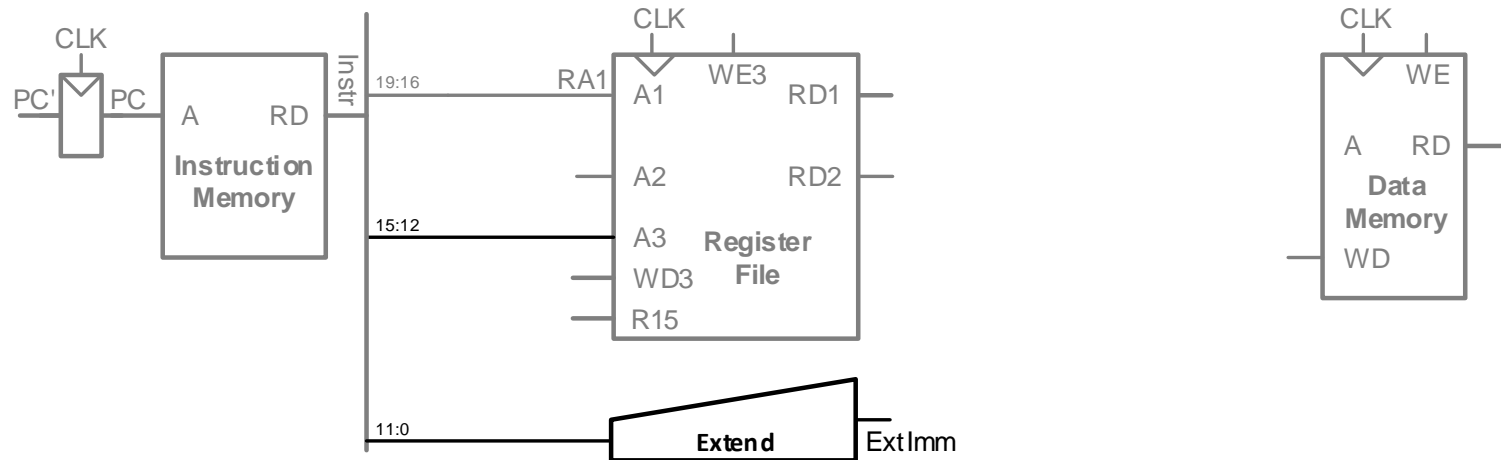



Single-Cycle Datapath: LDR Address

STEP 4: Compute the memory address

 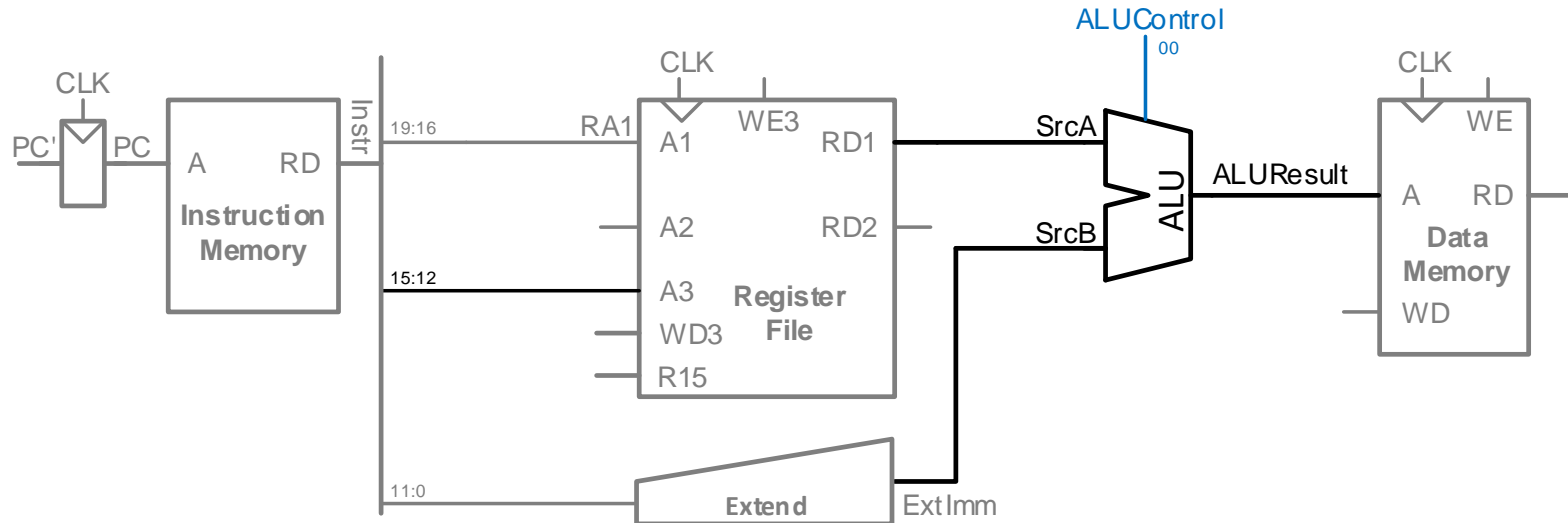


Single-Cycle Datapath: LDR Mem Read

 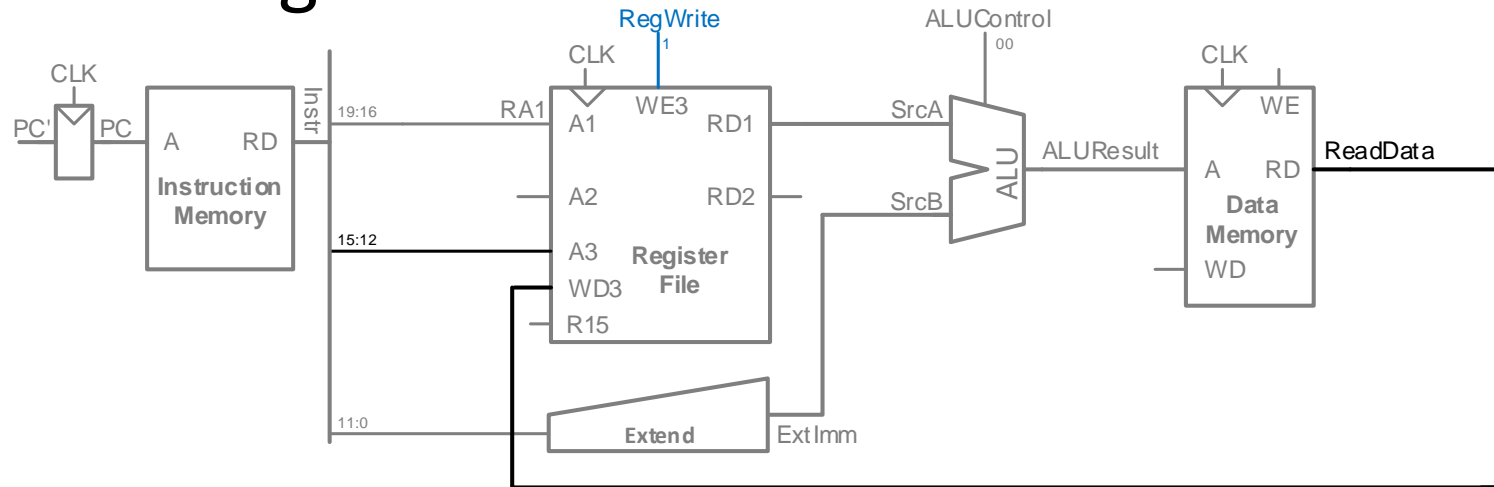STEP 5: Read data from memory and write it back to register file




Single-Cycle Datapath: PC Increment

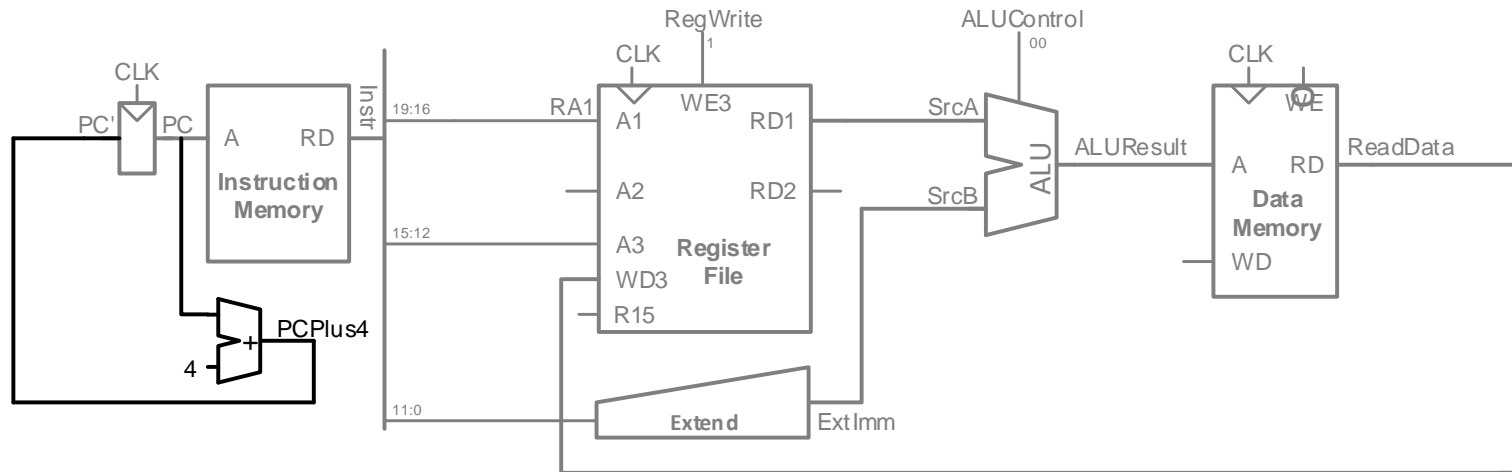STEP 6: Determine address of next instruction



Single-Cycle Datapath: Access to PC

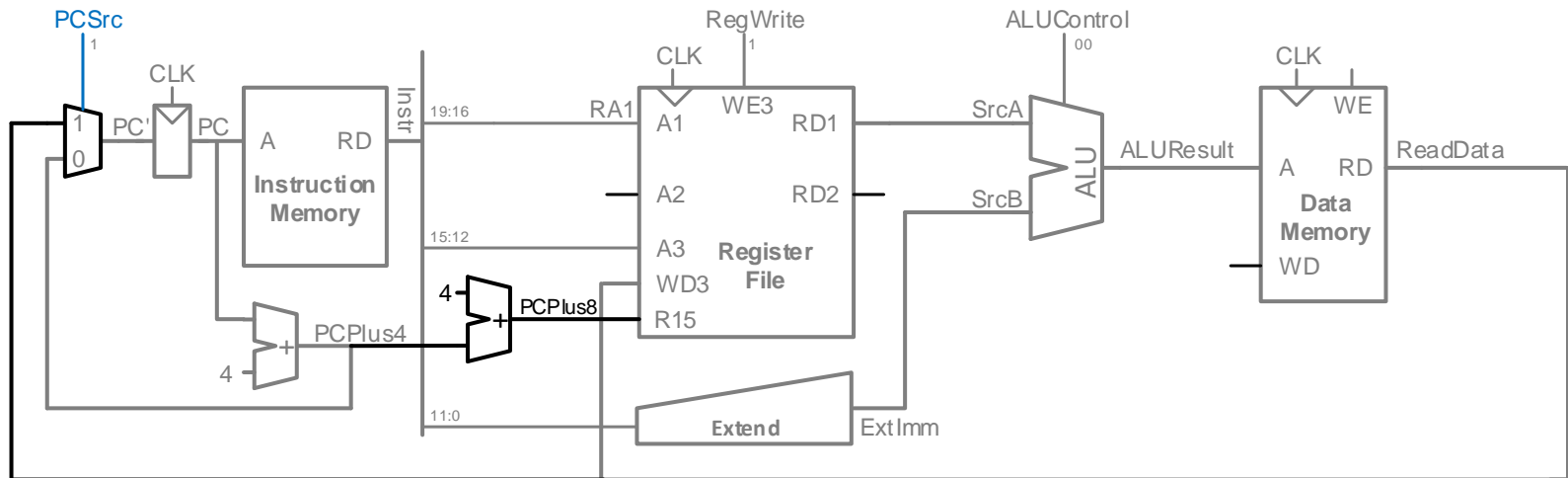
PC can be source/destination of instruction



Single-Cycle Datapath: Access to PC

PC can be source/destination of instruction

 
- **Source:** R15 must be available in Register File
 - **PC** is read as the current **PC plus 8**



Single-Cycle Datapath: Access to PC

PC can be source/destination of instruction


 
- **Source:** R15 must be available in Register File
 - **PC** is read as the current **PC plus 8**
- **Destination:** Be able to write result to PC



Single-Cycle Datapath: STR

Expand datapath to handle STR:


- Write data in Rd to memory

 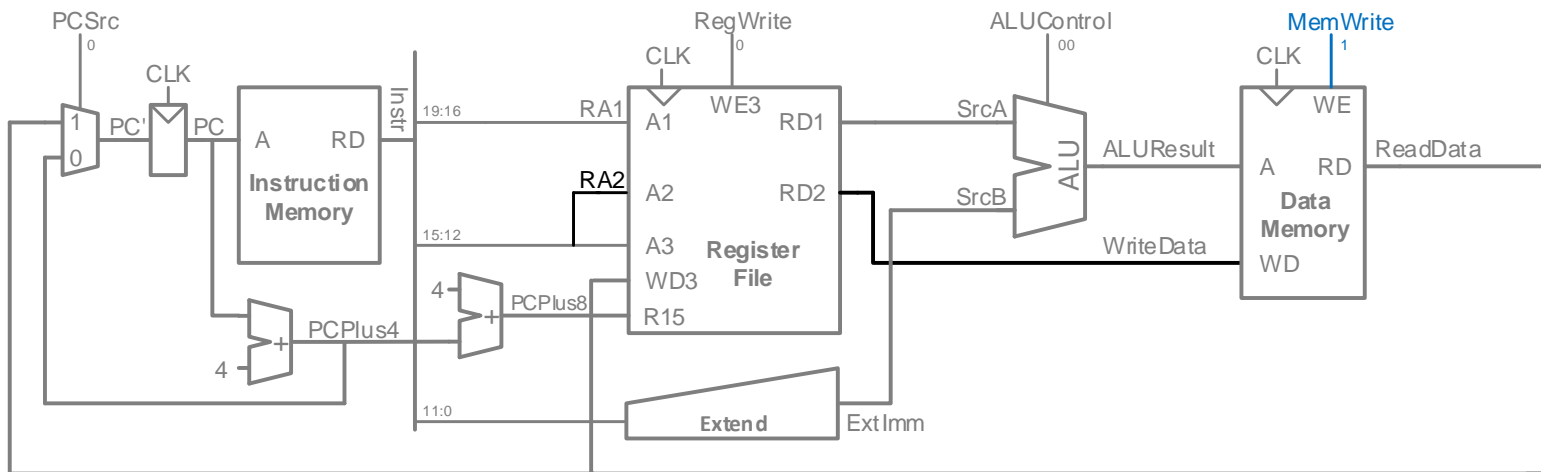

Single-Cycle Datapath: Data-processing

With **immediate Src2**:

 - Read from R_n and $Imm8$ (*ImmSrc* chooses the zero-extended $Imm8$ instead of $Imm12$)
- Write *ALUResult* to register file
- Write to R_d




ADD $R_d, R_n, imm8$



Single-Cycle Datapath: Data-processing

With **immediate Src2**:

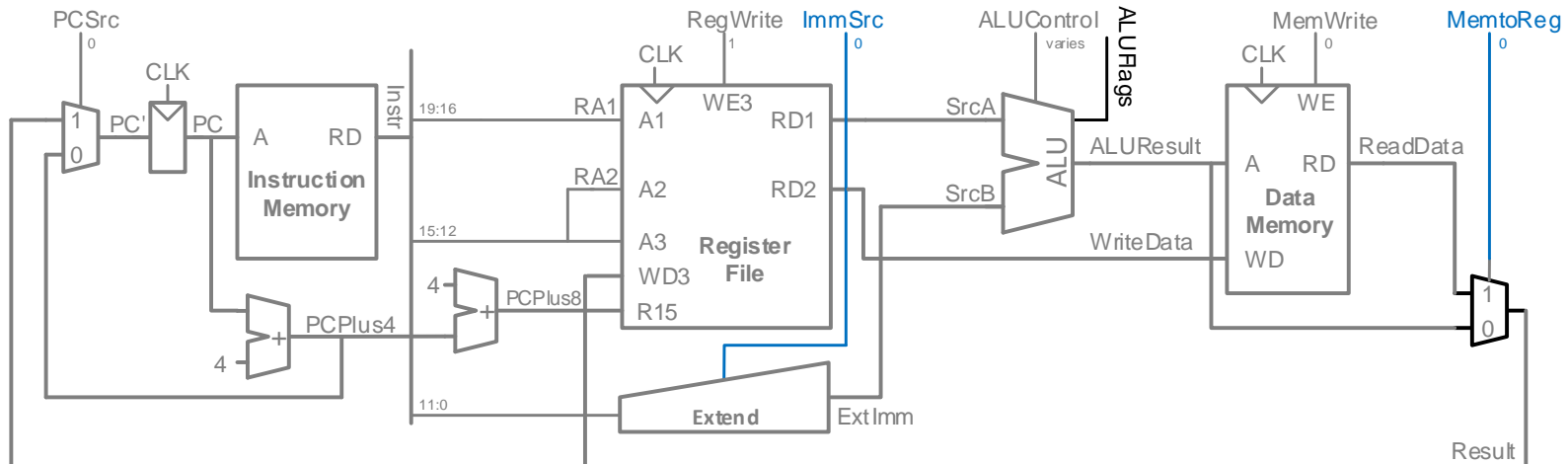- Read from R_n and $Imm8$ ($ImmSrc$ chooses the zero-extended $Imm8$ instead of $Imm12$)
- Write $ALUResult$ to register file
- Write to R_d




ADD R_d , R_n , $imm8$



Single-Cycle Datapath: Data-processing

With register Src2:

 - Read from R_n and R_m (instead of $Imm8$)
- Write $ALUResult$ to register file
- Write to R_d




ADD R_d , R_n , R_m



Single-Cycle Datapath: Data-processing

With register Src2:

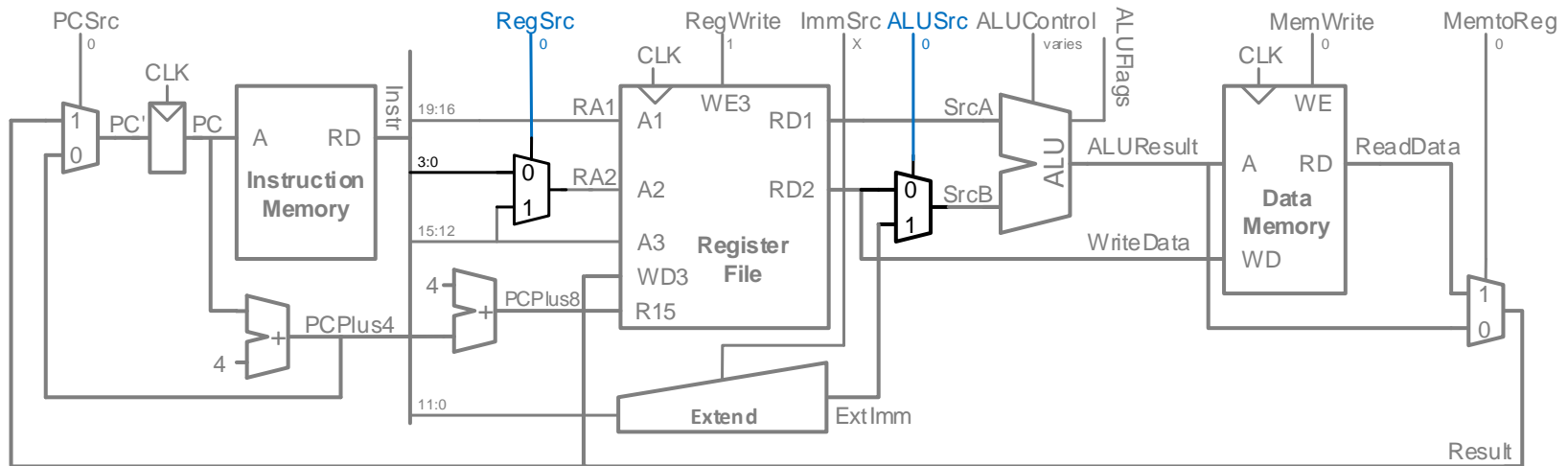- Read from Rn and Rm (instead of Imm8)
- Write *ALUResult* to register file
- Write to Rd




ADD Rd, Rn, Rm

Single-Cycle Datapath: B


Calculate branch target address:

$$\text{BTA} = (\text{ExtImm}) + (\text{PC} + 8)$$
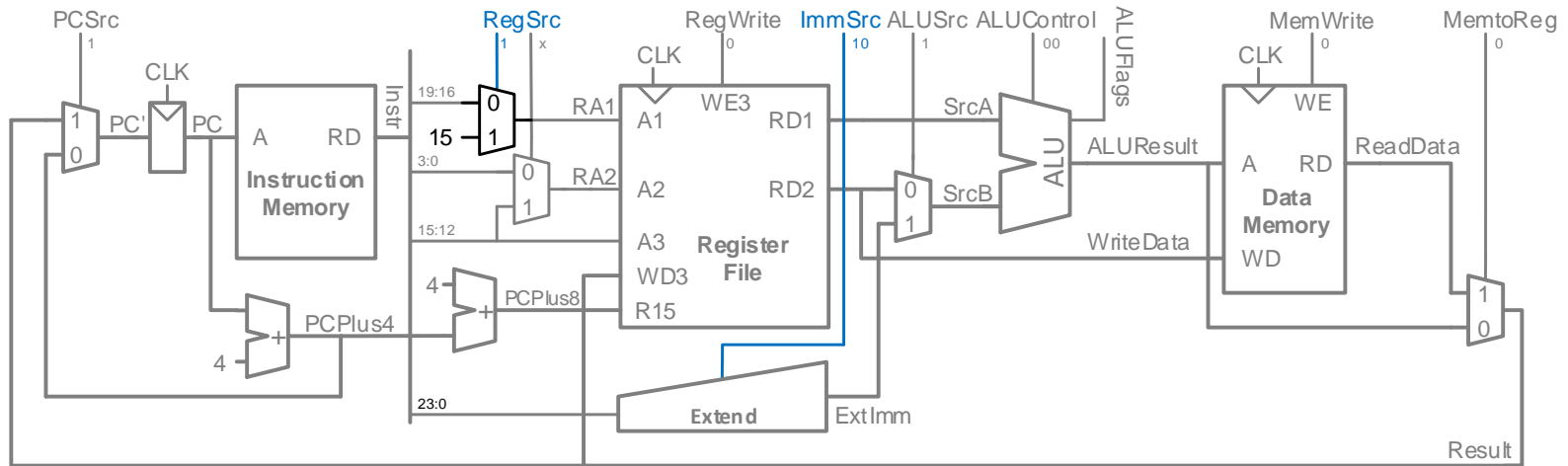
$$\text{ExtImm} = \text{Imm24} \ll 2 \text{ and sign-extended}$$



Branch

 


funct

B Label




Single-Cycle Datapath: ExtImm

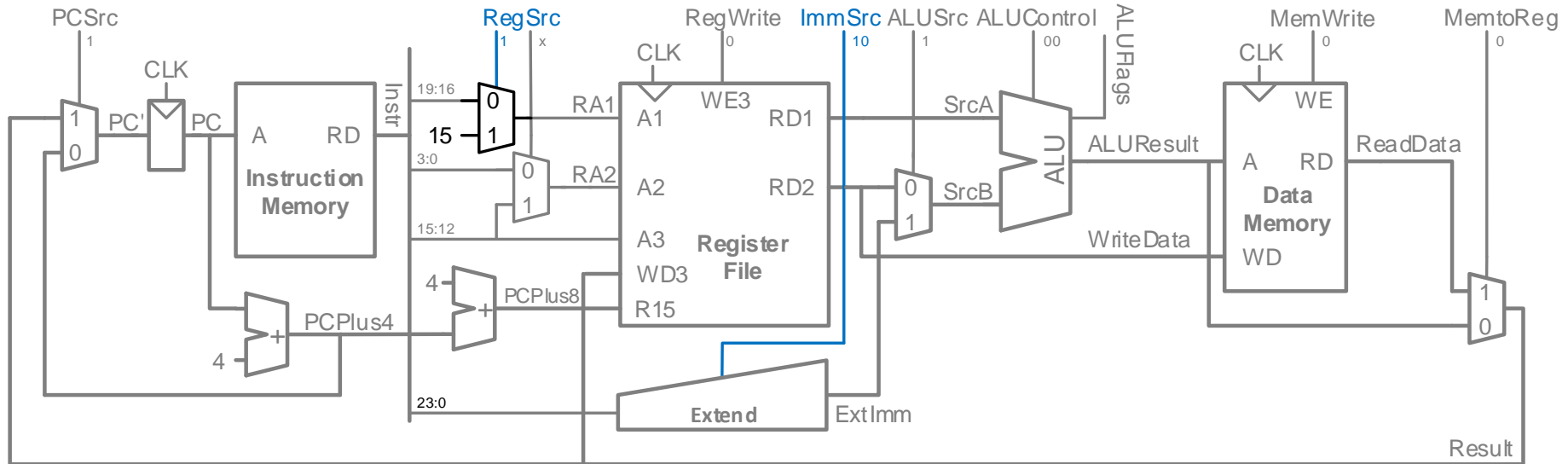


ImmSrc _{1:0}	ExtImm	Description
00	{24'b0, Instr _{7:0} }	Zero-extended <i>imm8</i>
01	{20'b0, Instr _{11:0} }	Zero-extended <i>imm12</i>
10	{6{Instr ₂₃ }, Instr _{23:0} }	Sign-extended <i>imm24</i>




Single-Cycle ARM Processor

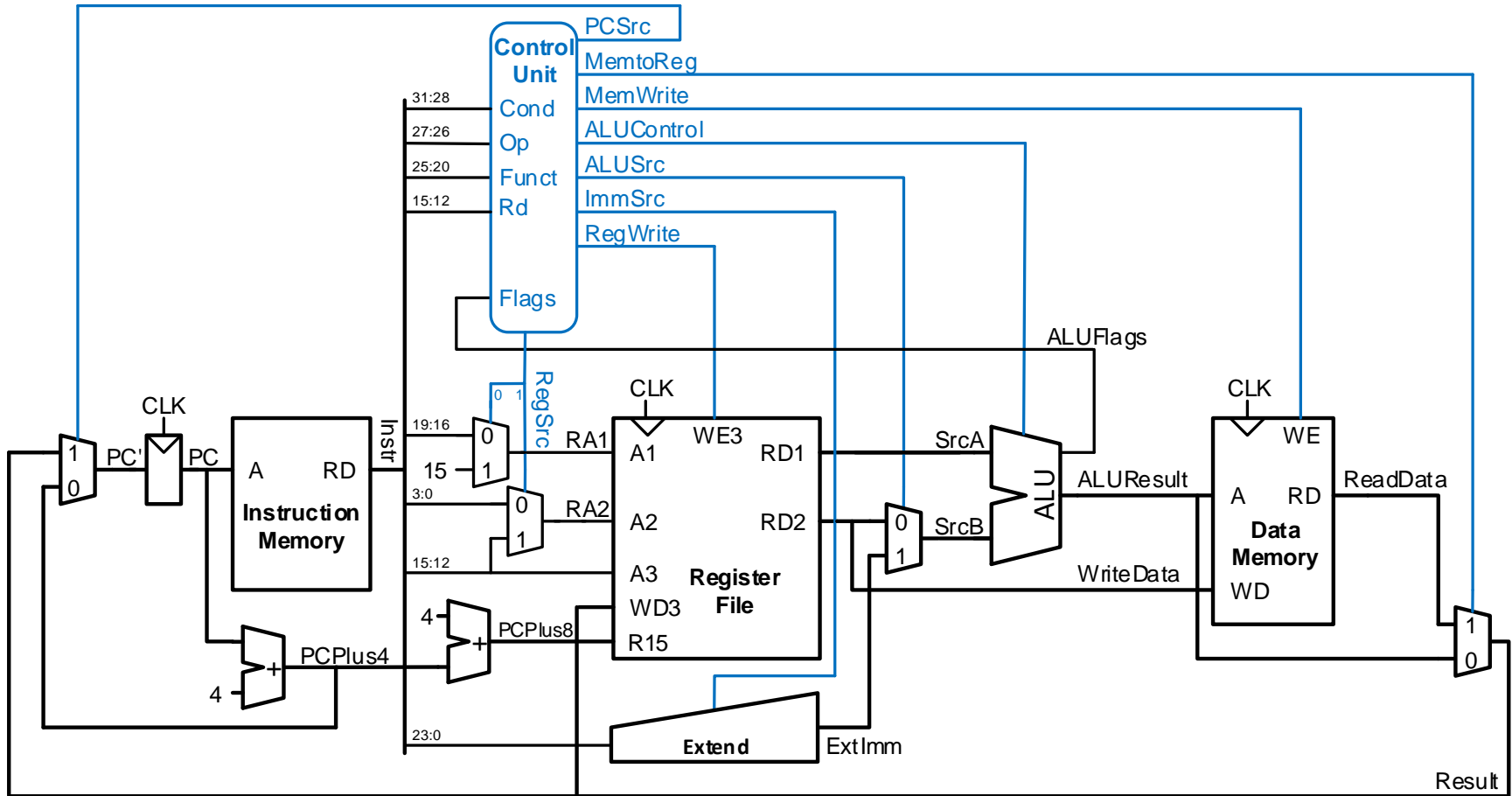


Single-Cycle Control

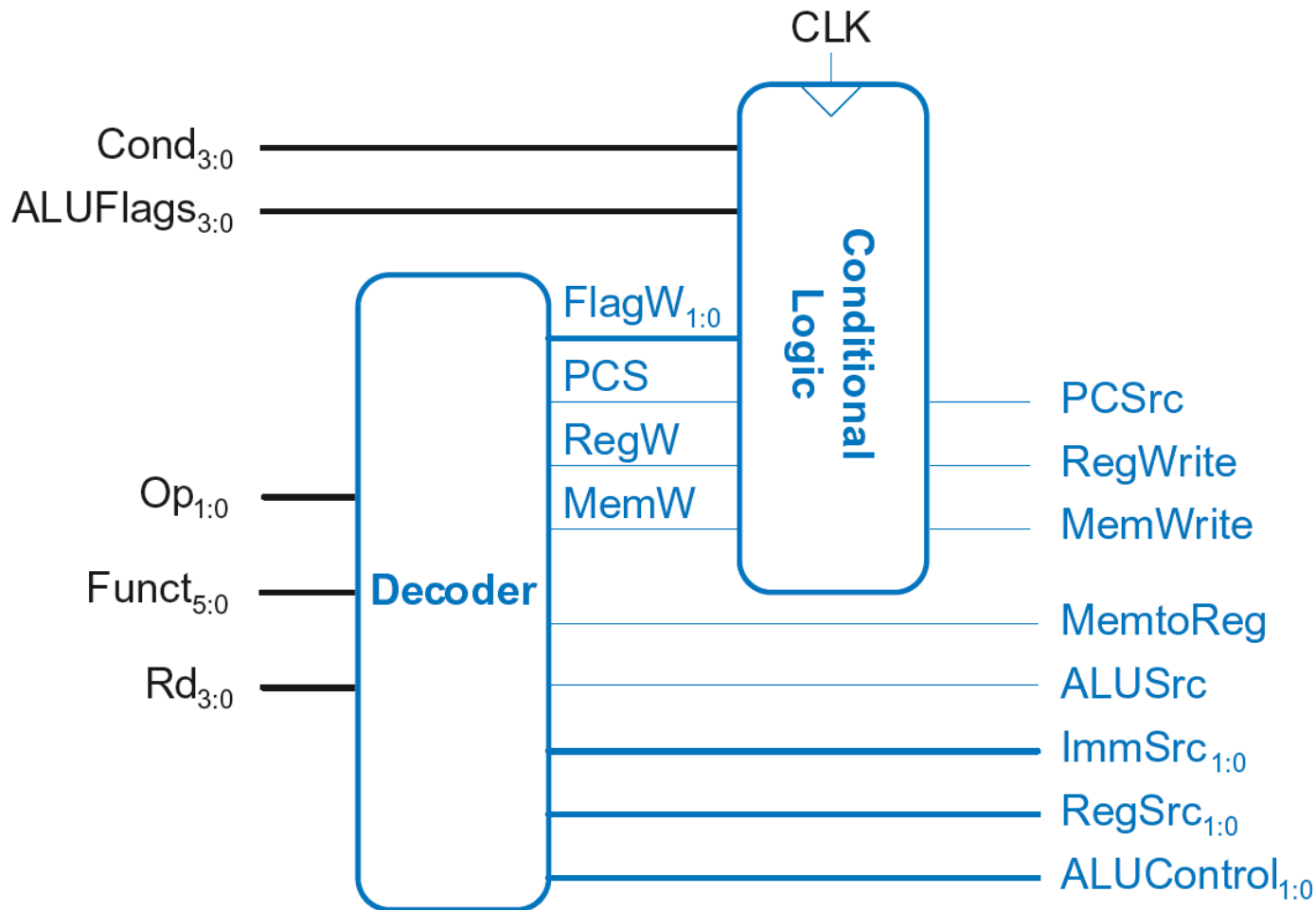


Single-Cycle Control

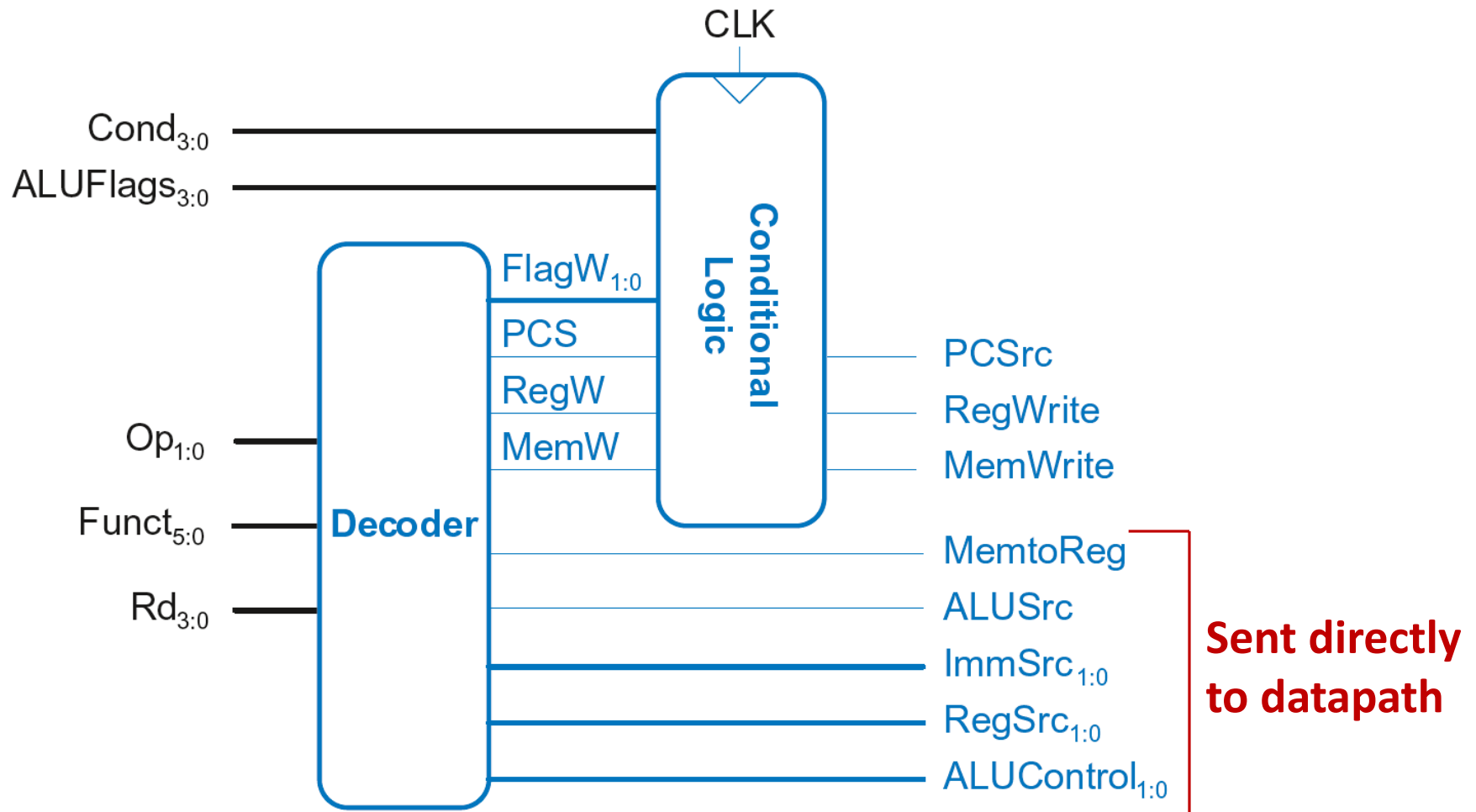


Single-Cycle Control

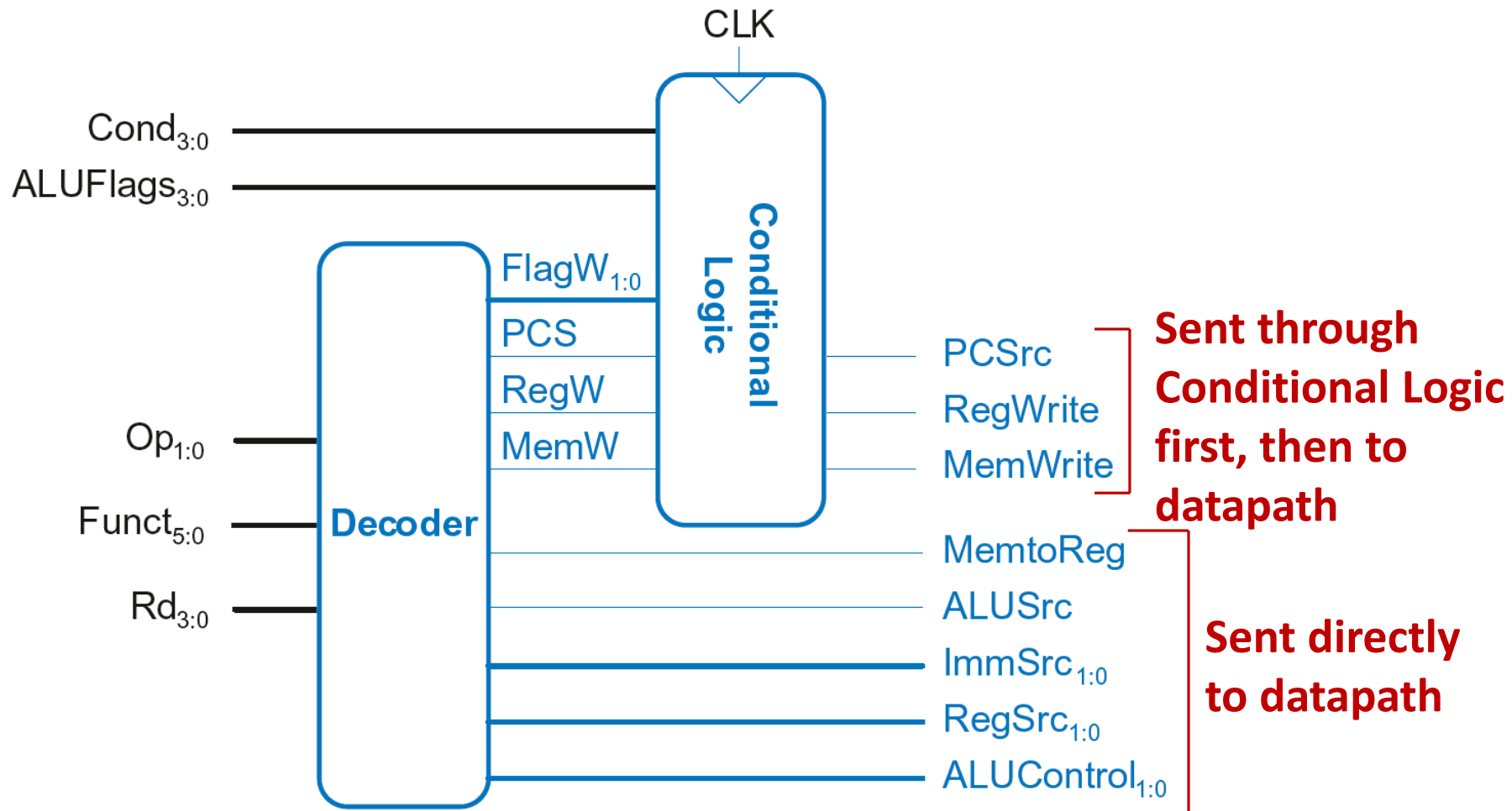

Single-Cycle Control

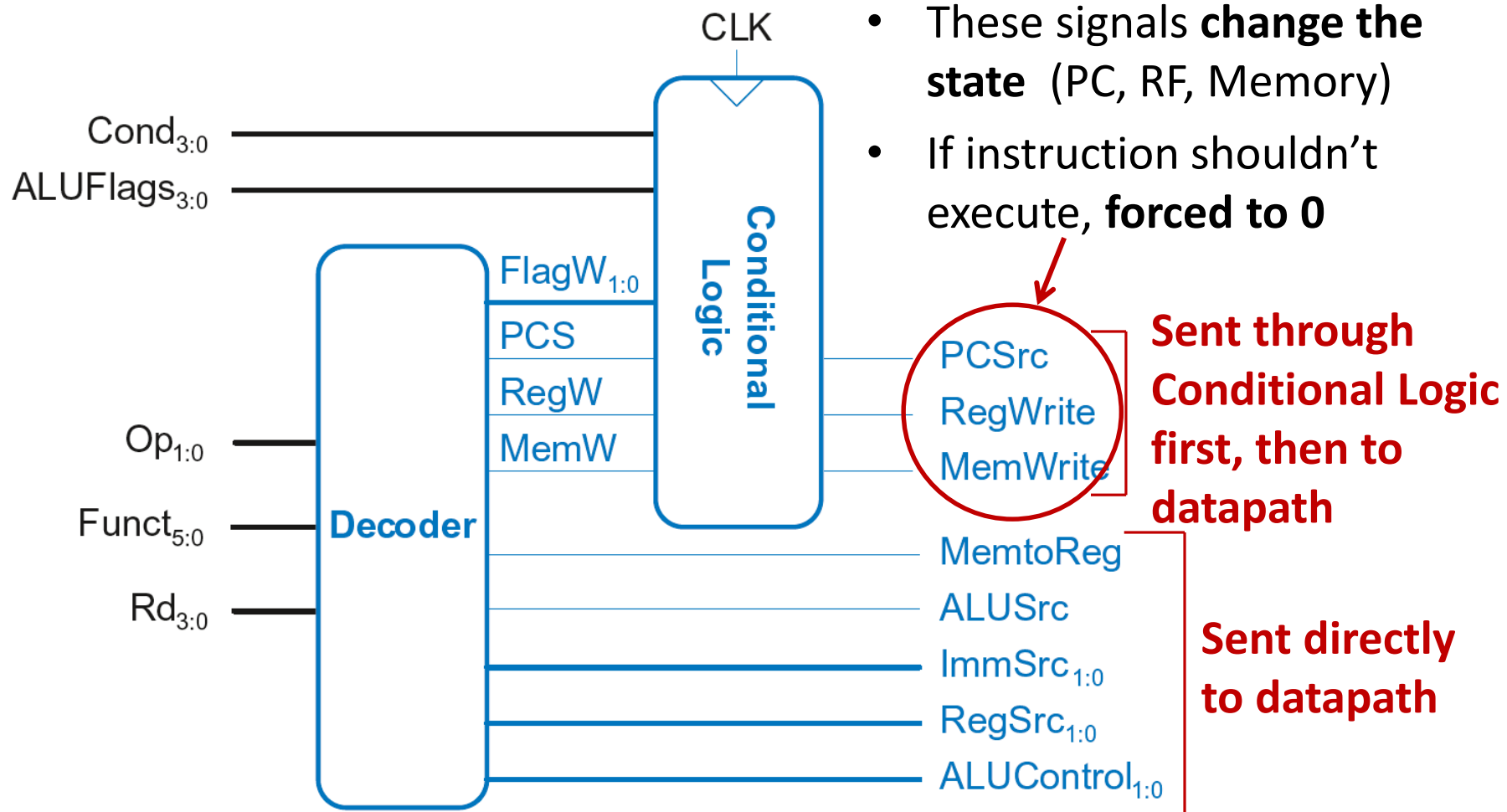


Single-Cycle Control

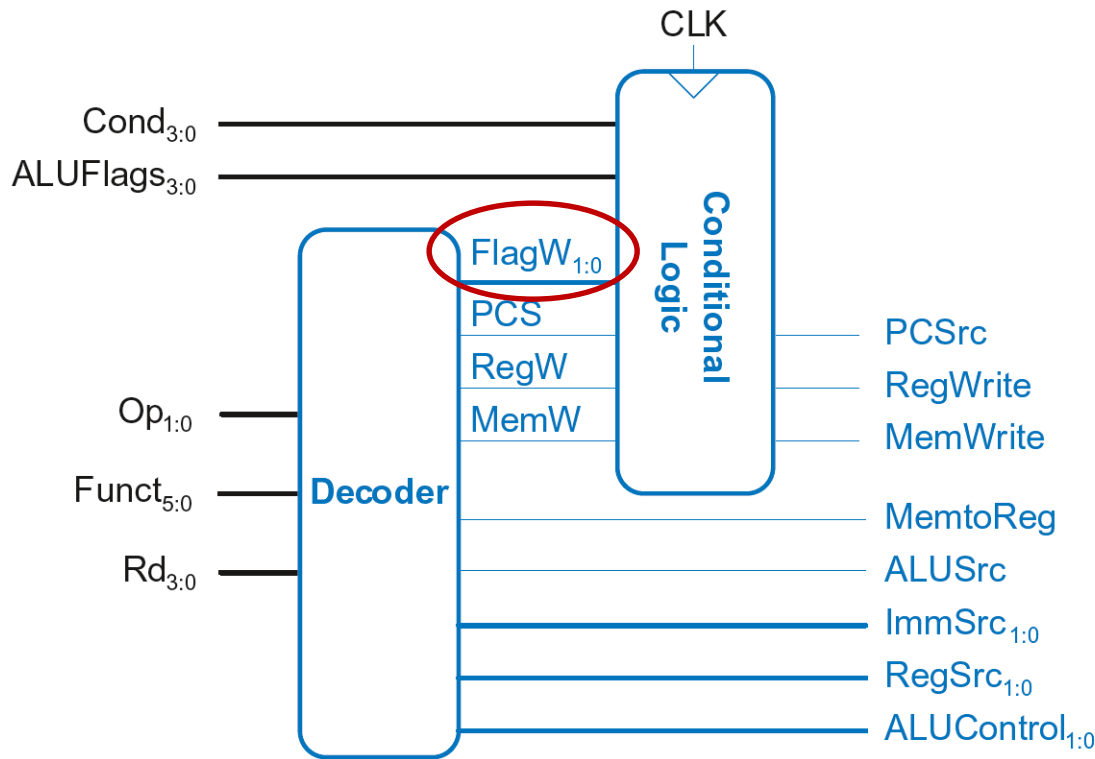

- **$FlagW_{1:0}$:** Flag Write signal, asserted when $ALUFlags$ should be saved (i.e., on instruction with $S=1$)




Single-Cycle Control

 

- **$FlagW_{1:0}$** : Flag Write signal, asserted when *ALUFlags* should be saved (i.e., on instruction with $S=1$)
- ADD, SUB update all flags (**NZCV**)
- AND, ORR only update **NZ** flags




Single-Cycle Control

 


- **FlagW_{1:0}**: Flag Write signal, asserted when *ALUFlags* should be saved (i.e., on instruction with $S=1$)
- ADD, SUB update all flags (**NZCV**)
- AND, ORR only update **NZ** flags
- So, two bits needed:
 - **FlagW₁ = 1**: NZ saved (*ALUFlags_{3:2}* saved)
 - **FlagW₀ = 1**: CV saved (*ALUFlags_{1:0}* saved)



Single-Cycle Control

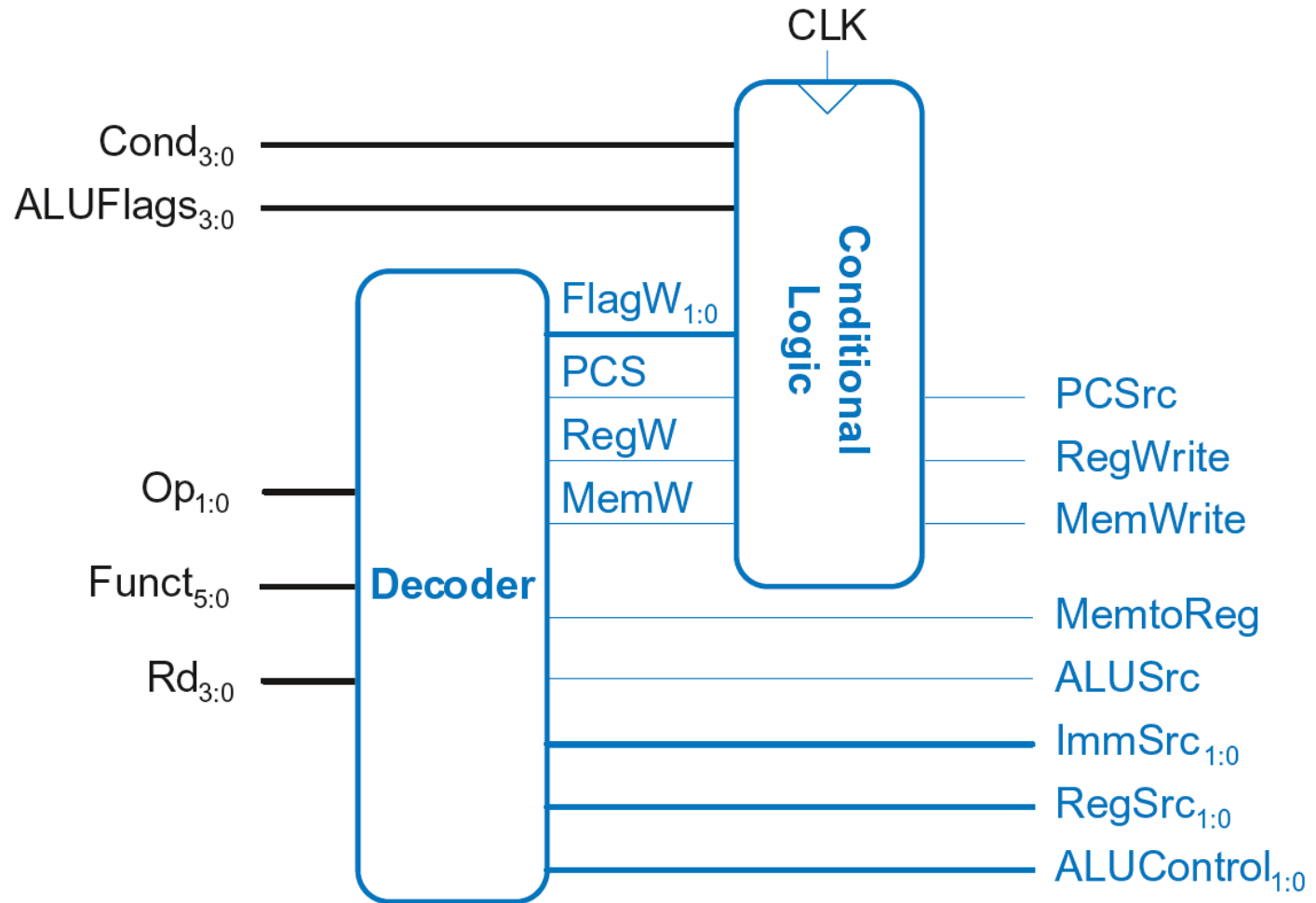


Single-Cycle Control: Decoder

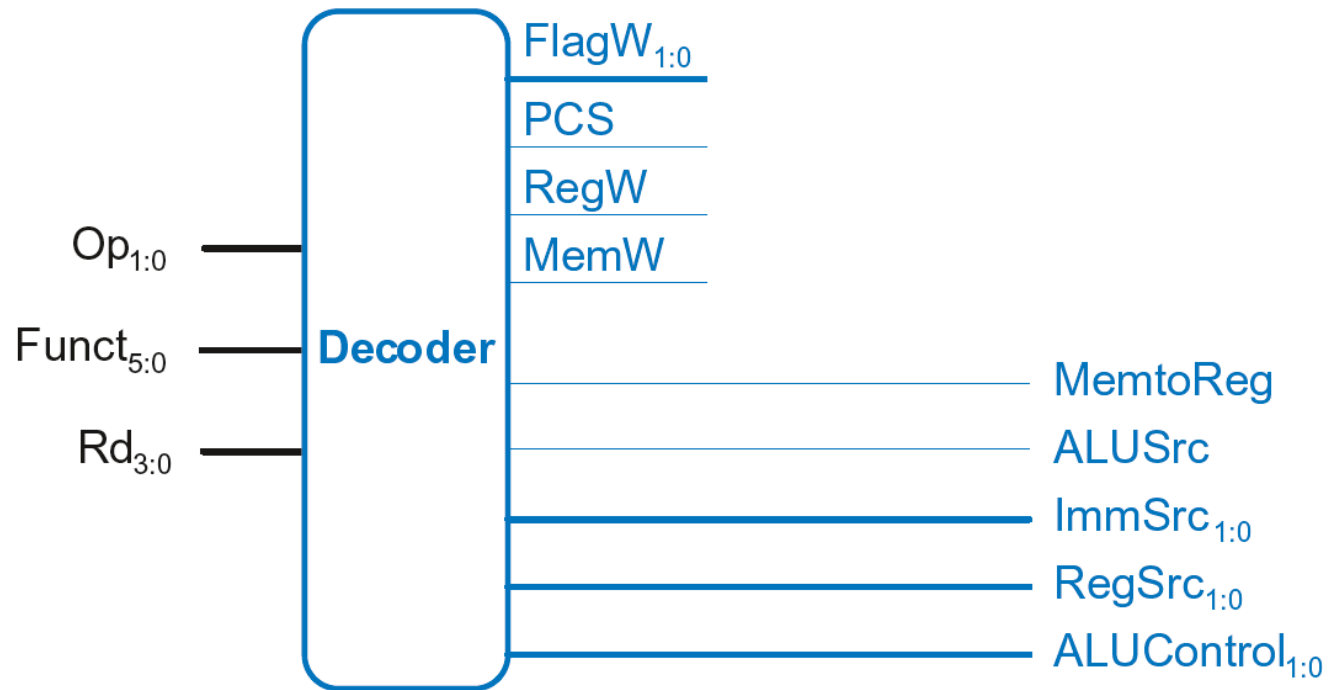

Single-Cycle Control: Decoder

Submodules:


- Main Decoder
- ALU Decoder
- PC Logic

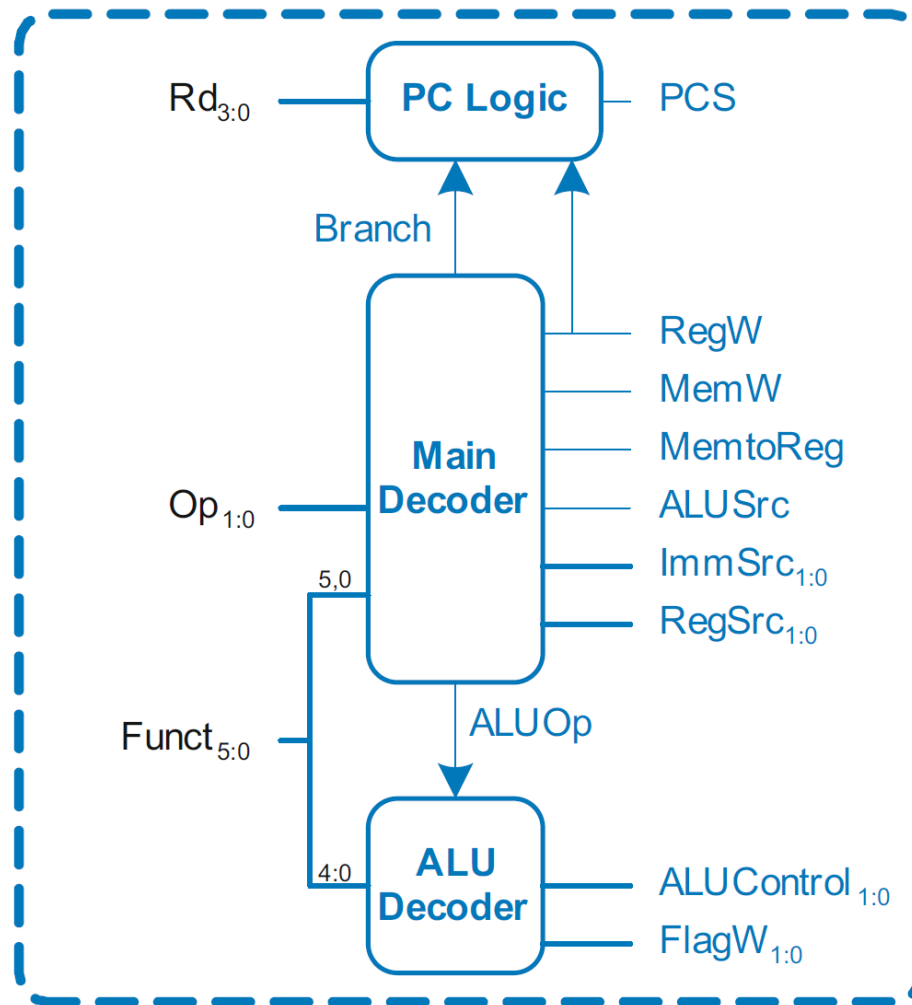

Single-Cycle Control: Decoder

Submodules:

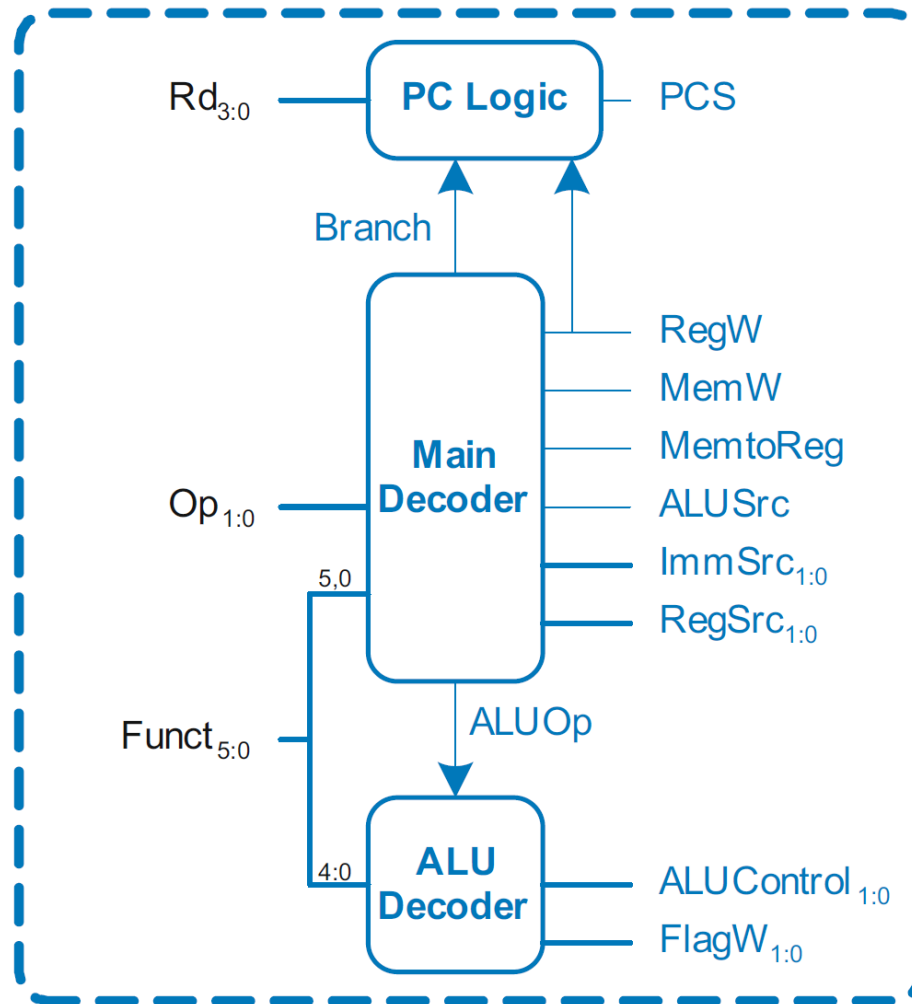- **Main Decoder**
- ALU Decoder
- PC Logic



Control Unit: Main Decoder


Op	Funct ₅	Funct ₀	Type	Branch	MemtoReg	MemW	ALUSrc	ImmSrc	RegW	RegSrc	ALUOp
00	0	X	DP Reg	0	0	0	0	XX	1	00	1
00	1	X	DP Imm	0	0	0	1	00	1	X0	1
01	X	0	STR	0	X	1	1	01	0	10	0
01	X	1	LDR	0	1	0	1	01	1	X0	0
11	X	X	B	1	0	0	1	10	0	X1	0



Single-Cycle Control: Decoder


Submodules:

 - Main Decoder
- **ALU Decoder**
- PC Logic




Review: ALU

ALUControl _{1:0}	Function
00	Add
01	Subtract
10	AND
11	OR

 


Review: ALU

 

Single-Cycle Control: Decoder

Submodules:

 - Main Decoder
- **ALU Decoder**
- PC Logic



Control Unit: ALU Decoder

ALUOp	Funct _{4:1} (cmd)	Funct ₀ (S)	Type	ALUControl _{1:0}	FlagW _{1:0}
0	X	X	Not DP	00	00
1	0100	0	ADD	00	00
		1			11
	0010	0	SUB	01	00
		1			11
	0000	0	AND	10	00
		1			10
	1100	0	ORR	11	00
		1			10


- $FlagW_1 = 1$: NZ ($Flags_{3:2}$) should be saved
- $FlagW_0 = 1$: CV ($Flags_{1:0}$) should be saved



Single-Cycle Control: Decoder

Submodules:

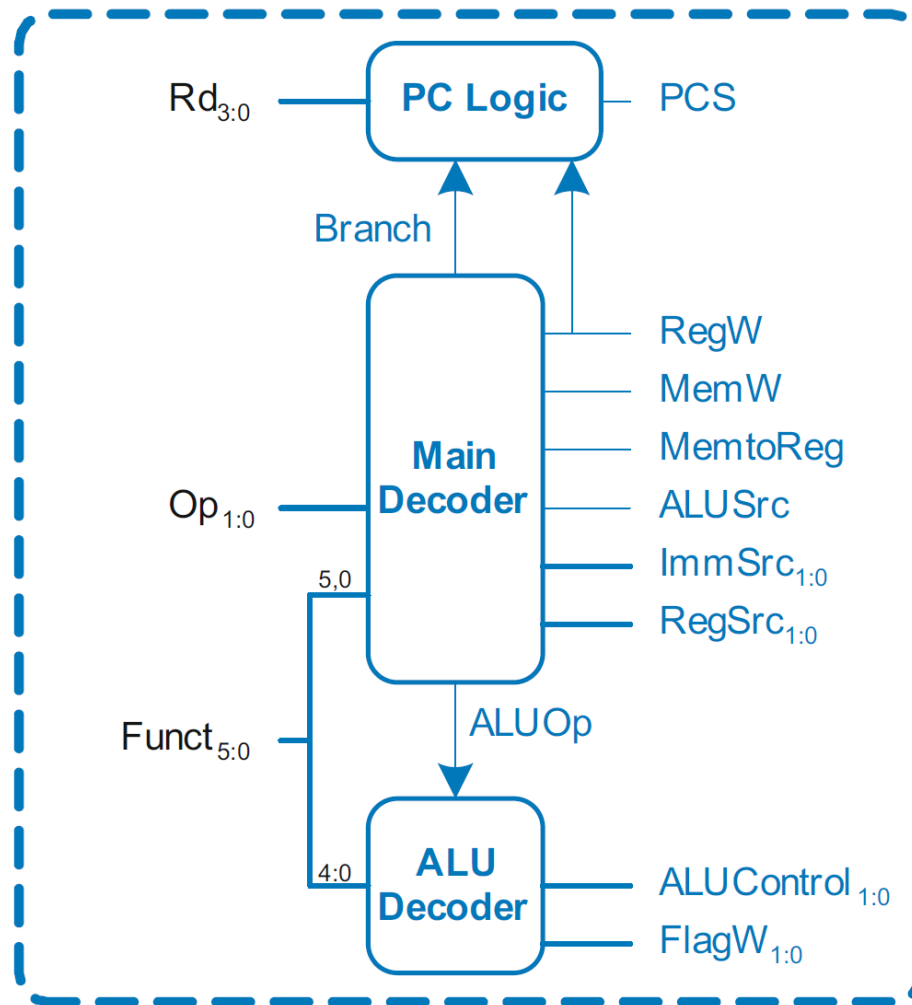
- Main Decoder
- ALU Decoder
- **PC Logic**



Single-Cycle Control: PC Logic

PCSrc = 1 if PC is written by an instruction or branch (B):

$$PCSrc = ((Rd == 15) \& RegW) | Branch$$

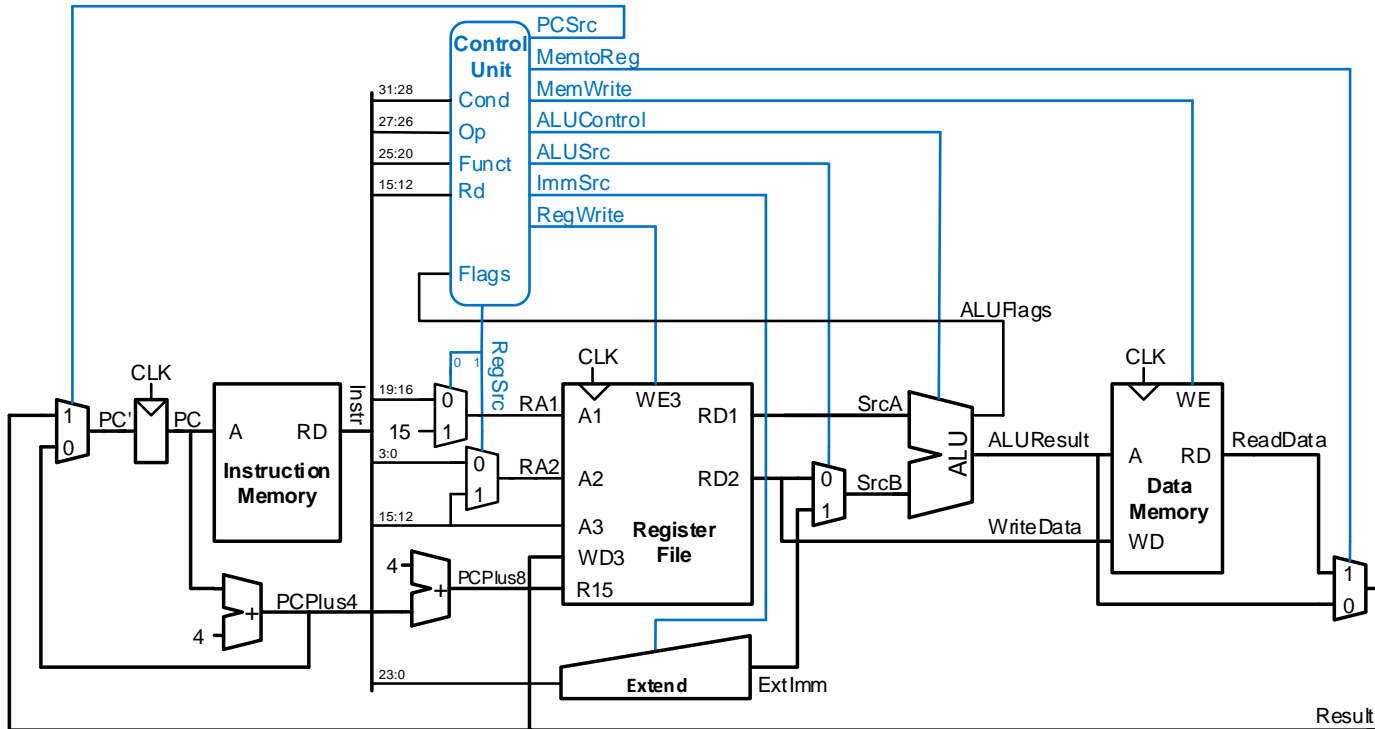


If instruction is executed: $PCSrc = PCS$

Else


$PCSrc = 0$ (i.e., $PC = PC + 4$)




Single-Cycle Control

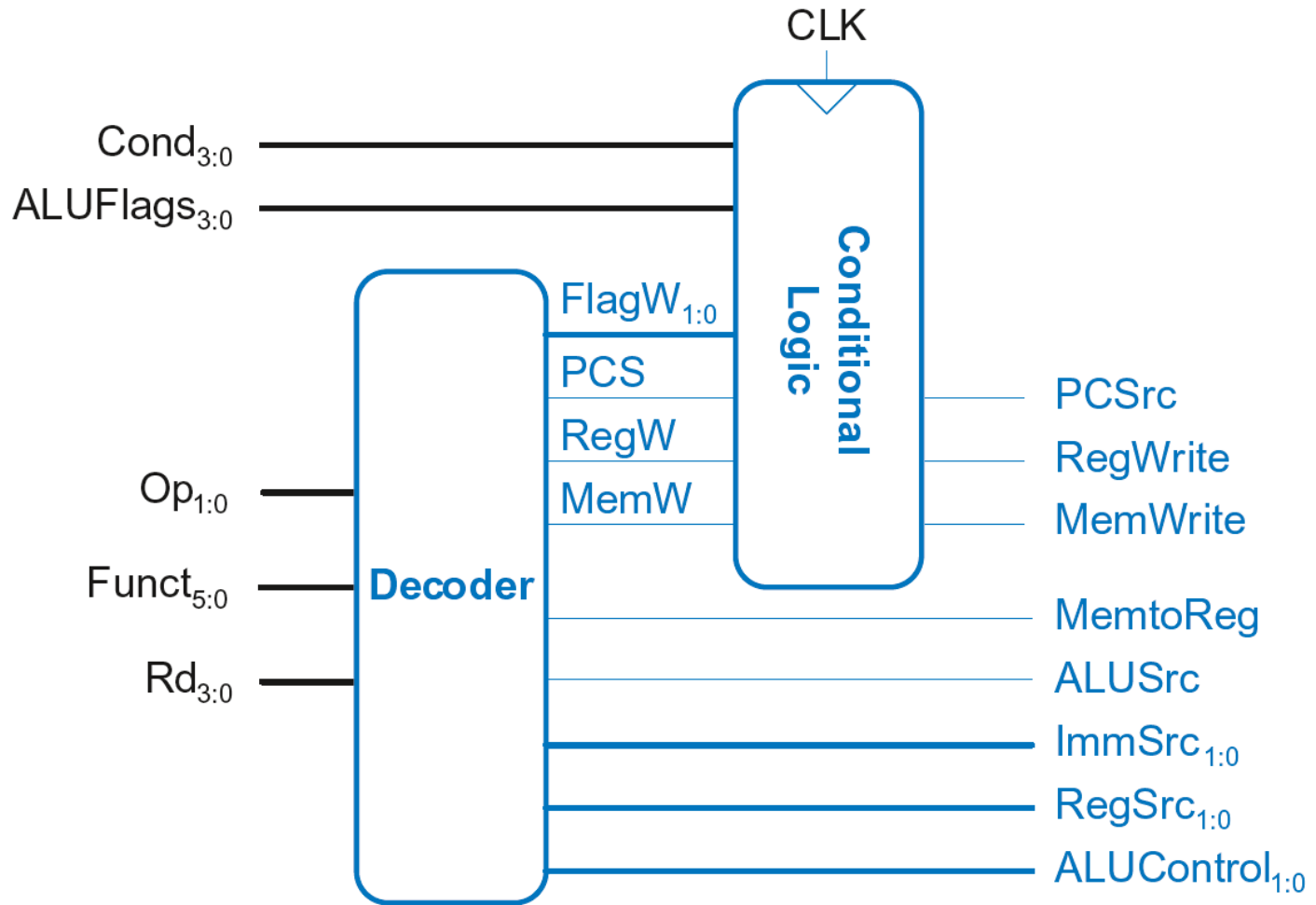

Single-Cycle Control: Cond. Logic

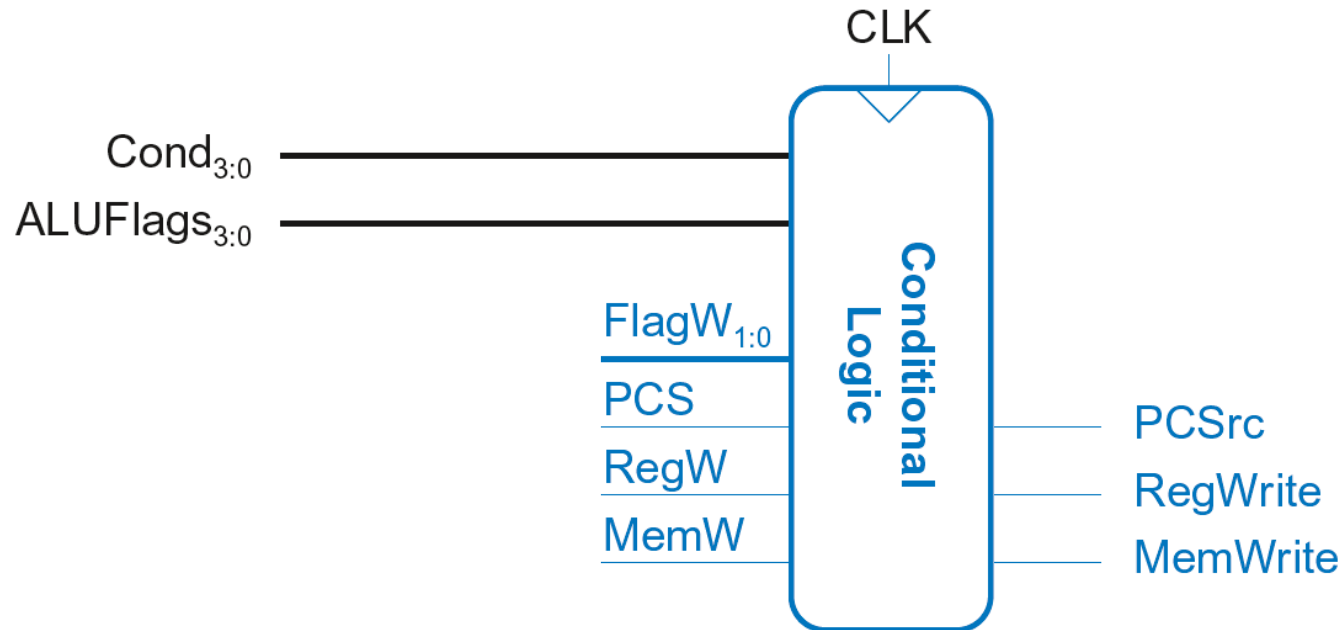

Conditional Logic

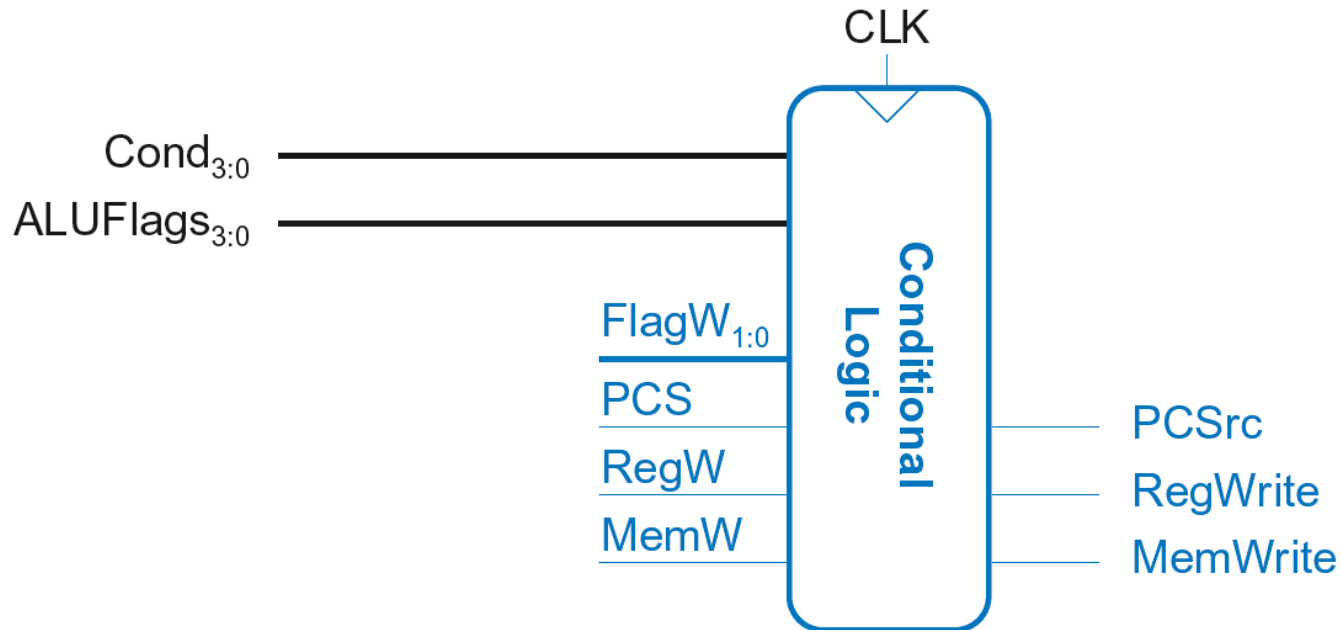


Function:

1. Check if instruction should execute (if not, force PCSrc, RegWrite, and MemWrite to 0)
2. Possibly update Status Register (Flags_{3:0})



Conditional Logic

 


Function:


1. Check if instruction should execute (if not, force PCSrc, RegWrite, and MemWrite to 0)
2. Possibly update Status Register (Flags_{3:0})



Single-Cycle Control: Conditional Logic

 

Conditional Logic: Conditional Execution

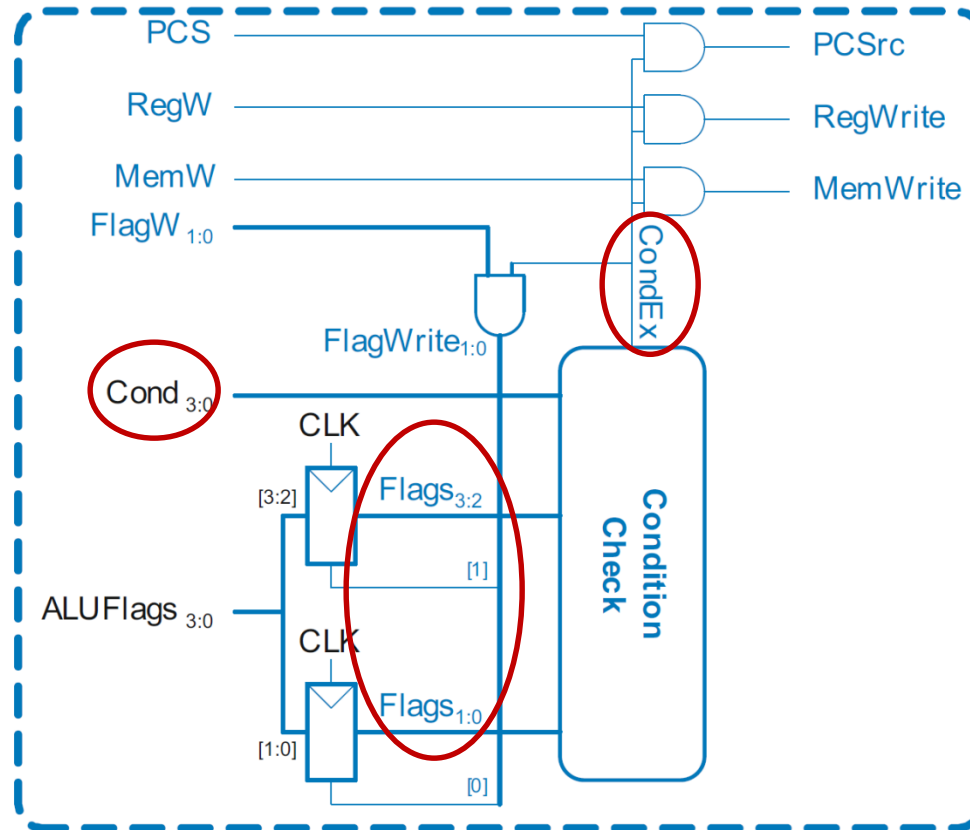


Depending on condition mnemonic (**Cond**_{3:0}) and condition flags (**Flags**_{3:0}) the instruction is executed (**CondEx** = 1)



Conditional Logic: Conditional Execution

Flags_{3:0} is the
status register

 

Depending on condition mnemonic (**Cond_{3:0}**) and condition flags (**Flags_{3:0}**) the instruction is executed (**CondEx = 1**)




Review: Condition Mnemonics

Cond _{3:0}	Mnemonic	Name	CondEx
0000	EQ	Equal	Z
0001	NE	Not equal	\bar{Z}
0010	CS / HS	Carry set / Unsigned higher or same	C
0011	CC / LO	Carry clear / Unsigned lower	\bar{C}
0100	MI	Minus / Negative	N
0101	PL	Plus / Positive of zero	\bar{N}
0110	VS	Overflow / Overflow set	V
0111	VC	No overflow / Overflow clear	\bar{V}
1000	HI	Unsigned higher	$\bar{Z}C$
1001	LS	Unsigned lower or same	$Z OR \bar{C}$
1010	GE	Signed greater than or equal	$\overline{N \oplus V}$
1011	LT	Signed less than	$N \oplus V$
1100	GT	Signed greater than	$\bar{Z}(\overline{N \oplus V})$
1101	LE	Signed less than or equal	$Z OR (N \oplus V)$
1110	AL (or none)	Always / unconditional	ignored



Conditional Logic: Conditional Execution

$\text{Flags}_{3:0} = \text{NZCV}$

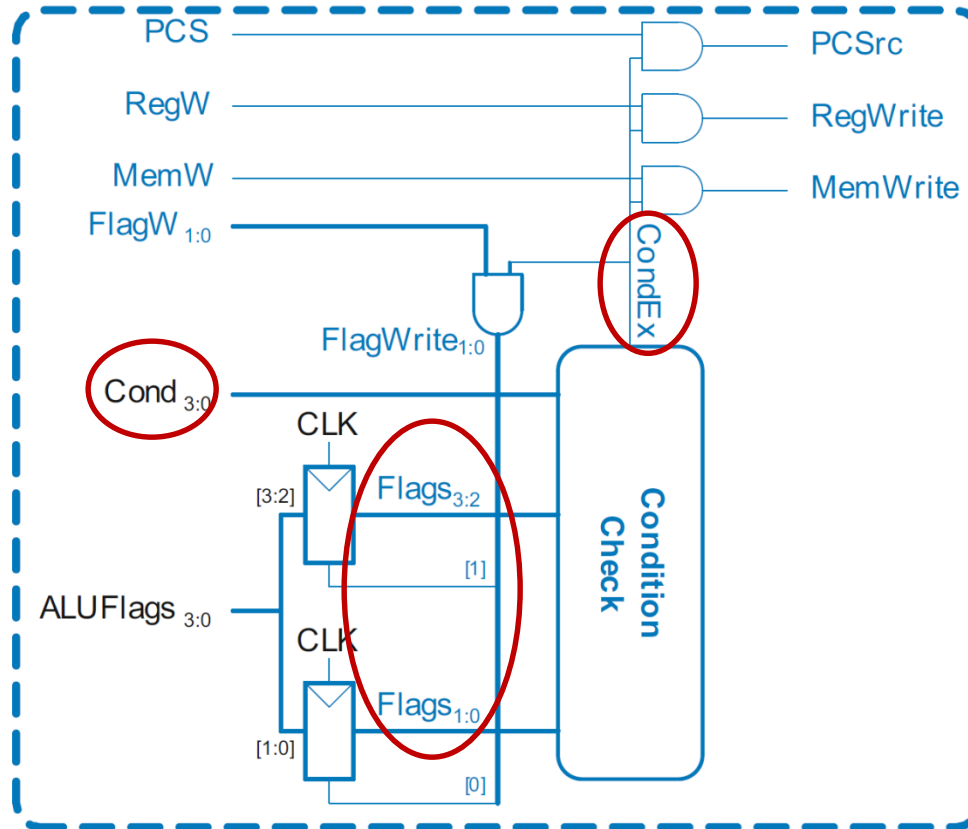

Example:

AND R1, R2, R3


$\text{Cond}_{3:0} = 1110$ (unconditional)

$\Rightarrow \text{CondEx} = 1$



Conditional Logic: Conditional Execution

Flags_{3:0} = NZCV

 


Example:

EOREQ R5, R6, R7

Cond_{3:0}=0000 (EQ): if Flags_{3:2}=0100 => CondEx = 1



Conditional Logic

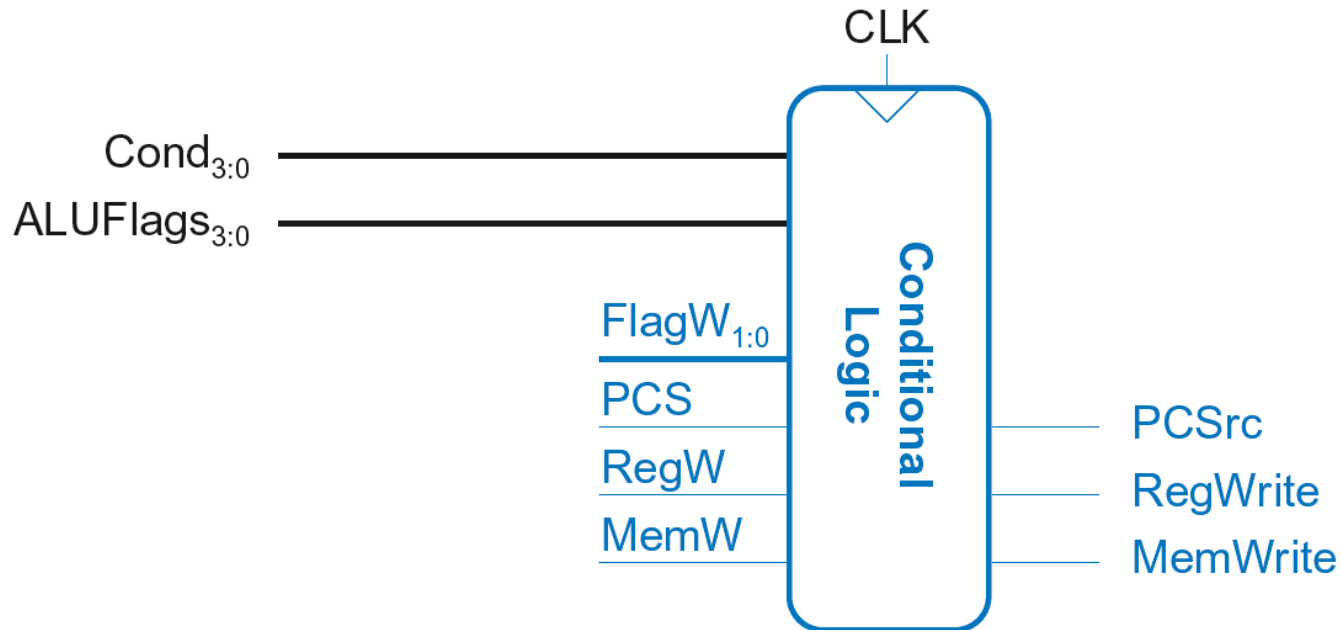


Function:

1. Check if instruction should execute (if not, force PCSrc, RegWrite, and MemWrite to 0)
2. **Possibly update Status Register (Flags_{3:0})**



Conditional Logic: Update (Set) Flags

$\text{Flags}_{3:0} = \text{NZCV}$

 


$\text{Flags}_{3:0}$ **updated** (with $\text{ALUFlags}_{3:0}$) if:

- **FlagW** is 1 (i.e., the instruction's S-bit is 1) AND
- **CondEx** is 1 (the instruction should be executed)



Conditional Logic: Update (Set) Flags

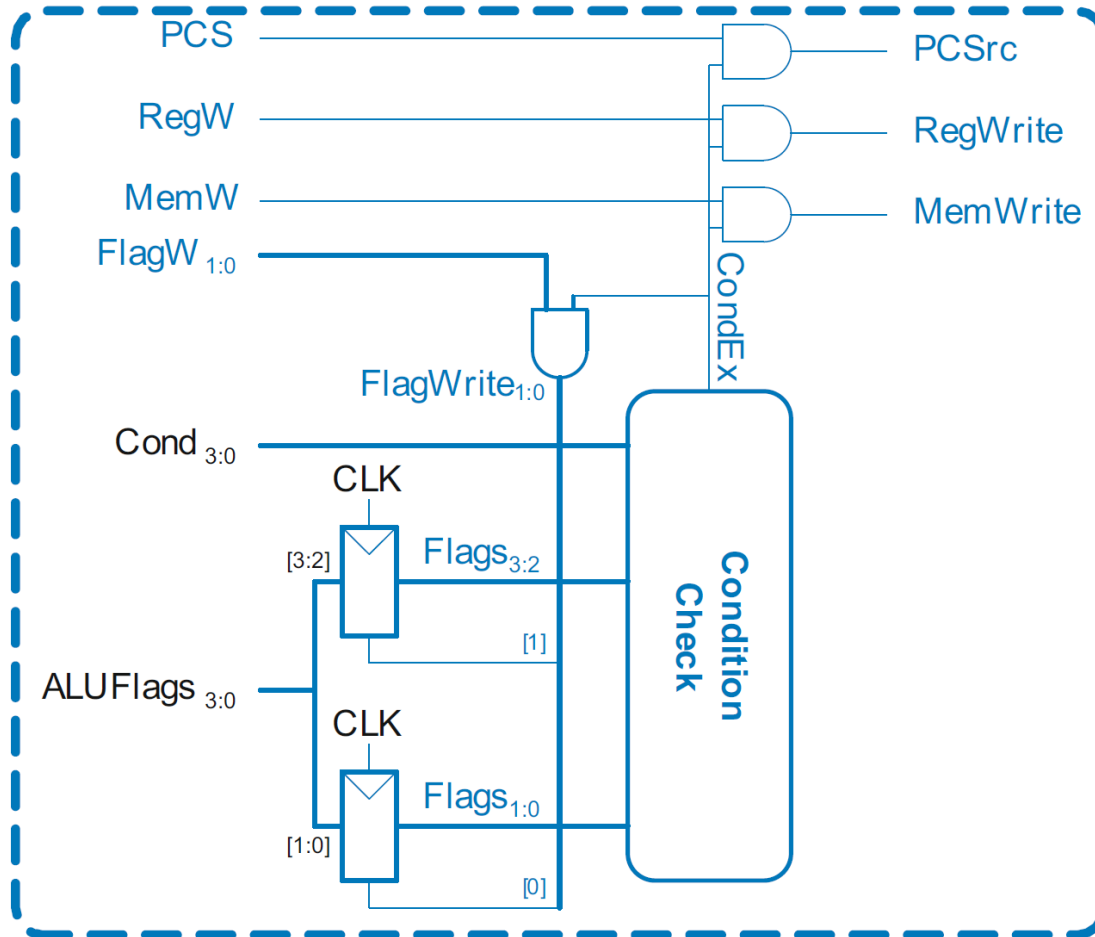

Recall:

- ADD, SUB update **all** Flags
- AND, OR update **NZ only**
- So Flags status register has two write enables:
FlagW_{1:0}



Review: ALU Decoder


ALUOp	Funct _{4:1} (cmd)	Funct ₀ (S)	Type	ALUControl _{1:0}	FlagW _{1:0}
0	X	X	Not DP	00	00
1	0100	0	ADD	00	00
		1			11
	0010	0	SUB	01	00
		1			11
	0000	0	AND	10	00
		1			10
	1100	0	ORR	11	00
		1			10

- $FlagW_1 = 1$: NZ ($Flags_{3:2}$) should be saved
- $FlagW_0 = 1$: CV ($Flags_{1:0}$) should be saved



Conditional Logic: Update (Set) Flags

All Flags updated

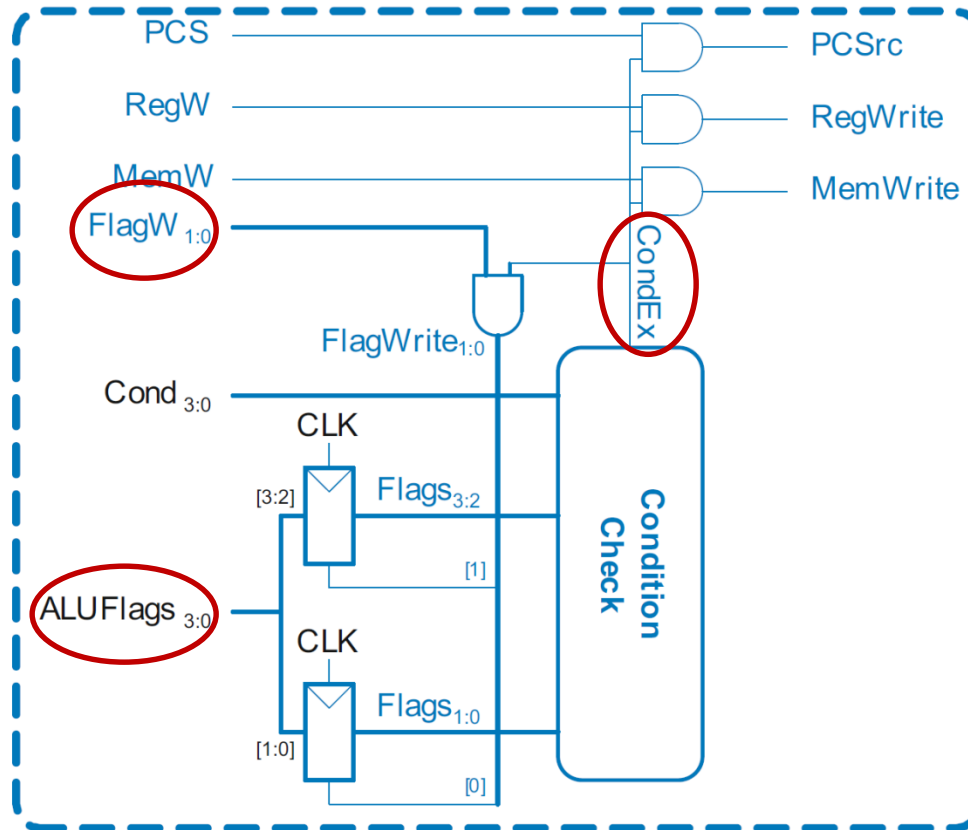

Example: SUBS R5, R6, R7


$\text{FlagW}_{1:0} = 11$ AND $\text{CondEx} = 1$ (unconditional) $\Rightarrow \text{FlagWrite}_{1:0} = 11$



Conditional Logic: Update (Set) Flags

$\text{Flags}_{3:0} = \text{NZCV}$

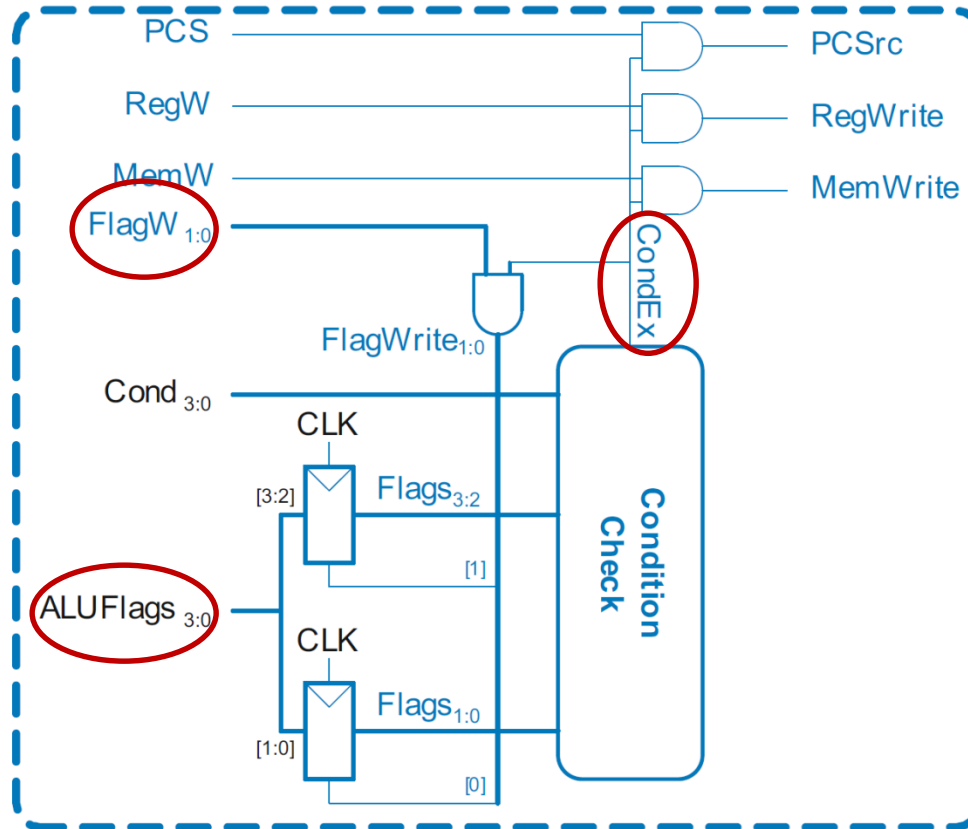- Only $\text{Flags}_{3:2}$ updated
- i.e., only **NZ** Flags updated




Example: ANDS R7, R1, R3

$\text{FlagW}_{1:0} = 10$ AND $\text{CondEx} = 1$ (unconditional) $\Rightarrow \text{FlagWrite}_{1:0} = 10$




Example: ORR


Op	Funct ₅	Funct ₀	Type	Branch	MementoReg	MemW	ALUSrc	ImmSrc	RegW	RegSrc	ALUOp
00	0	X	DP Reg	0	0	0	0	XX	1	00	1

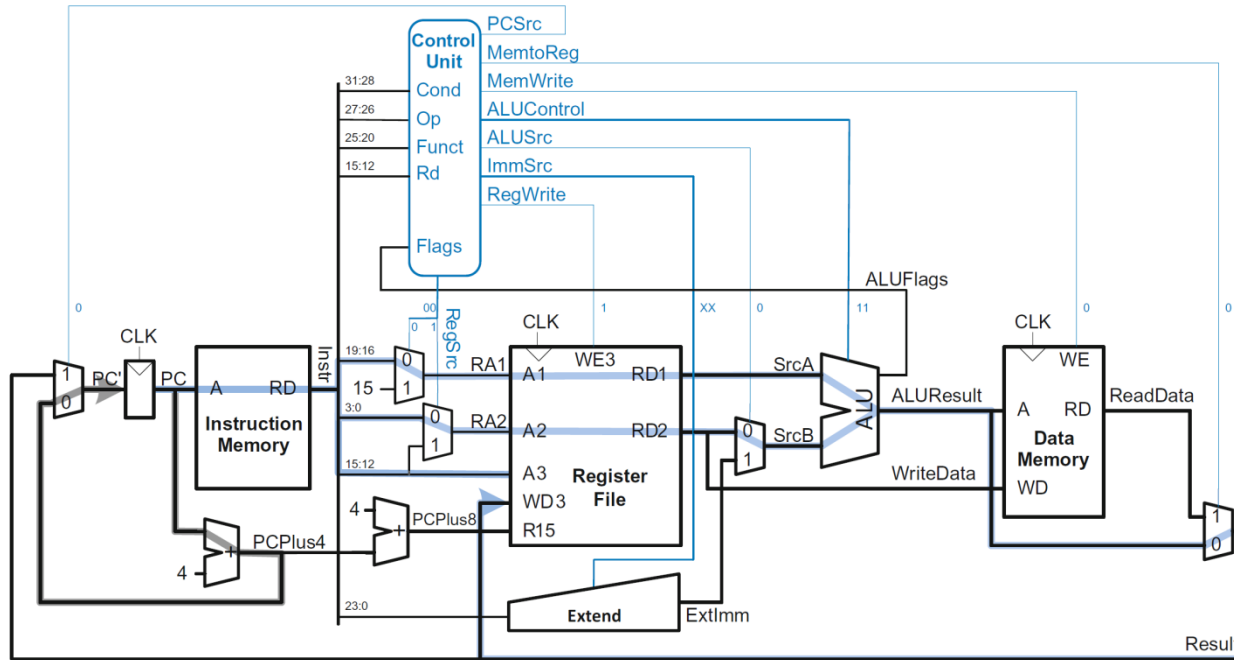


Example: ORR

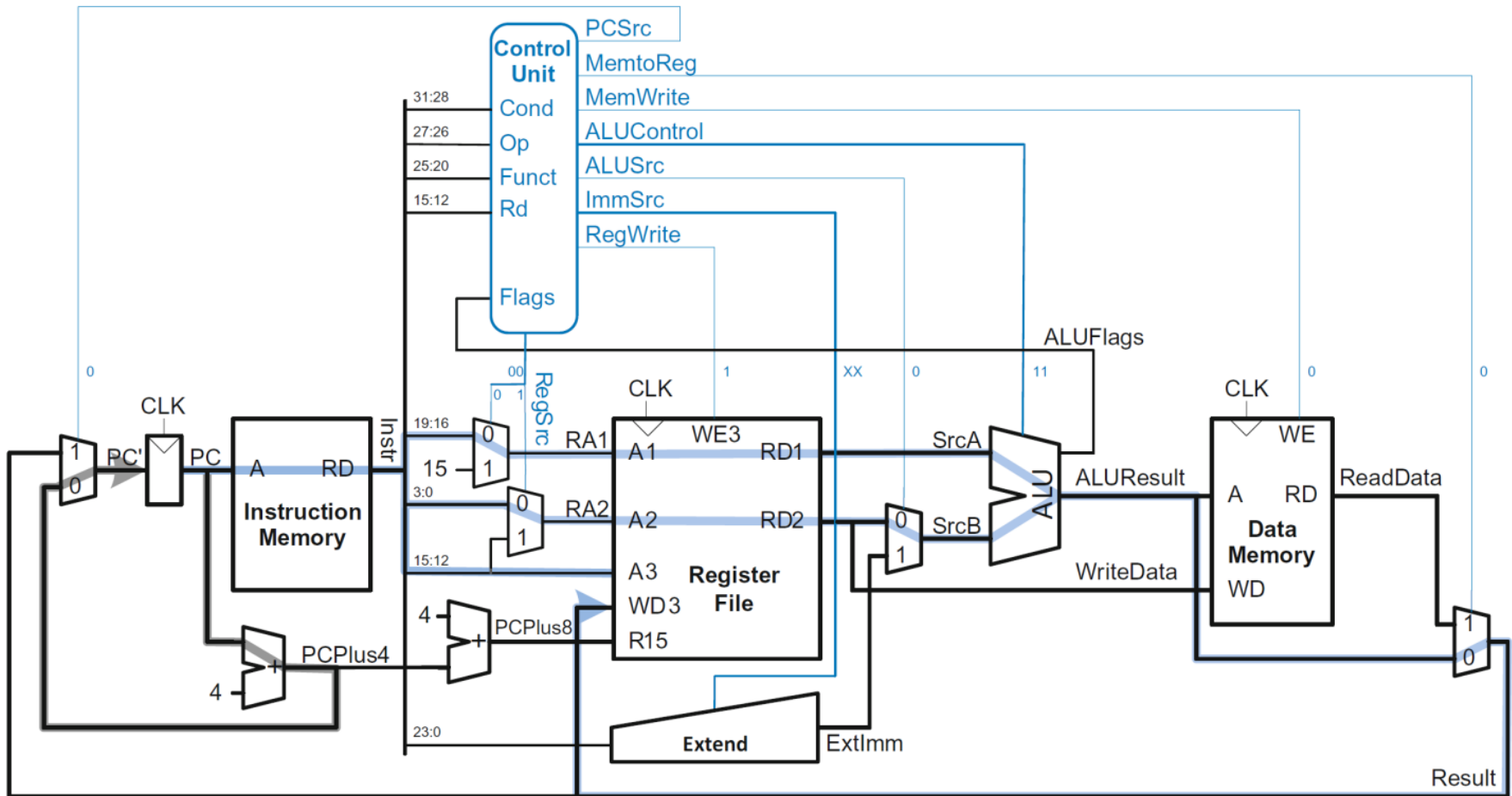

Extended Functionality: CMP

 


Extended Functionality: CMP

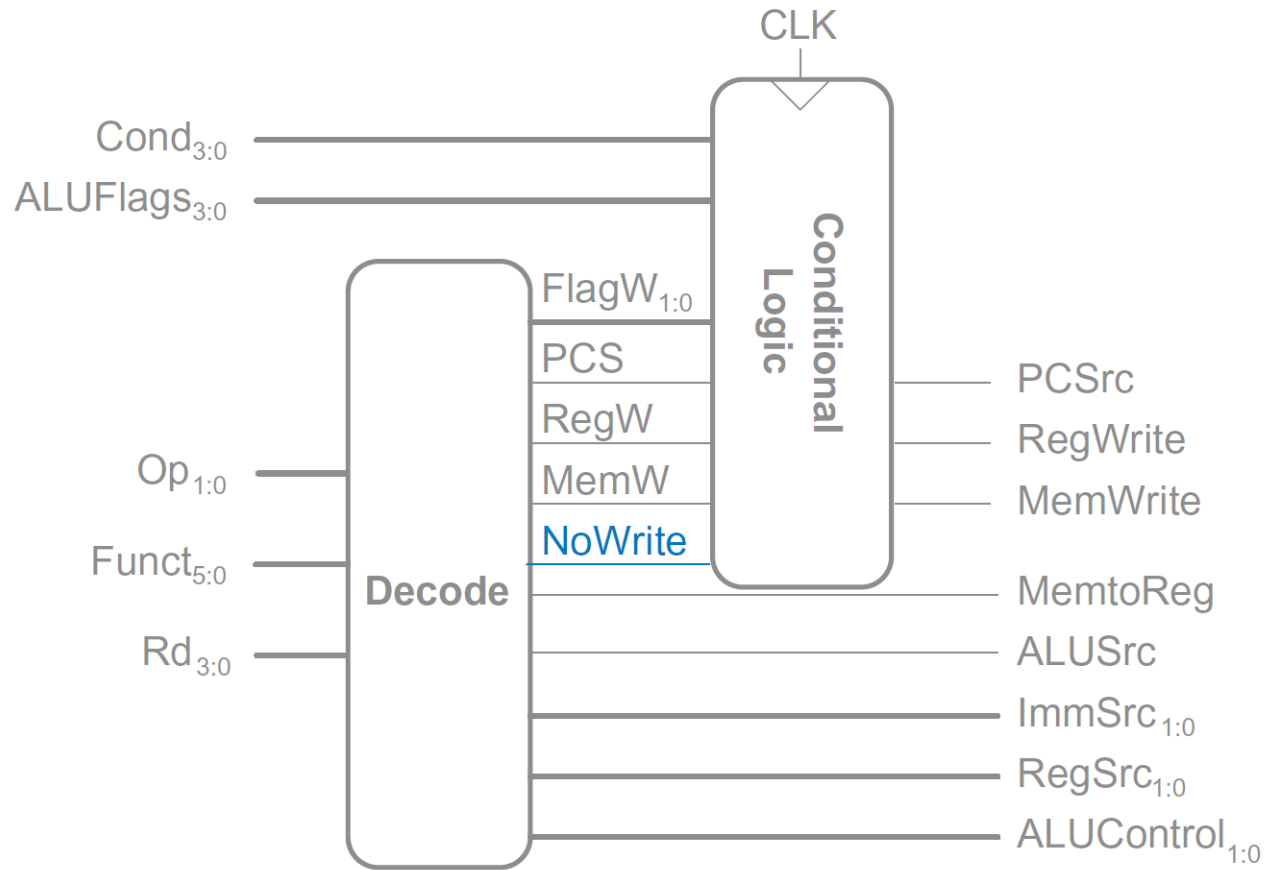

No change to datapath



Extended Functionality: CMP

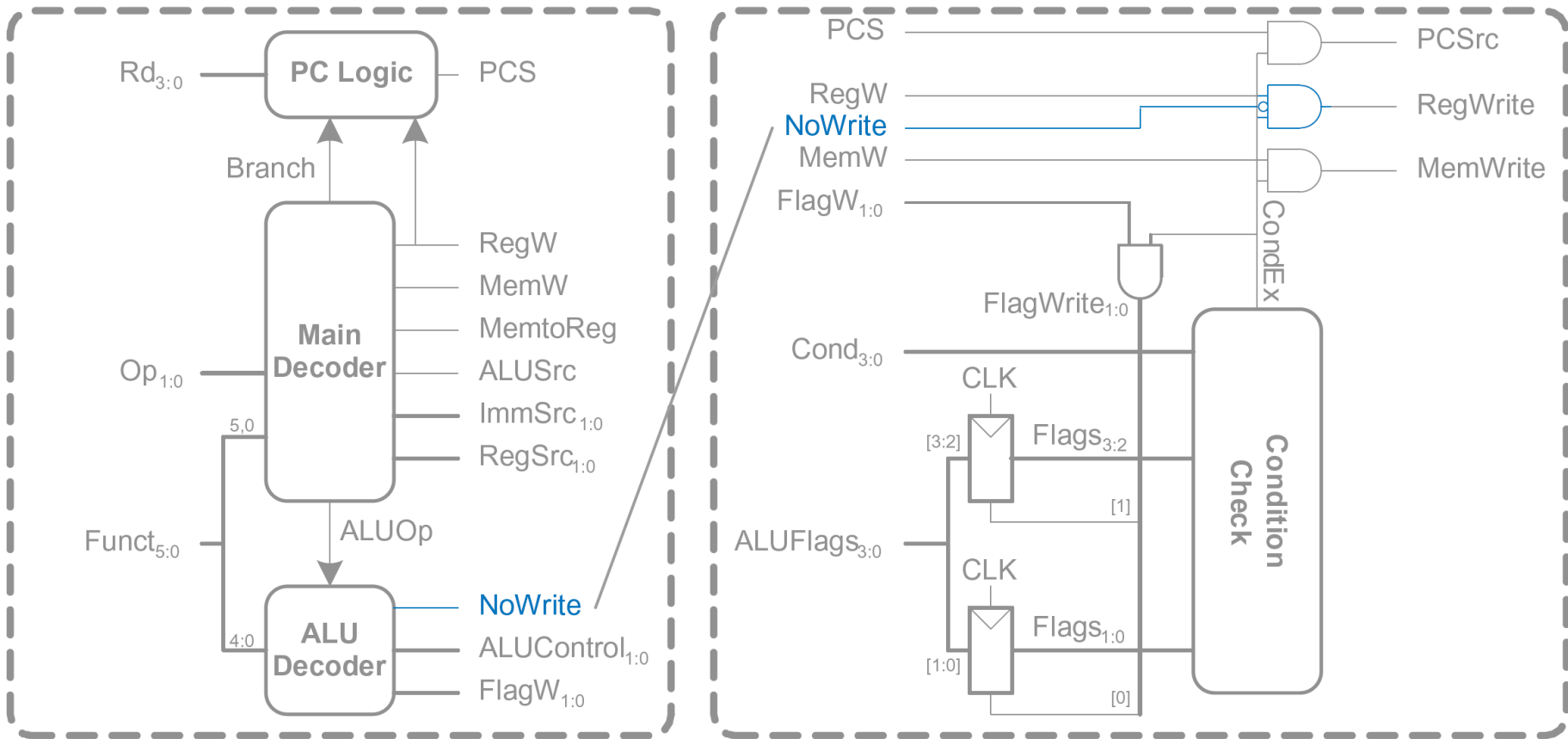


Extended Functionality: CMP

ALUOp	Funct _{4:1} (cmd)	Funct ₀ (S)	Type	ALUControl _{1:0}	FlagW _{1:0}	NoWrite
0	X	X	Not DP	00	00	0
1	0100	0	ADD	00	00	0
		1			11	0
	0010	0	SUB	01	00	0
		1			11	0
	0000	0	AND	10	00	0
		1			10	0
	1100	0	ORR	11	00	0
		1			10	0
1010	1	1	CMP	01	11	1



Extended Functionality: Shifted Register

 


ADD R7, R2, R12, LSR #5

31:28	27:26	25	24:21	20	19:16	15:12	11:7	6:5	4	3:0	
14	0	0	4	0	2	7	5	0	1	12	
cond		op		I		cmd		S		rn	
		rd		shamt5		sh				rm	



Extended Functionality: Shifted Register

 

No change to controller



Review: Processor Performance


Program Execution Time

$$= (\#instructions)(cycles/instruction)(seconds/cycle)$$

$$= \# \text{ instructions} \times \text{CPI} \times T_C$$



Single-Cycle Performance

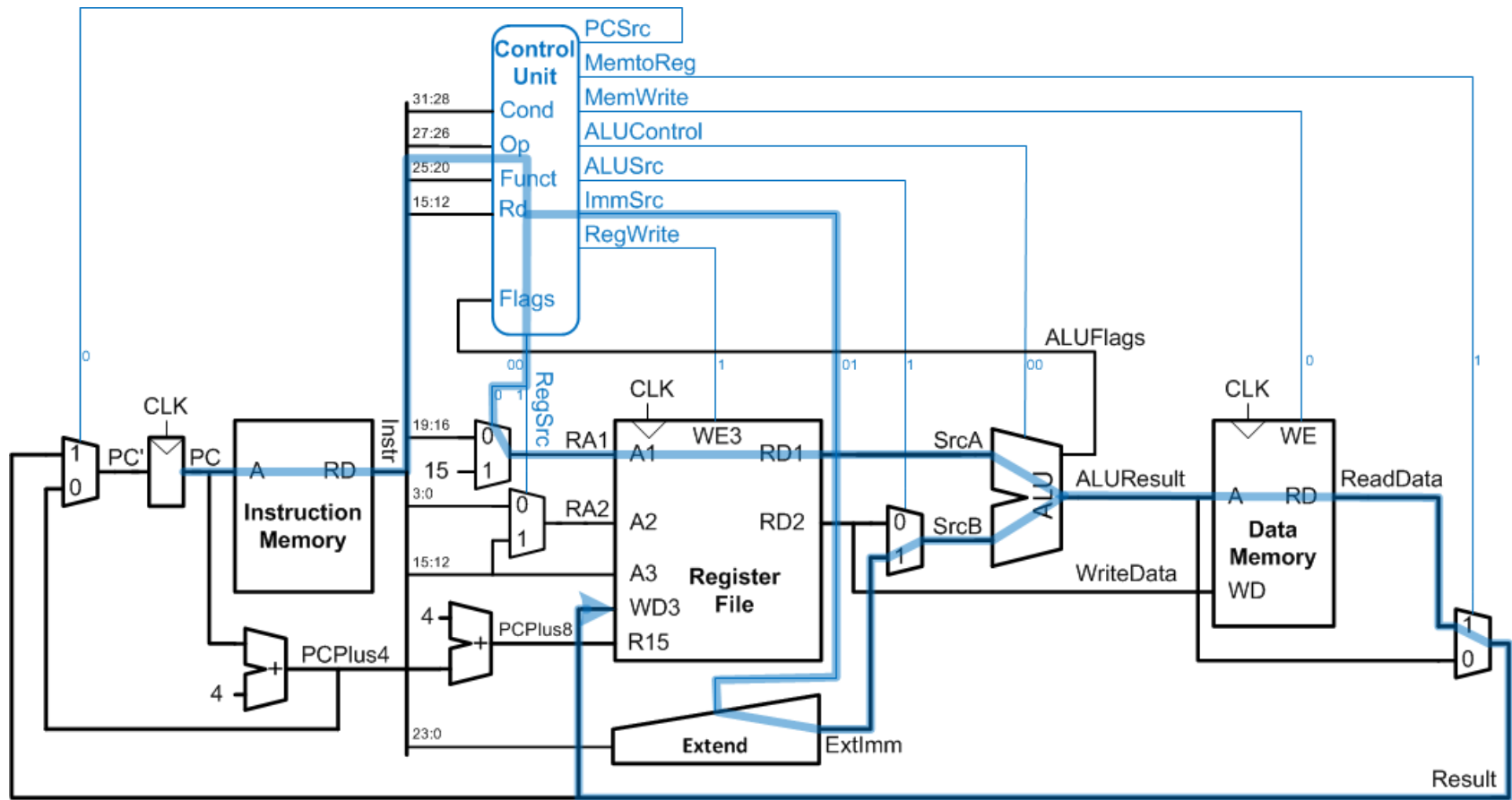

T_c limited by critical path (LDR)



Single-Cycle Performance

- **Single-cycle critical path:**

$$T_{c1} = t_{pcq_PC} + t_{mem} + t_{dec} + \max[t_{mux} + t_{RFread}, t_{sext} + t_{mux}] + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$$

- **Typically, limiting paths are:**

- memory, ALU, register file

- $T_{c1} = t_{pcq_PC} + 2t_{mem} + t_{dec} + t_{RFread} + t_{ALU} + 2t_{mux} + t_{RFsetup}$



Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	25
ALU	t_{ALU}	120
Decoder	t_{dec}	70
Memory read	t_{mem}	200
Register file read	t_{RFread}	100
Register file setup	$t_{RFsetup}$	60

$$T_{cl} = ?$$



Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	25
ALU	t_{ALU}	120
Decoder	t_{dec}	70
Memory read	t_{mem}	200
Register file read	t_{RFread}	100
Register file setup	$t_{RFsetup}$	60

$$\begin{aligned}T_{cl} &= t_{pcq_PC} + 2t_{mem} + t_{dec} + t_{RFread} + t_{ALU} + 2t_{mux} + t_{RFsetup} \\ &= [50 + 2(200) + 70 + 100 + 120 + 2(25) + 60] \text{ ps} \\ &= \mathbf{840 \text{ ps}}\end{aligned}$$



Single-Cycle Performance Example

Program with 100 billion instructions:

$$\begin{aligned}\text{Execution Time} &= \# \text{ instructions} \times \text{CPI} \times T_C \\ &= (100 \times 10^9)(1)(840 \times 10^{-12} \text{ s}) \\ &= \mathbf{84 \text{ seconds}}\end{aligned}$$



Multicycle ARM Processor

- **Single-cycle:**
 - + simple
 - cycle time limited by longest instruction (LDR)
 - separate memories for instruction and data
 - 3 adders/ALUs
- **Multicycle processor addresses these issues by breaking instruction into shorter steps**
 - shorter instructions take fewer steps
 - can re-use hardware
 - cycle time is faster



Multicycle ARM Processor

- **Single-cycle:**
 - + simple
 - cycle time limited by longest instruction (LDR)
 - separate memories for instruction and data
 - 3 adders/ALUs
- **Multicycle:**
 - + higher clock speed
 - + simpler instructions run faster
 - + reuse expensive hardware on multiple cycles
 - sequencing overhead paid many times



Multicycle ARM Processor

- **Single-cycle:**

- + simple
- cycle time limited by longest instruction (LDR)
- separate memories for instruction and data
- 3 adders/ALUs

- **Multicycle:**

- + higher clock speed
- + simpler instructions run faster
- + reuse expensive hardware on multiple cycles
- sequencing overhead paid many times


**Same design steps
as single-cycle:**

- **first datapath**
- **then control**





Multicycle State Elements

 Replace Instruction and Data memories with a single unified memory – more realistic





Multicycle Datapath: Instruction Fetch

STEP 1: Fetch instruction

 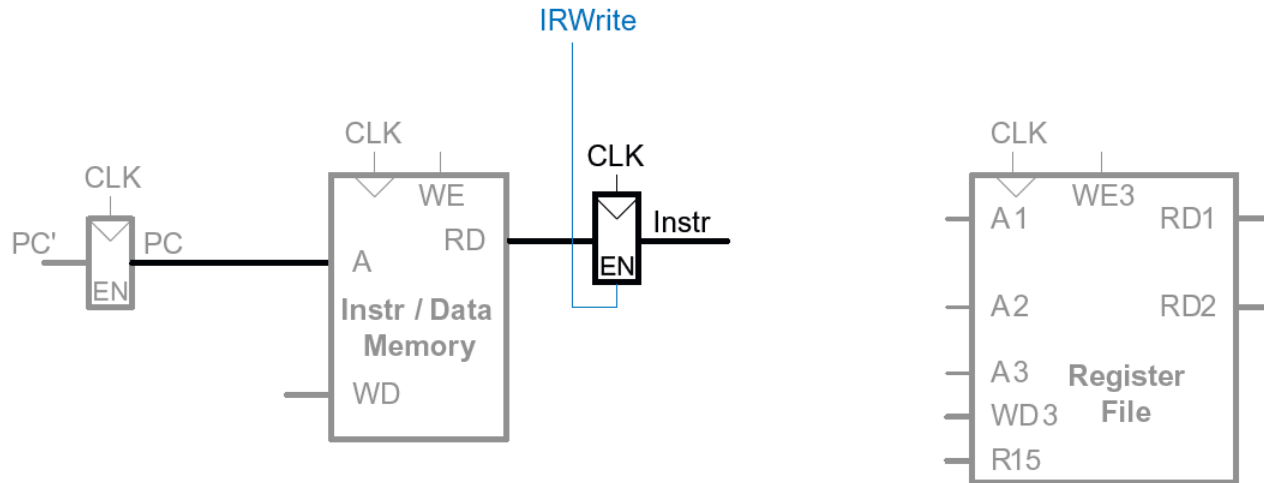


Multicycle Datapath: LDR Register Read

STEP 2: Read source operands from RF

 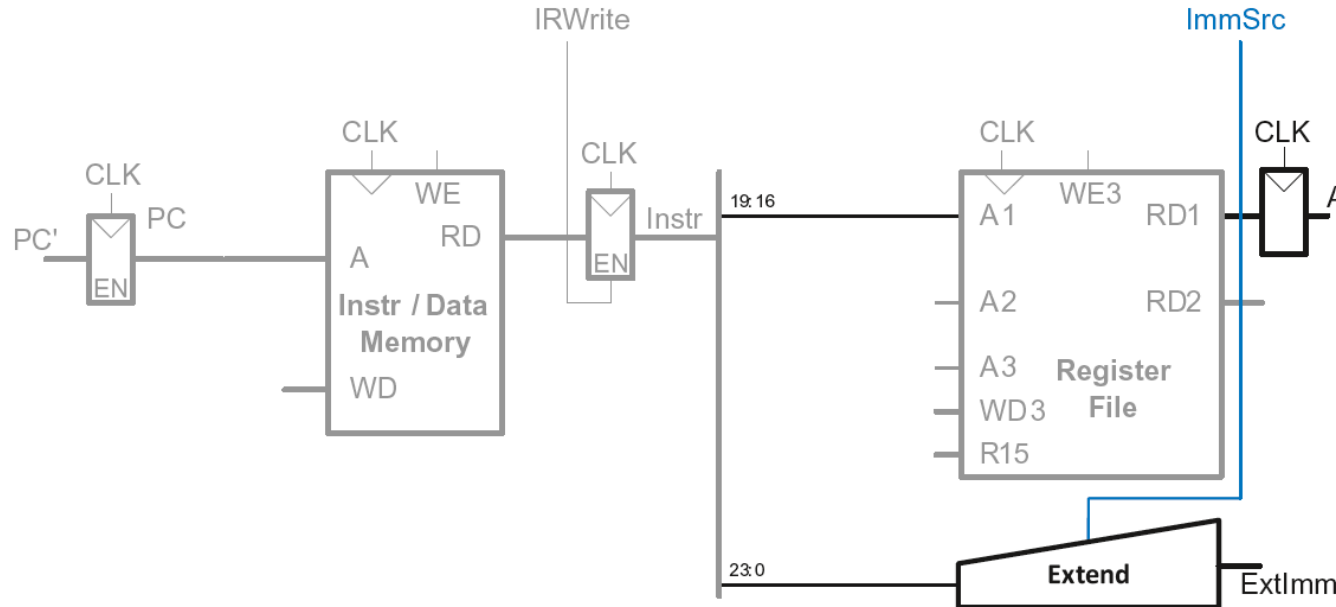



Multicycle Datapath: LDR Address

STEP 3: Compute the memory address

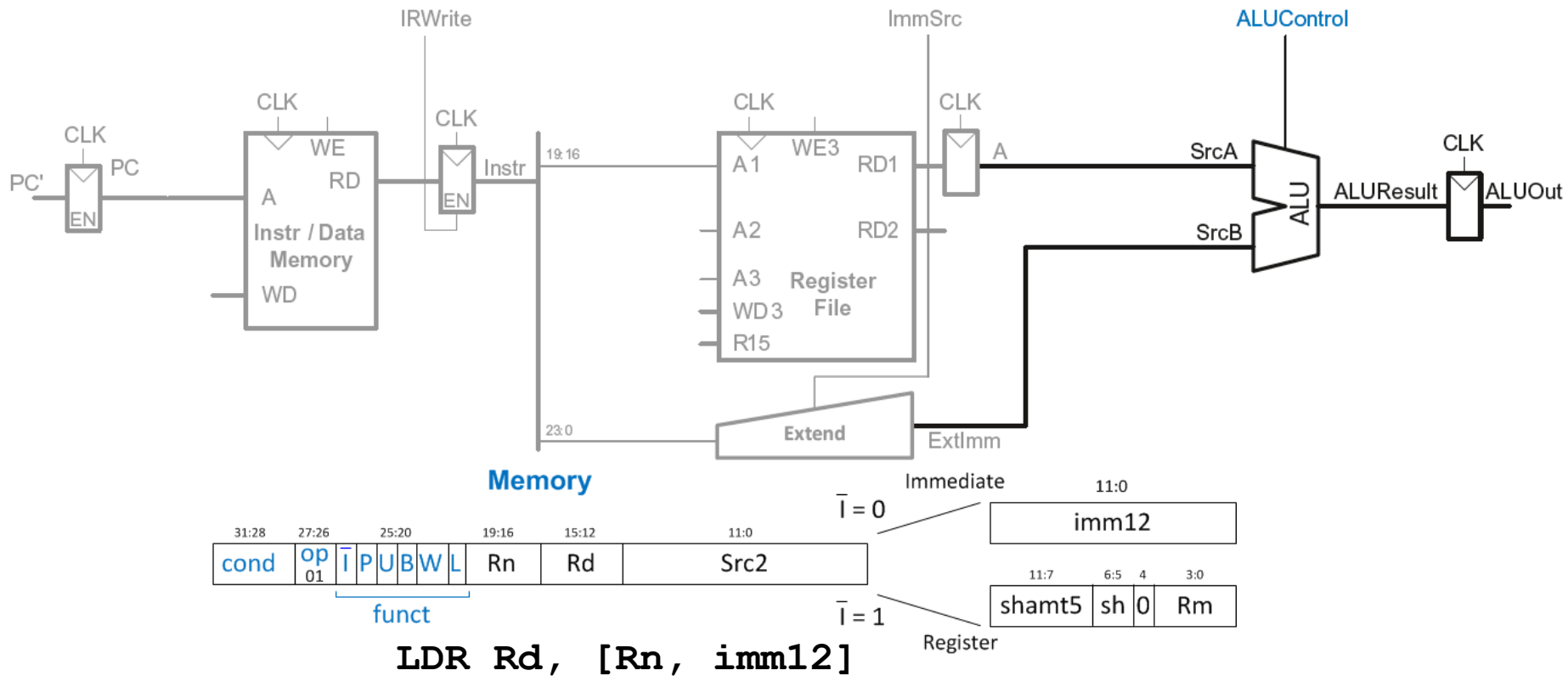



Multicycle Datapath: LDR Memory Read

STEP 4: Read data from memory

 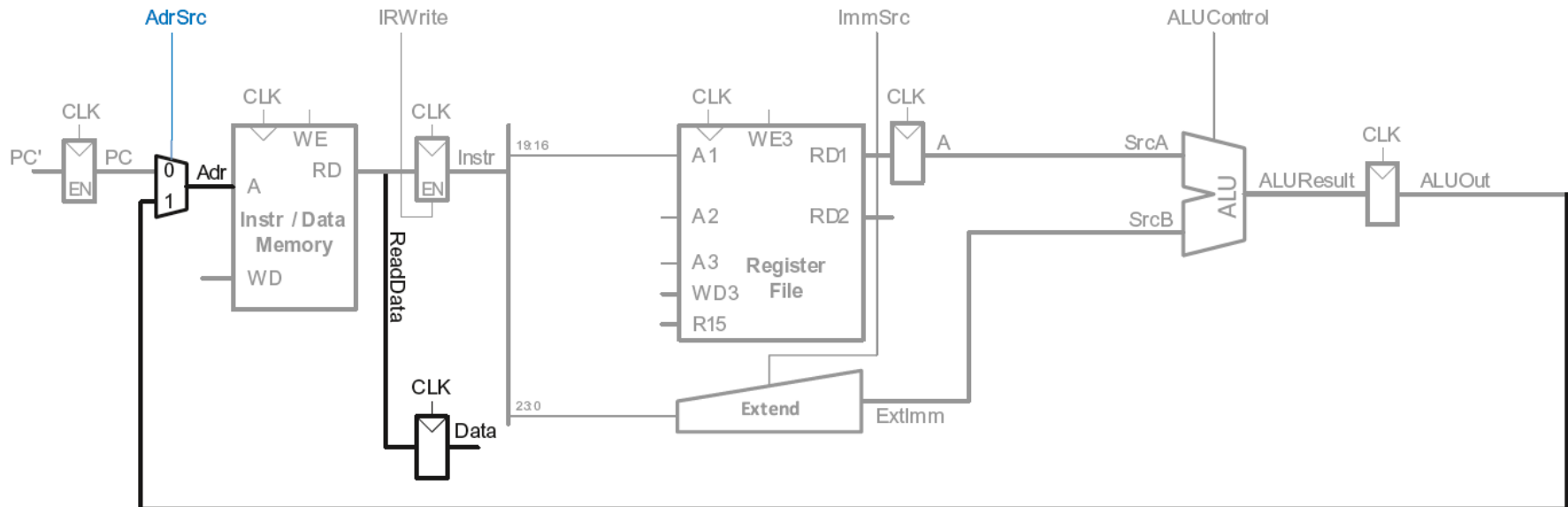

Multicycle Datapath: LDR Write Register

STEP 5: Write data back to register file

 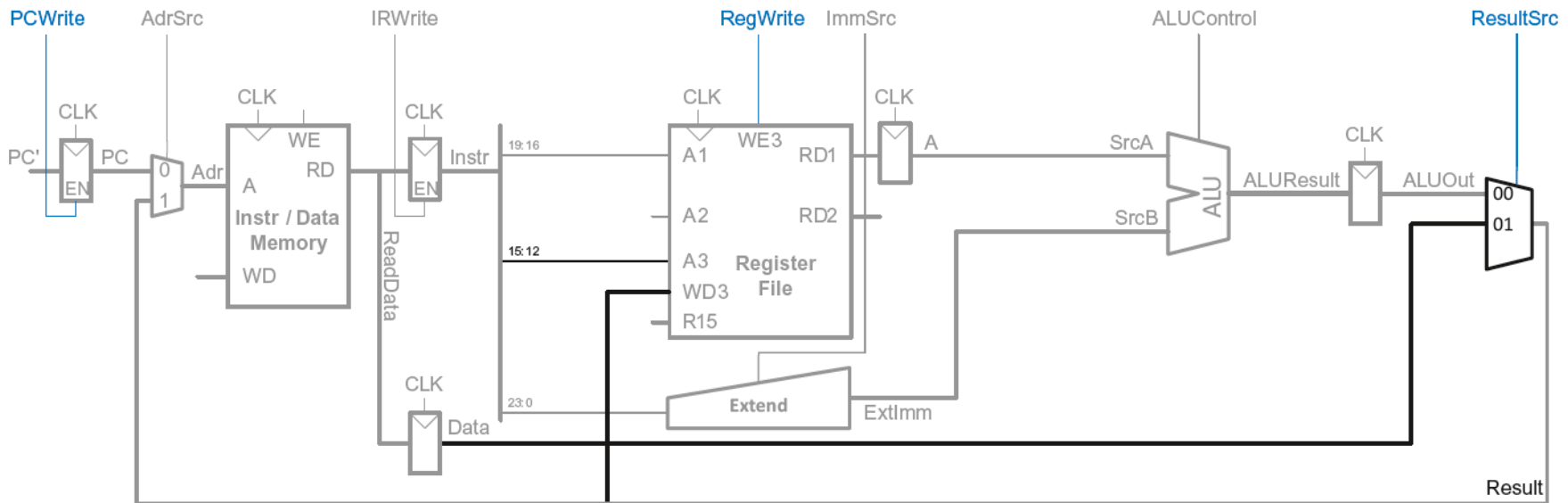


LDR Rd, [Rn, imm12]




Multicycle Datapath: Increment PC

STEP 6: Increment PC

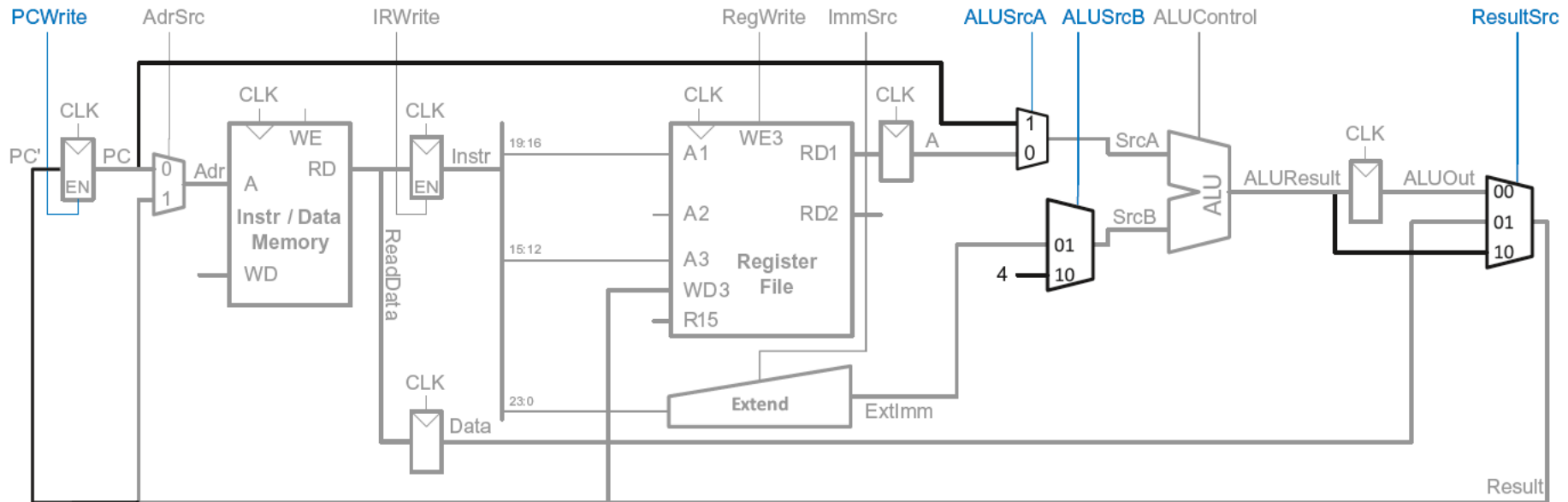

Multicycle Datapath: Access to PC


PC can be read/written by instruction

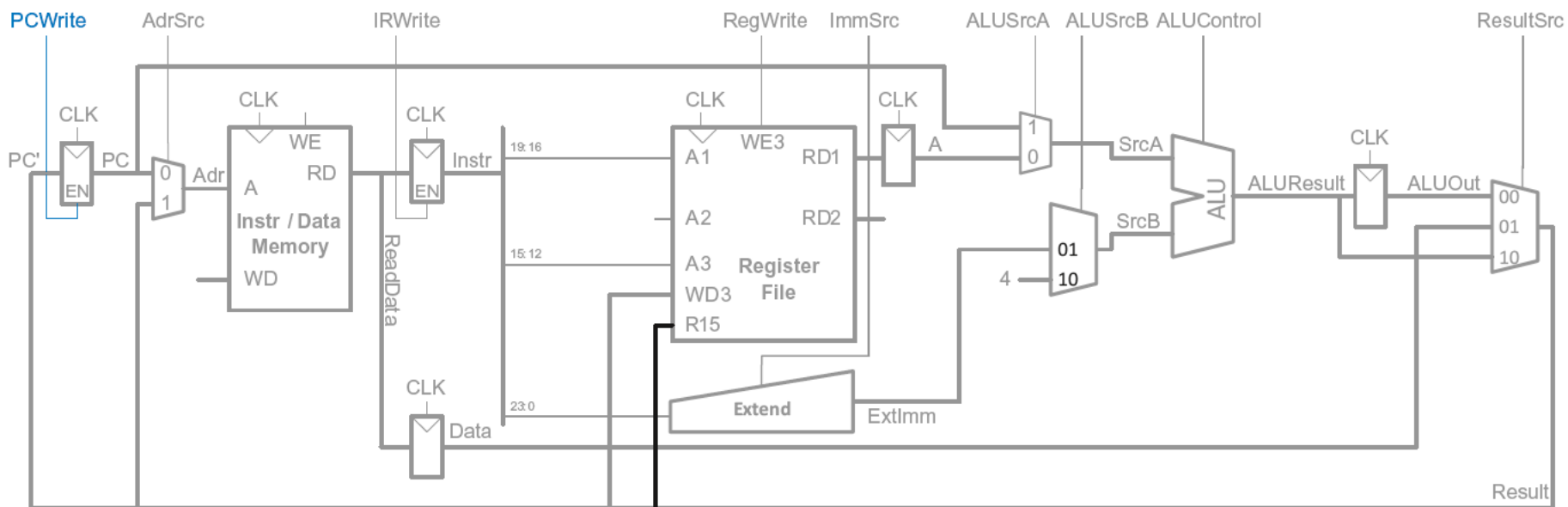

Multicycle Datapath: Access to PC

PC can be read/written by instruction

 - **Read:** R15 (PC+8) available in Register File



Multicycle Datapath: Read to PC (R15)


Example: ADD R1, **R15**, R2



Multicycle Datapath: Read to PC (R15)

 Example: ADD R1, R15, R2

- R15 needs to be read as PC+8 from Register File (RF) in 2nd step
- So (also in 2nd step) PC + 8 is produced by ALU and routed to R15 input of RF



Multicycle Datapath: Read to PC (R15)

Example: `ADD R1, R15, R2`


- R15 needs to be read as PC+8 from Register File (RF) in 2nd step
- So (also in 2nd step) PC + 8 is produced by ALU and routed to R15 input of RF
 - $SrcA = PC$ (which was already updated in step 1 to PC+4)
 - $SrcB = 4$
 - $ALUResult = PC + 8$
- ALUResult is fed to R15 input port of RF in 2nd step (which is then routed to RD1 output of RF)



Multicycle Datapath: Read to PC (R15)

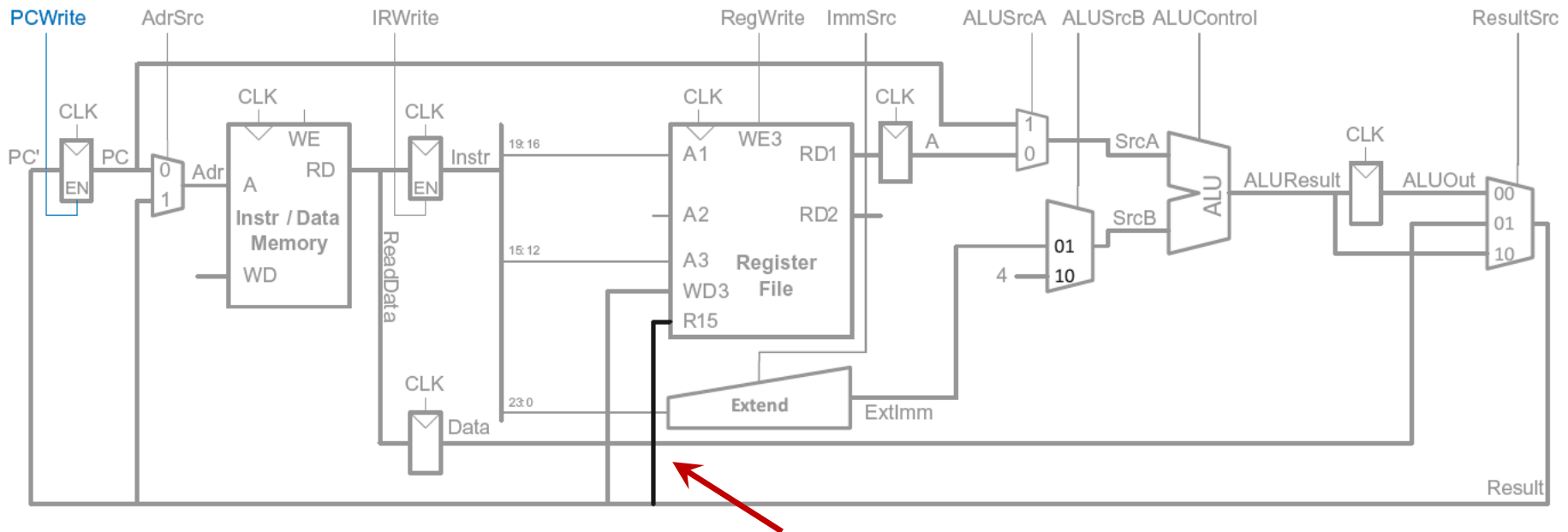Example: ADD R1, R15, R2


- R15 needs to be read as PC+8 from Register File (RF) in 2nd step
- So (also in 2nd step) PC + 8 is produced by ALU and routed to R15 input of RF



Multicycle Datapath: Access to PC

PC can be read/written by instruction

 - **Read:** R15 (PC+8) available in Register File
- **Write:** Be able to write result of instruction to PC



Multicycle Datapath: Write to PC (R15)

Example: SUB **R15**, R8, R3



Multicycle Datapath: Write to PC (R15)

Example: SUB **R15**, R8, R3


- Result of instruction needs to be written to the PC register
- ALUResult already routed to the PC register, just assert PCWrite



Multicycle Datapath: Write to PC (R15)

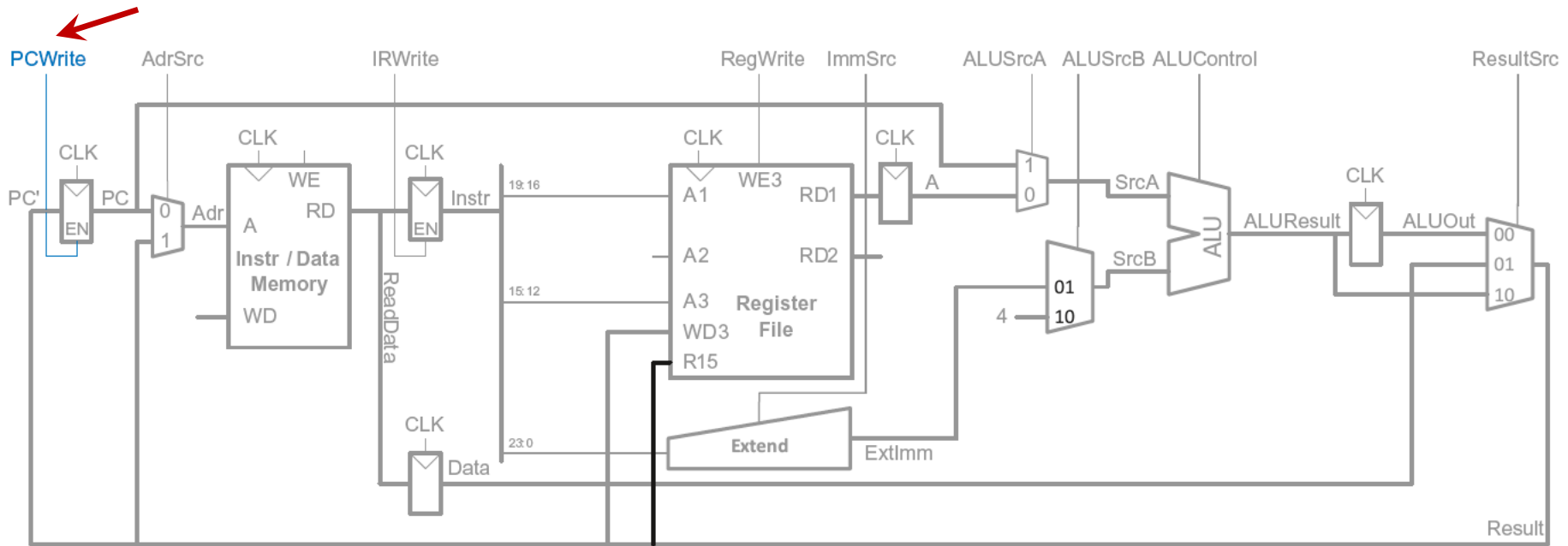
Example: SUB R15, R8, R3

- Result of instruction needs to be written to the PC register
- ALUResult already routed to the PC register, just assert PCWrite




Multicycle Datapath: STR

Write data in R_n to memory

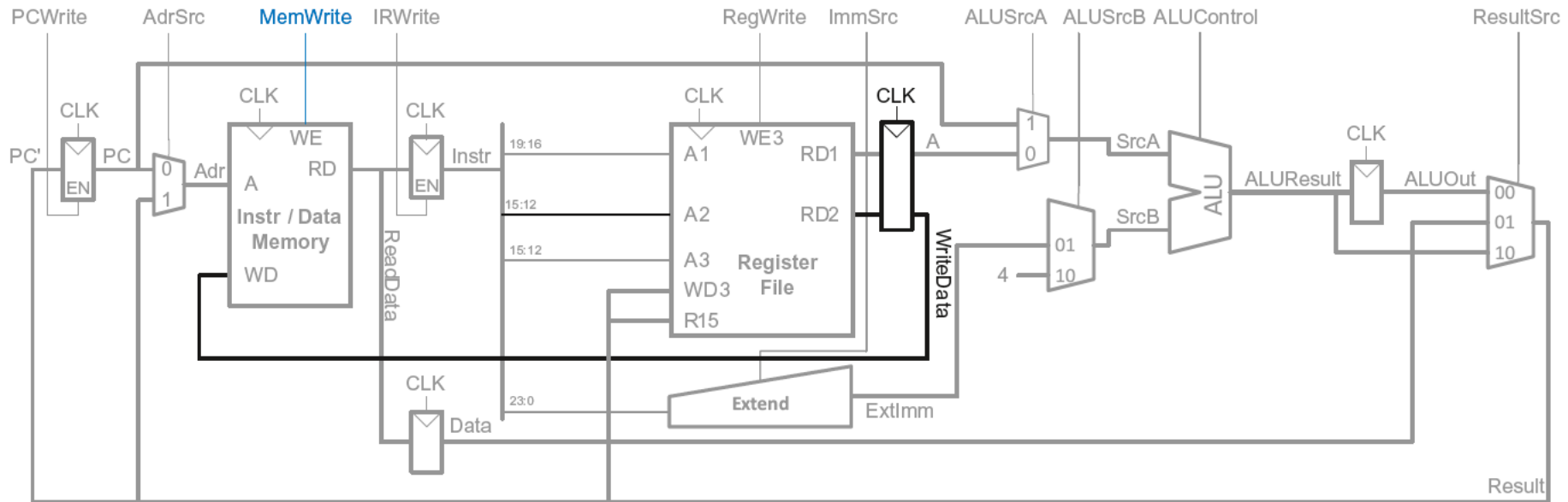


Multicycle Datapath: Data-processing

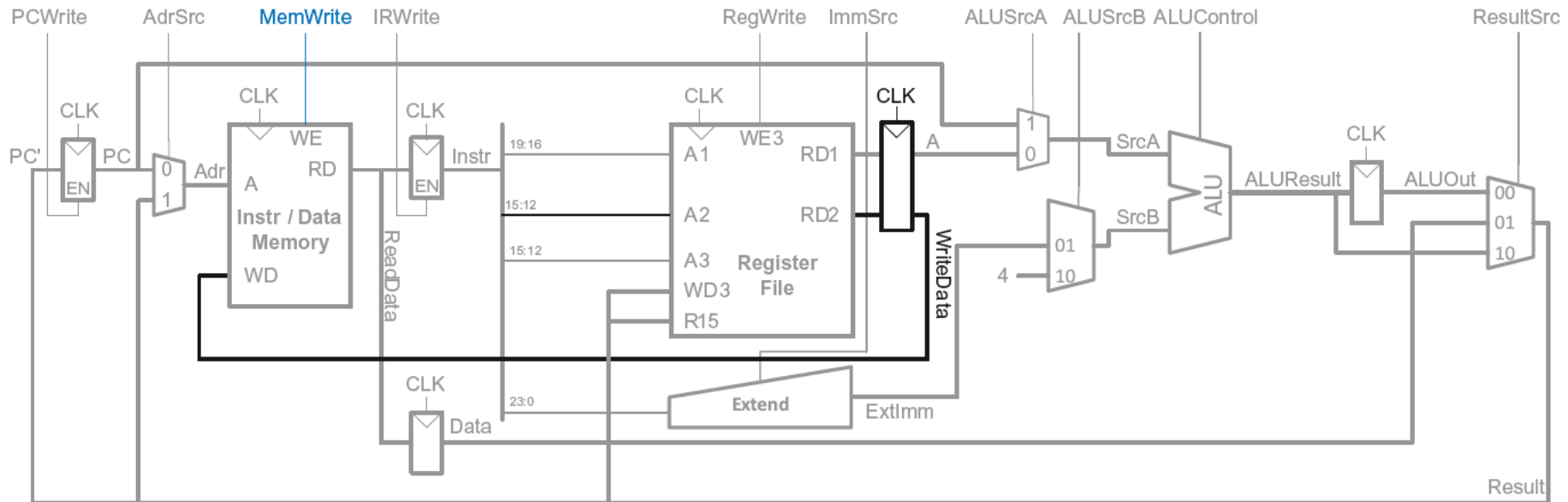With immediate addressing (i.e., an immediate *Src2*), no additional changes needed for datapath



Multicycle Datapath: Data-processing

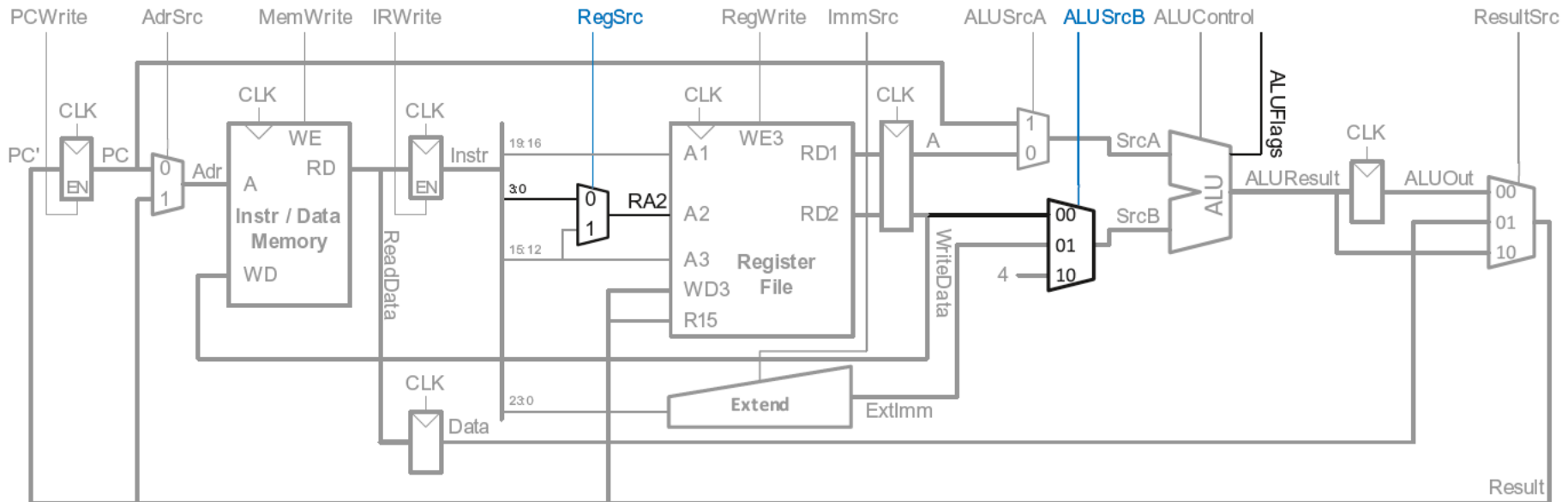With register addressing (register *Src2*):
Read from *Rn* and *Rm*




Multicycle Datapath: B


Calculate branch target address:

$$BTA = (ExtImm) + (PC+8)$$


$ExtImm = Imm24 \ll 2$ and sign-extended

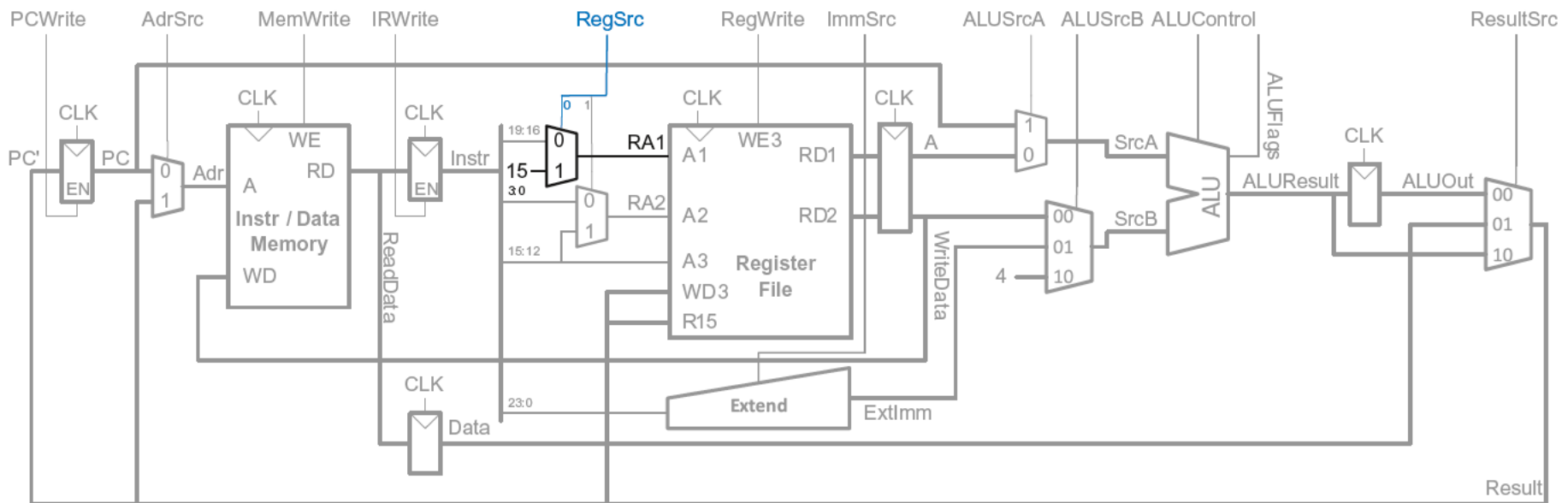

Multicycle ARM Processor

 


Multicycle Control

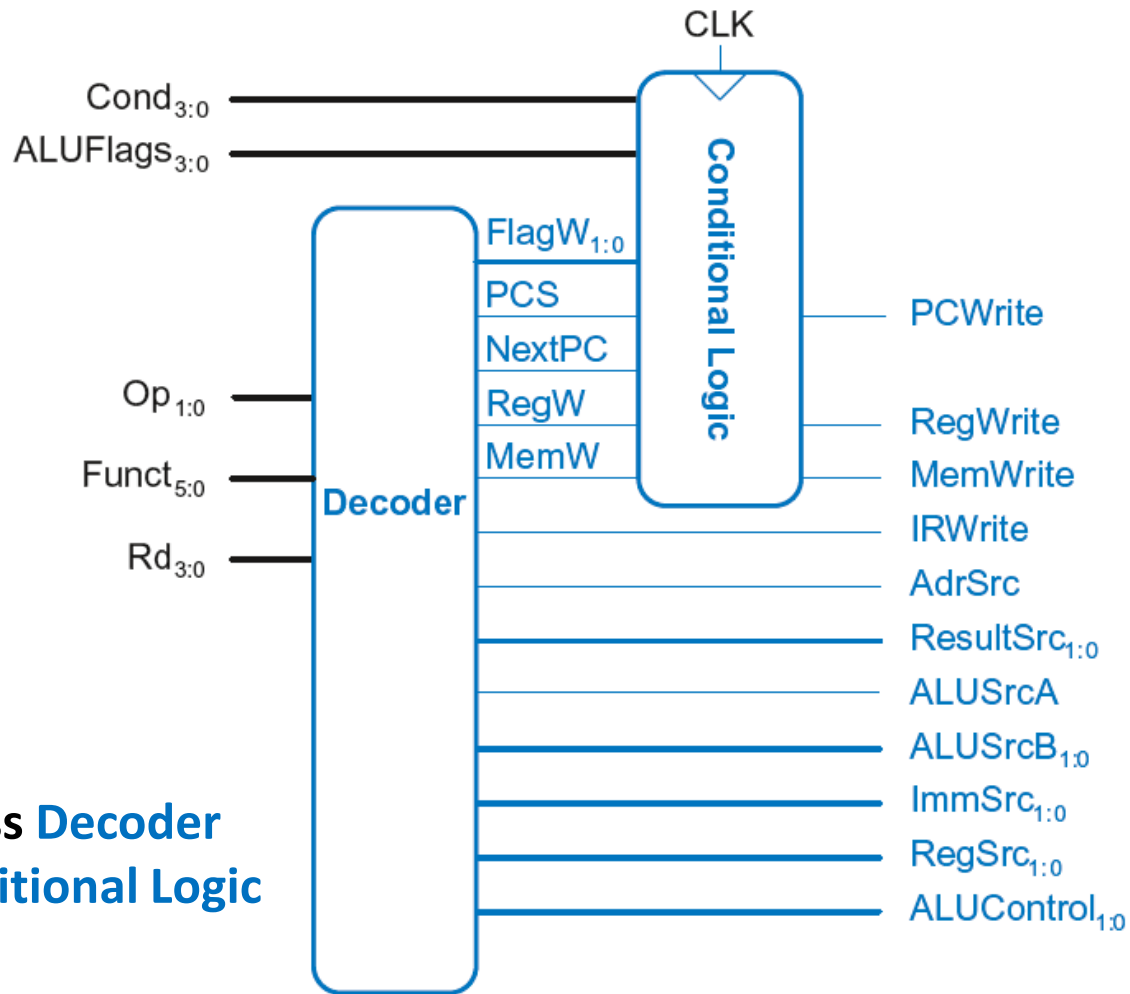


- First, discuss **Decoder**
- Then, **Conditional Logic**




Multicycle Control: Decoder

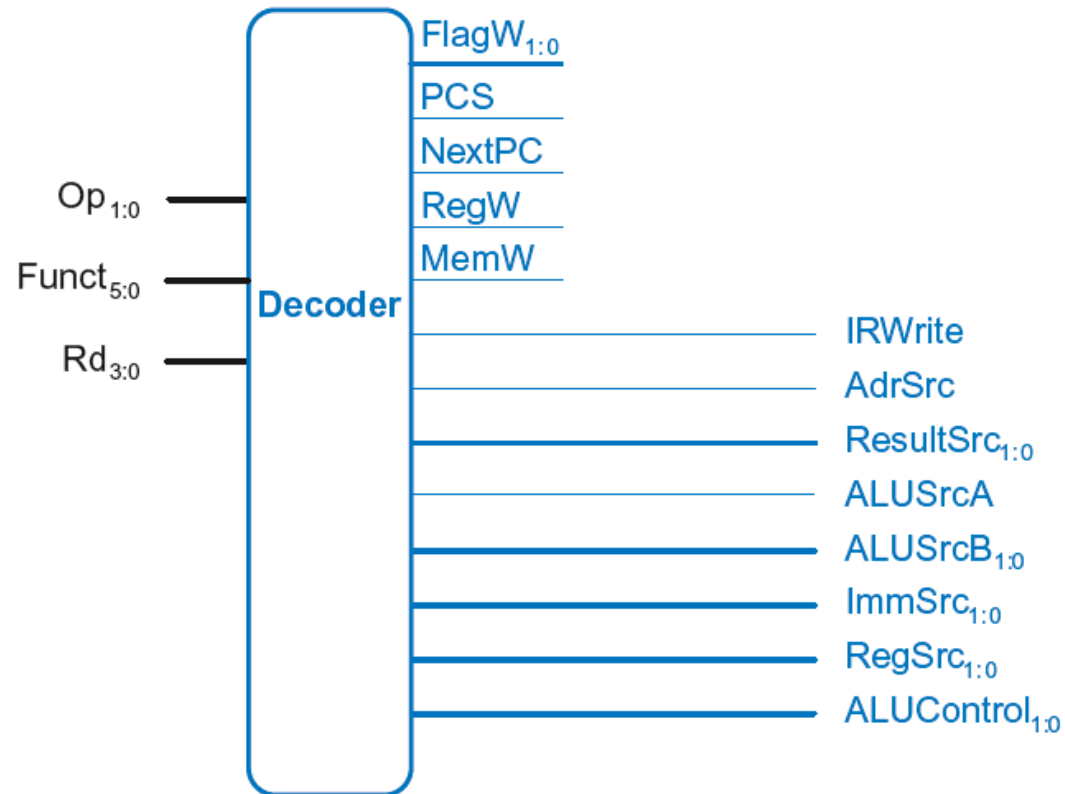

Multicycle Control: Decoder

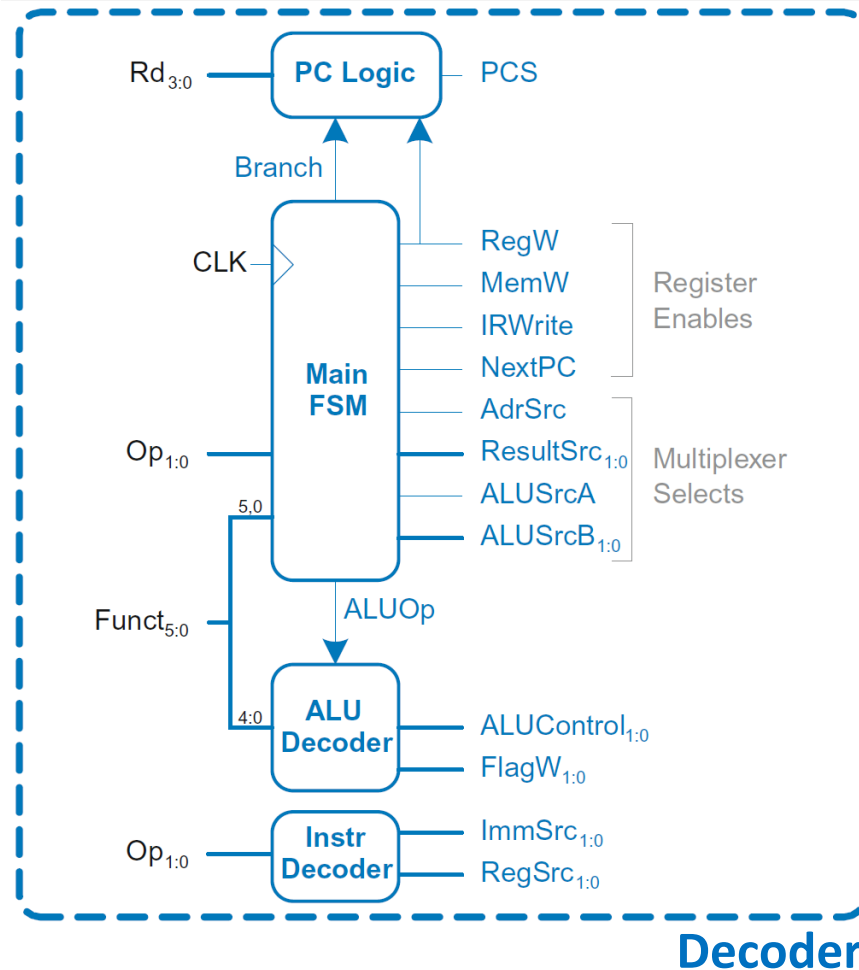


Multicycle Control: Decoder

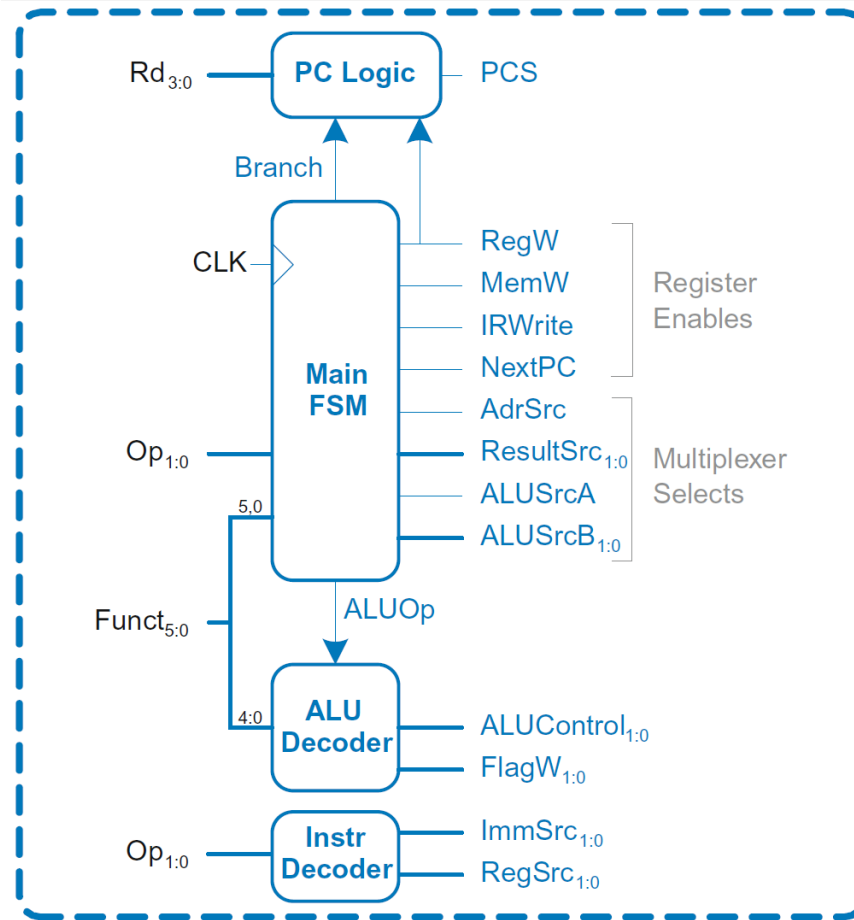

ALU Decoder and PC Logic same as single-cycle



Multicycle Control: Instr Decoder

 

$$RegSrc_0 = (Op == 10_2)$$


$$RegSrc_1 = (Op == 01_2)$$

$$ImmSrc_{1:0} = Op$$


Instruction	Op	$Funct_5$	$Funct_0$	$RegSrc_0$	$RegSrc_1$	$ImmSrc_{1:0}$
LDR	01	X	1	0	X	01
STR	01	X	0	0	1	01
DP immediate	00	1	X	0	X	00
DP register	00	0	X	0	0	00
B	10	X	X	1	X	10




Multicycle ARM Processor

 


Multicycle Control: Main FSM

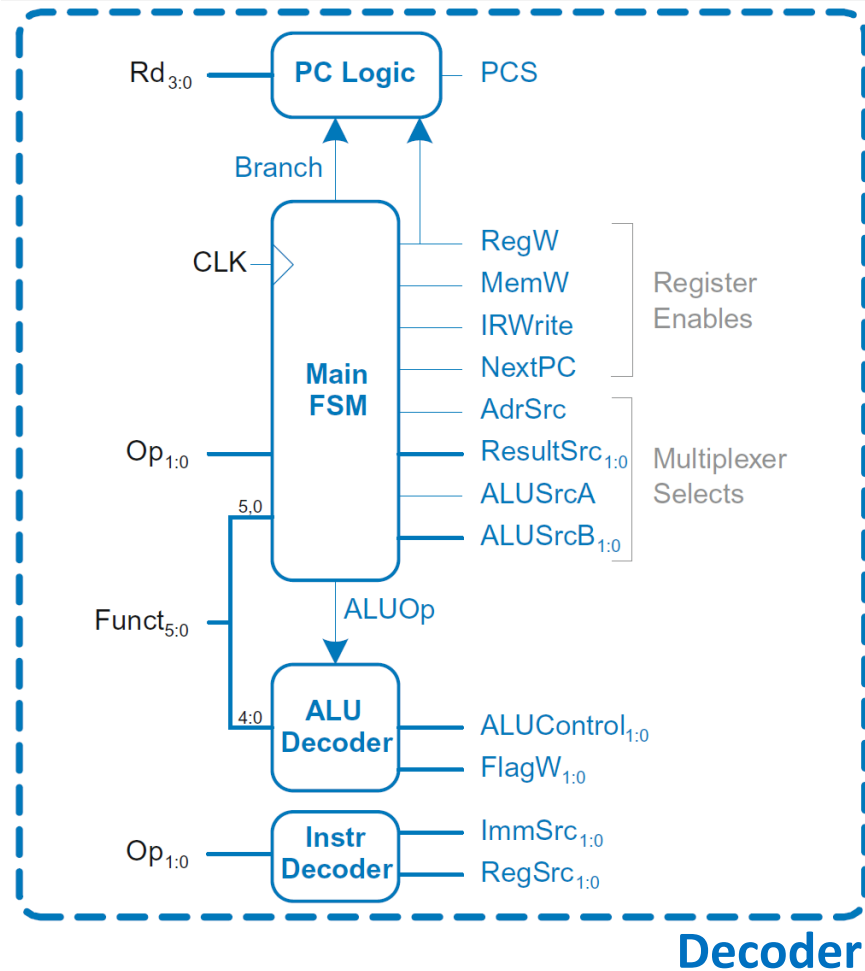



Main Controller FSM: Fetch

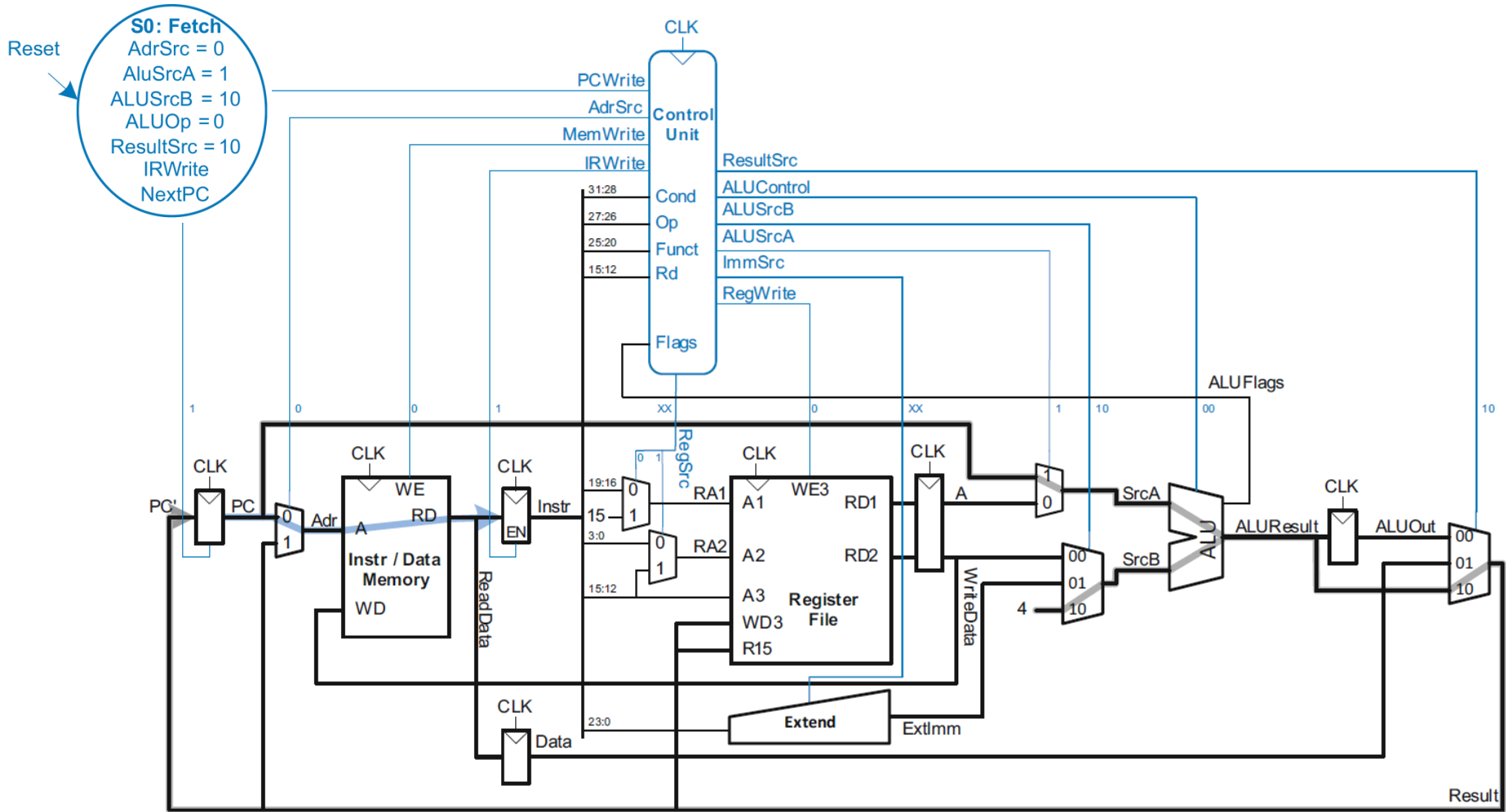


Main Controller FSM: Decode

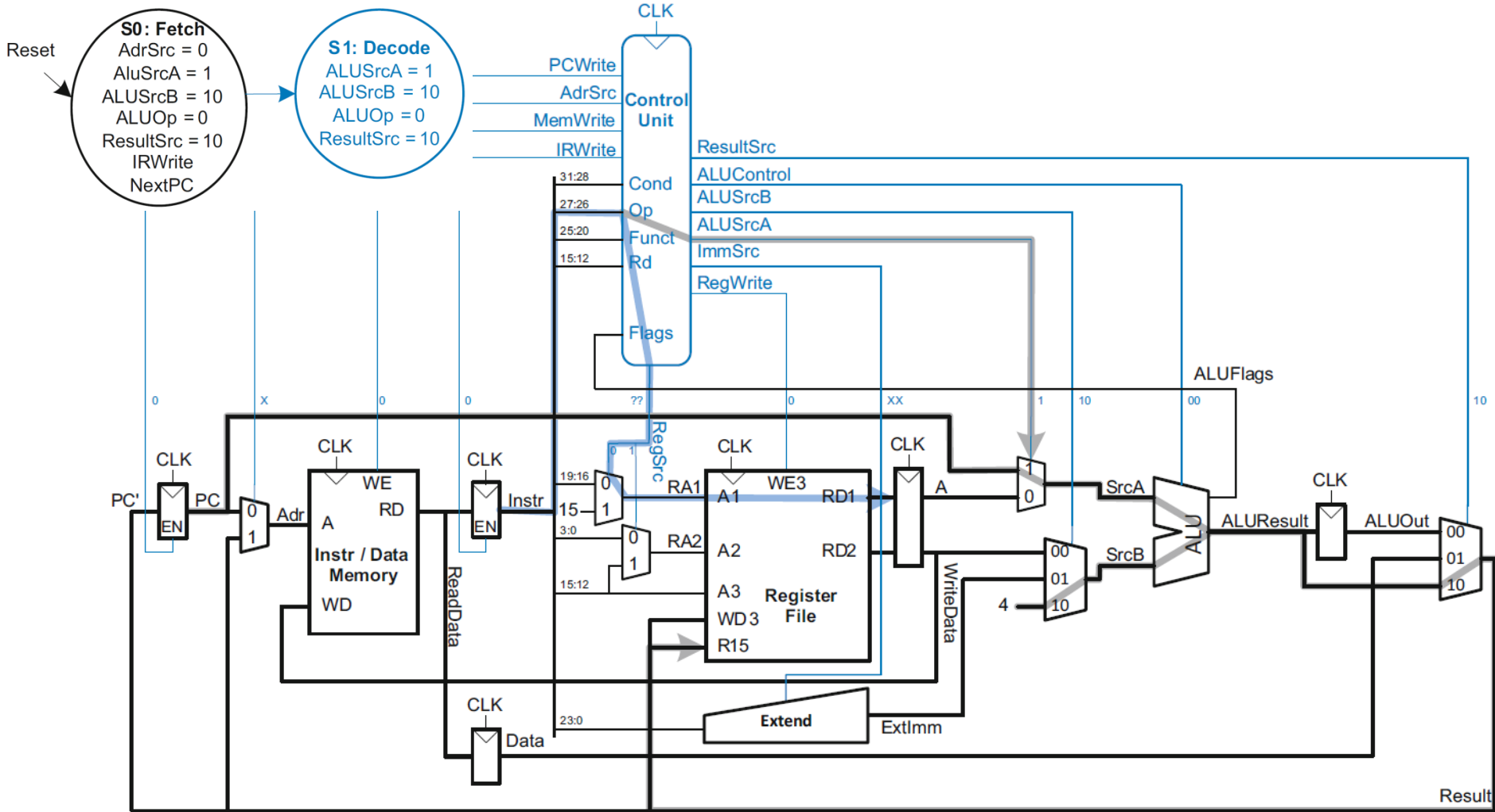


Main Controller FSM: Address

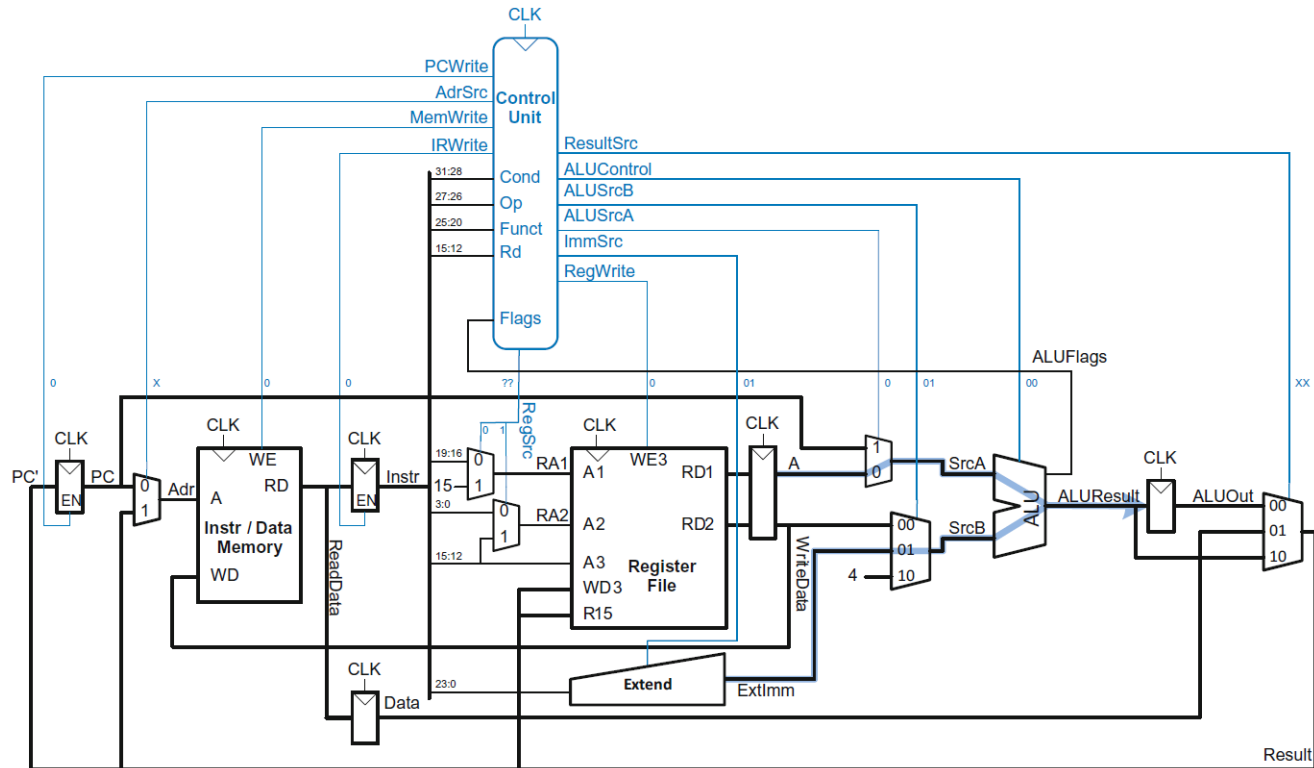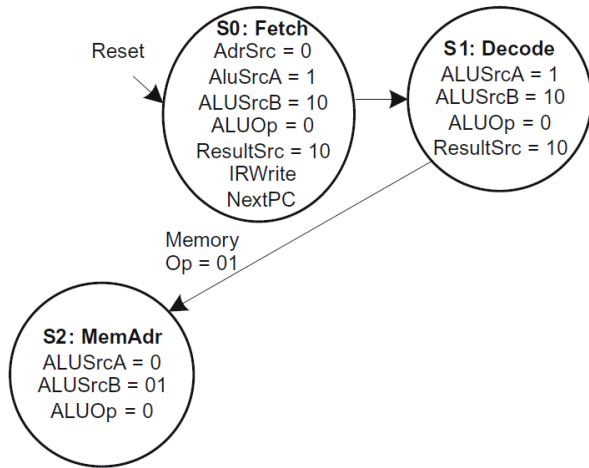


Main Controller FSM: Read Memory

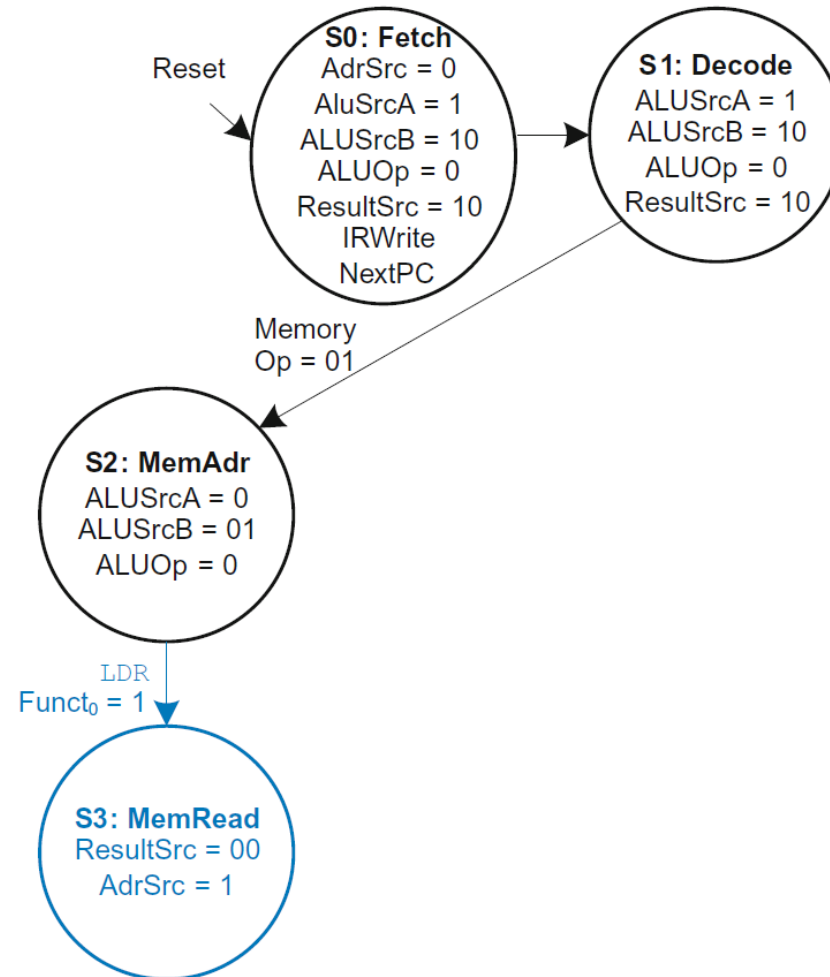


Multicycle ARM Processor

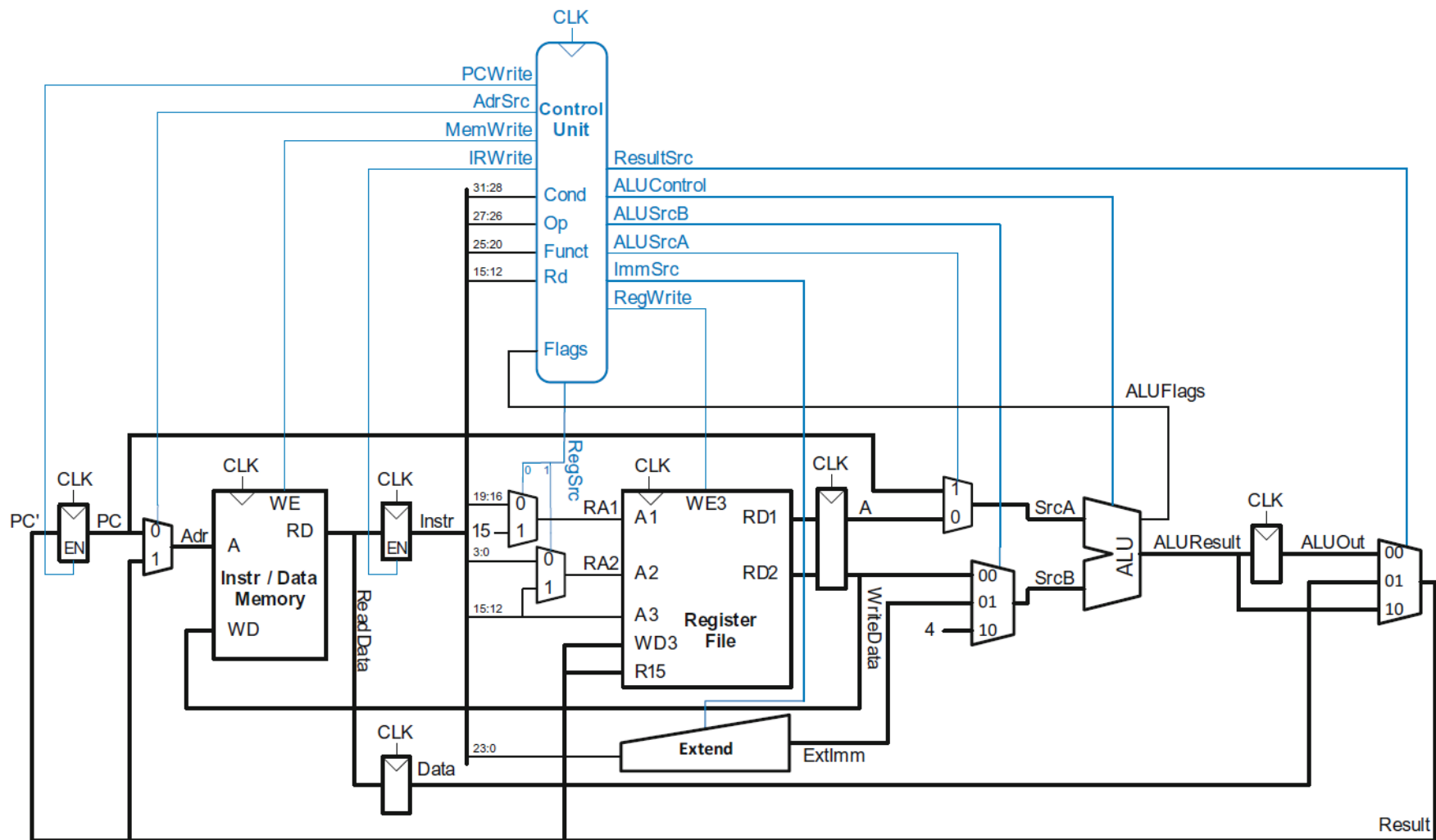


Main Controller FSM: LDR

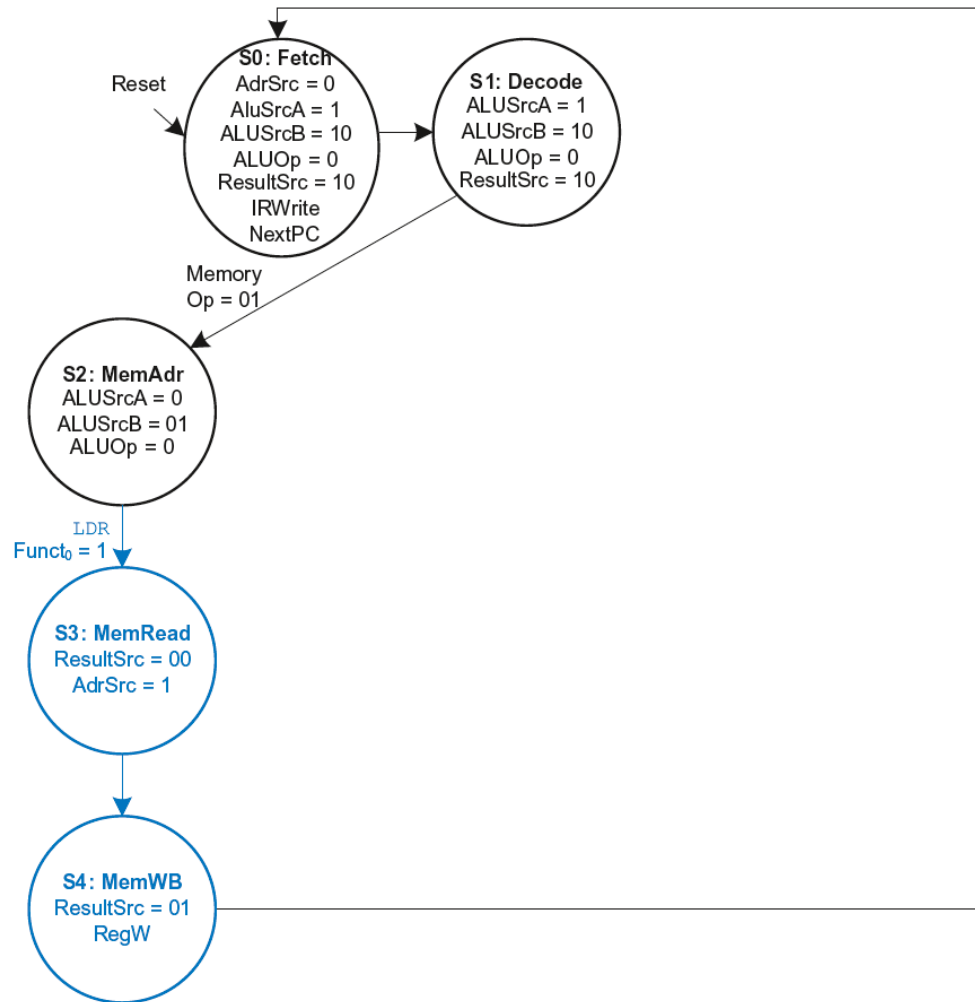


Main Controller FSM: STR

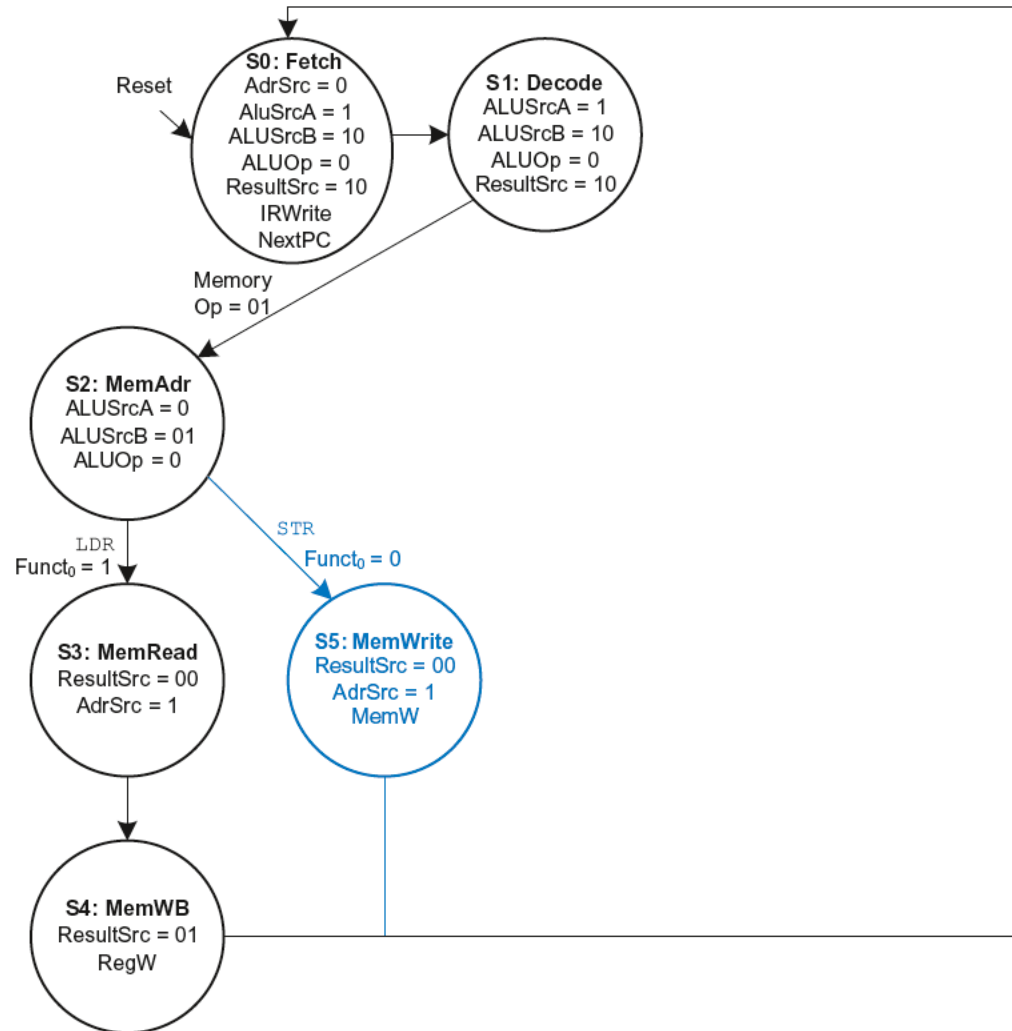

Main Controller FSM: Data-processing

 

Main Controller FSM: Data-processing

 

Multicycle Controller FSM

State

Fetch

Decode

MemAdr

MemRead

MemWB

MemWrite

ExecuteR

Executel

ALUWB

Branch

Datapath μ Op

Instr \leftarrow Mem[PC]; PC \leftarrow PC+4

ALUOut \leftarrow PC+4

ALUOut \leftarrow Rn + Imm

Data \leftarrow Mem[ALUOut]

Rd \leftarrow Data


Mem[ALUOut] \leftarrow Rd

ALUOut \leftarrow Rn op Rm


ALUOut \leftarrow Rn op Imm

Rd \leftarrow ALUOut

PC \leftarrow R15 + offset

 


Multicycle Control

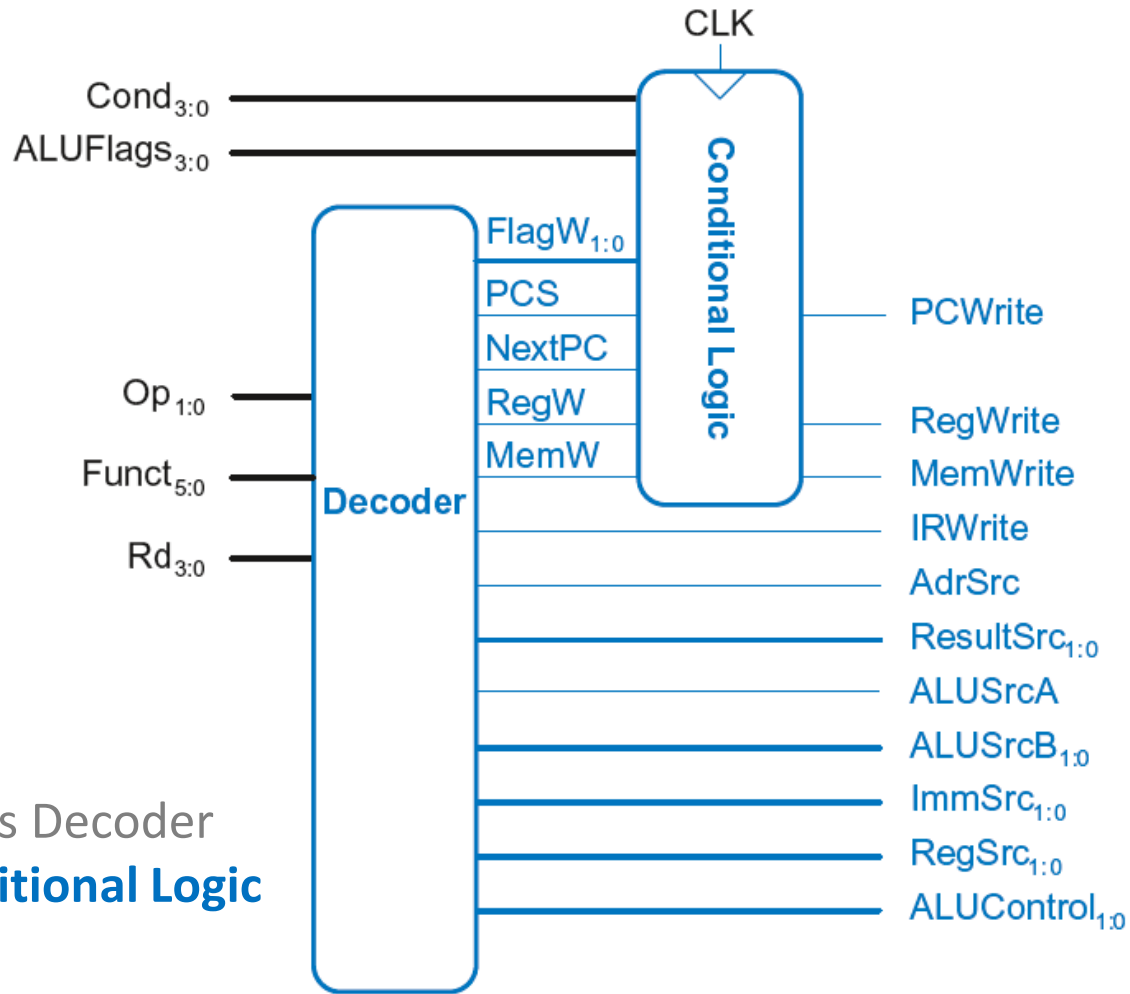


- First, discuss Decoder
- **Then, Conditional Logic**




Multicycle Control: Cond. Logic

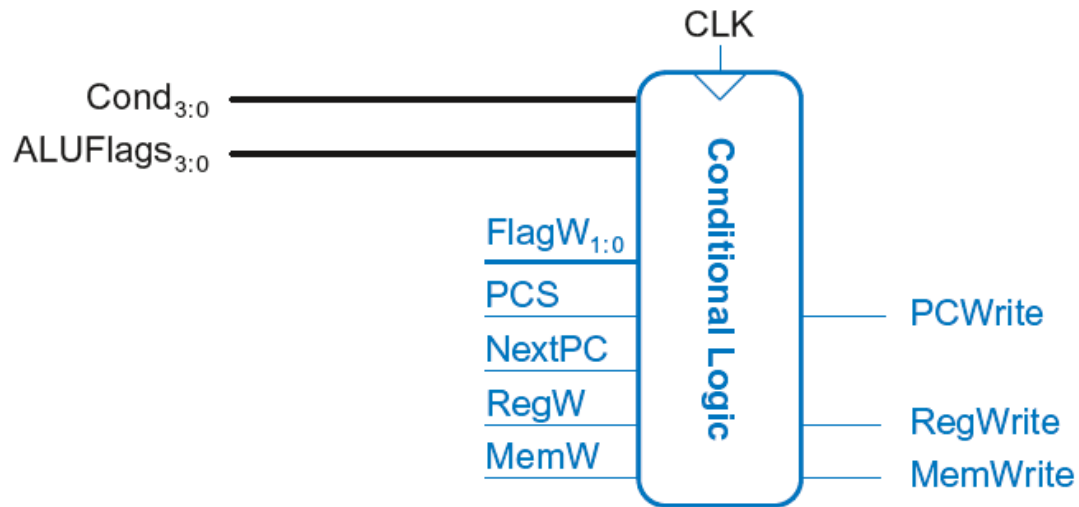

Single-Cycle Conditional Logic

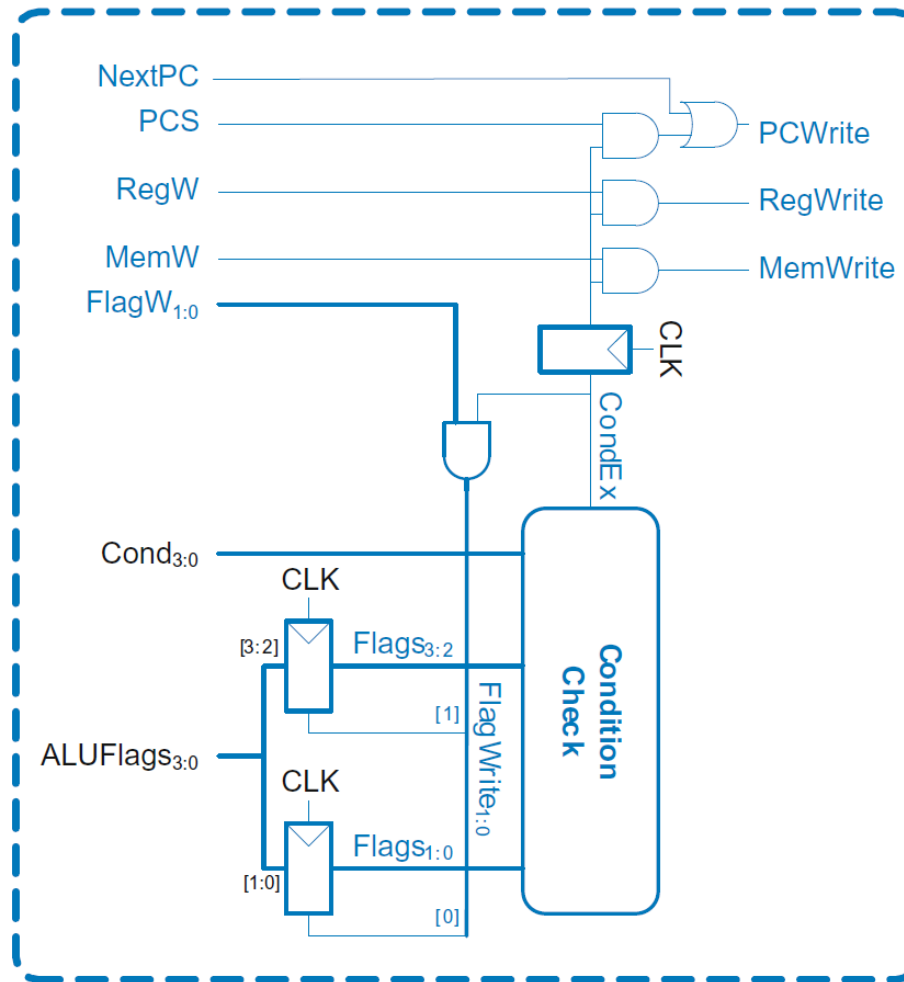

Multicycle Conditional Logic

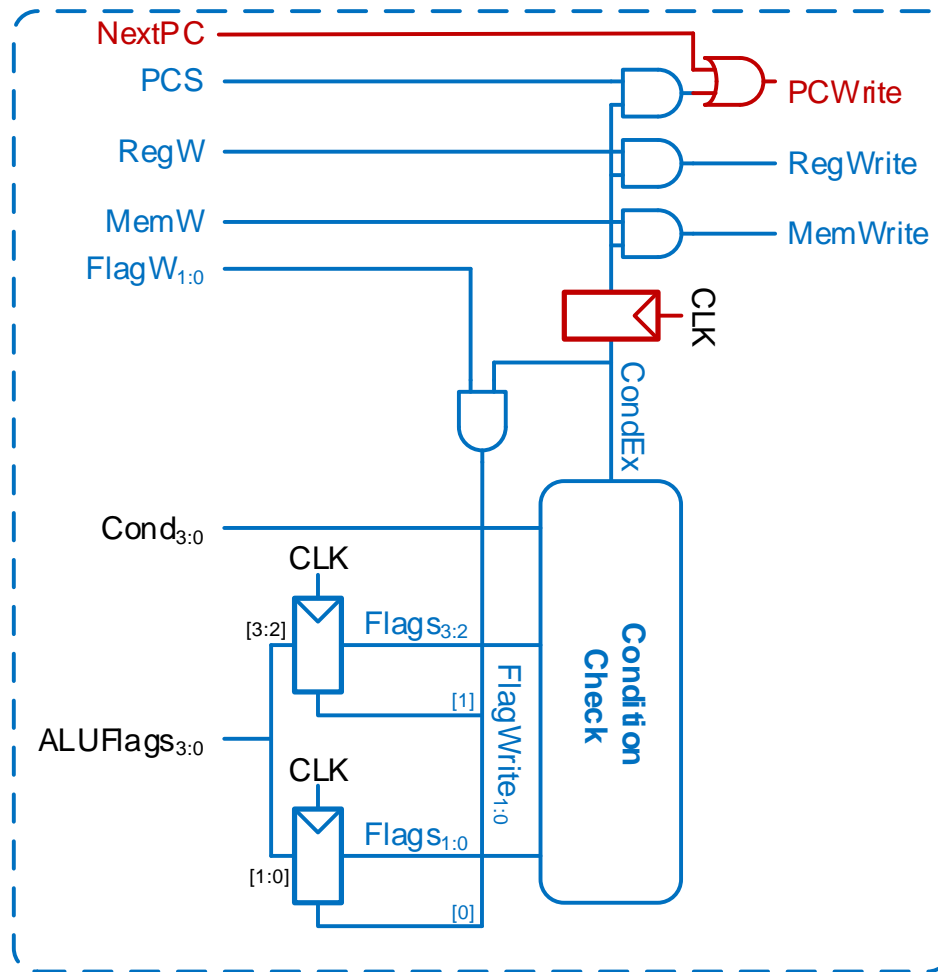

- **PCWrite** asserted in Fetch state
- **Executel/ExecuteR** state: **CondEx** asserts
ALUFlags generated
- **ALUWB** state: **Flags** updated
CondEx changes
PCWrite, **RegWrite**, and **MemWrite** don't see change till new instruction (Fetch state)



Multicycle Processor Performance

- Instructions take different number of cycles.



Multicycle Controller FSM

State

Fetch

Decode

MemAdr

MemRead

MemWB

MemWrite

ExecuteR

Executel

ALUWB

Branch

Datapath μ Op

Instr \leftarrow Mem[PC]; PC \leftarrow PC+4

ALUOut \leftarrow PC+4

ALUOut \leftarrow Rn + Imm

Data \leftarrow Mem[ALUOut]

Rd \leftarrow Data


Mem[ALUOut] \leftarrow Rd

ALUOut \leftarrow Rn op Rm

ALUOut \leftarrow Rn op Imm

Rd \leftarrow ALUOut

PC \leftarrow R15 + offset

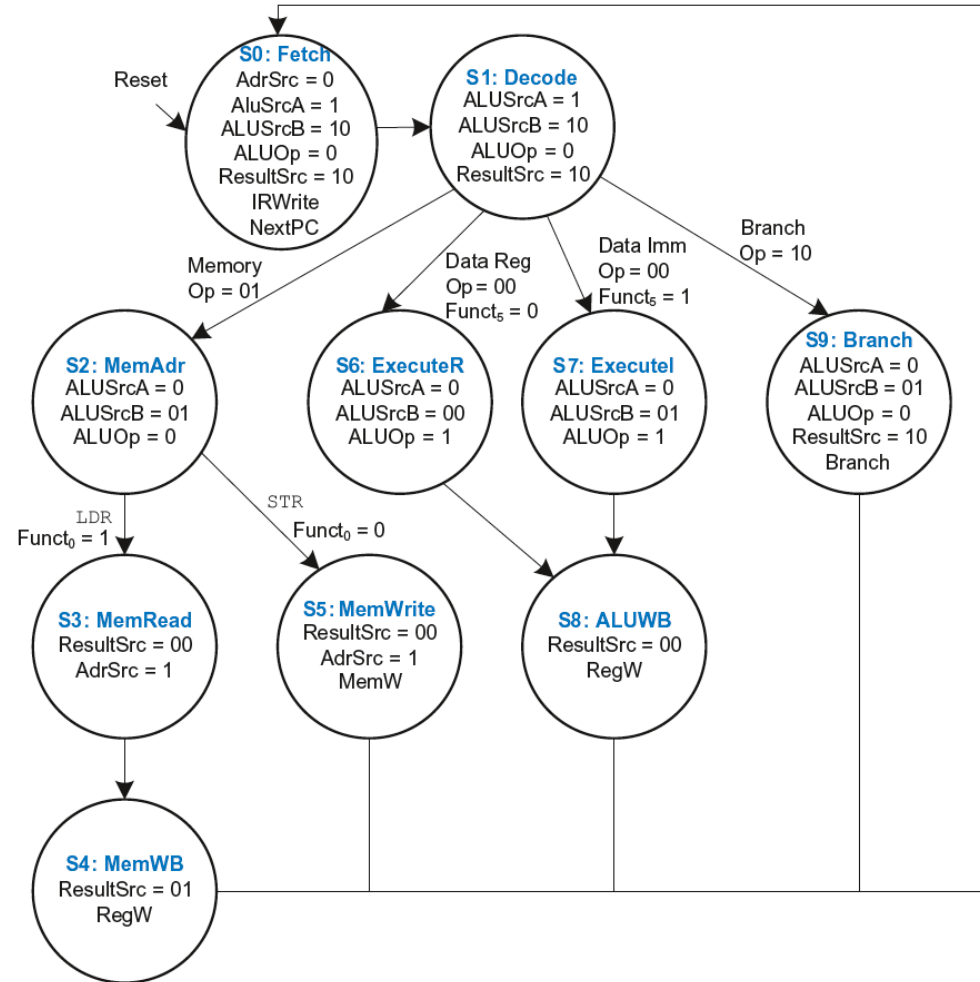

Multicycle Processor Performance

- Instructions take different number of cycles:
 - 3 cycles:
 - 4 cycles:
 - 5 cycles:



Multicycle Processor Performance

- Instructions take different number of cycles:
 - 3 cycles: B
 - 4 cycles: DP, STR
 - 5 cycles: LDR



Multicycle Processor Performance

- Instructions take different number of cycles:
 - 3 cycles: B
 - 4 cycles: DP, STR
 - 5 cycles: LDR
- CPI is weighted average
- SPECINT2000 benchmark:
 - 25% loads
 - 10% stores
 - 13% branches
 - 52% R-type



Multicycle Processor Performance

- Instructions take different number of cycles:
 - 3 cycles: B
 - 4 cycles: DP, STR
 - 5 cycles: LDR
- CPI is weighted average
- SPECINT2000 benchmark:
 - 25% loads
 - 10% stores
 - 13% branches
 - 52% R-type

$$\text{Average CPI} = (0.13)(3) + (0.52 + 0.10)(4) + (0.25)(5) = 4.12$$



Multicycle Processor Performance

Multicycle critical path:

- Assumptions:

- RF is faster than memory
- writing memory is faster than reading memory

$$T_{c2} = t_{pcq} + 2t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup}$$



Multicycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	25
ALU	t_{ALU}	120
Decoder	t_{dec}	70
Memory read	t_{mem}	200
Register file read	t_{RFread}	100
Register file setup	$t_{RFsetup}$	60

$$T_{c2} = ?$$



Multicycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	25
ALU	t_{ALU}	120
Decoder	t_{dec}	70
Memory read	t_{mem}	200
Register file read	t_{RFread}	100
Register file setup	$t_{RFsetup}$	60

$$\begin{aligned}T_{c2} &= t_{pcq} + 2t_{mux} + \max[t_{ALU} + t_{mux}, t_{mem}] + t_{setup} \\ &= [40 + 2(25) + 200 + 50] \text{ ps} = \mathbf{340 \text{ ps}}\end{aligned}$$



Multicycle Performance Example

For a program with **100 billion** instructions executing on a **multicycle** ARM processor

- **CPI** = 4.12 cycles/instruction
- **Clock cycle time:** $T_{c2} = 340$ ps

Execution Time = ?



Multicycle Performance Example

For a program with **100 billion** instructions executing on a **multicycle** ARM processor

- **CPI** = 4.12 cycles/instruction
- **Clock cycle time:** $T_{c2} = 340$ ps

$$\begin{aligned}\text{Execution Time} &= (\# \text{ instructions}) \times \text{CPI} \times T_c \\ &= (100 \times 10^9)(4.12)(340 \times 10^{-12}) \\ &= \mathbf{140 \text{ seconds}}\end{aligned}$$



Multicycle Performance Example

For a program with **100 billion** instructions executing on a **multicycle** ARM processor


- **CPI** = 4.12 cycles/instruction
- **Clock cycle time:** $T_{c2} = 340$ ps

$$\begin{aligned}\text{Execution Time} &= (\# \text{ instructions}) \times \text{CPI} \times T_c \\ &= (100 \times 10^9)(4.12)(340 \times 10^{-12}) \\ &= \mathbf{140 \text{ seconds}}\end{aligned}$$


This is **slower** than the single-cycle processor (84 sec.)



Review: Single-Cycle ARM Processor

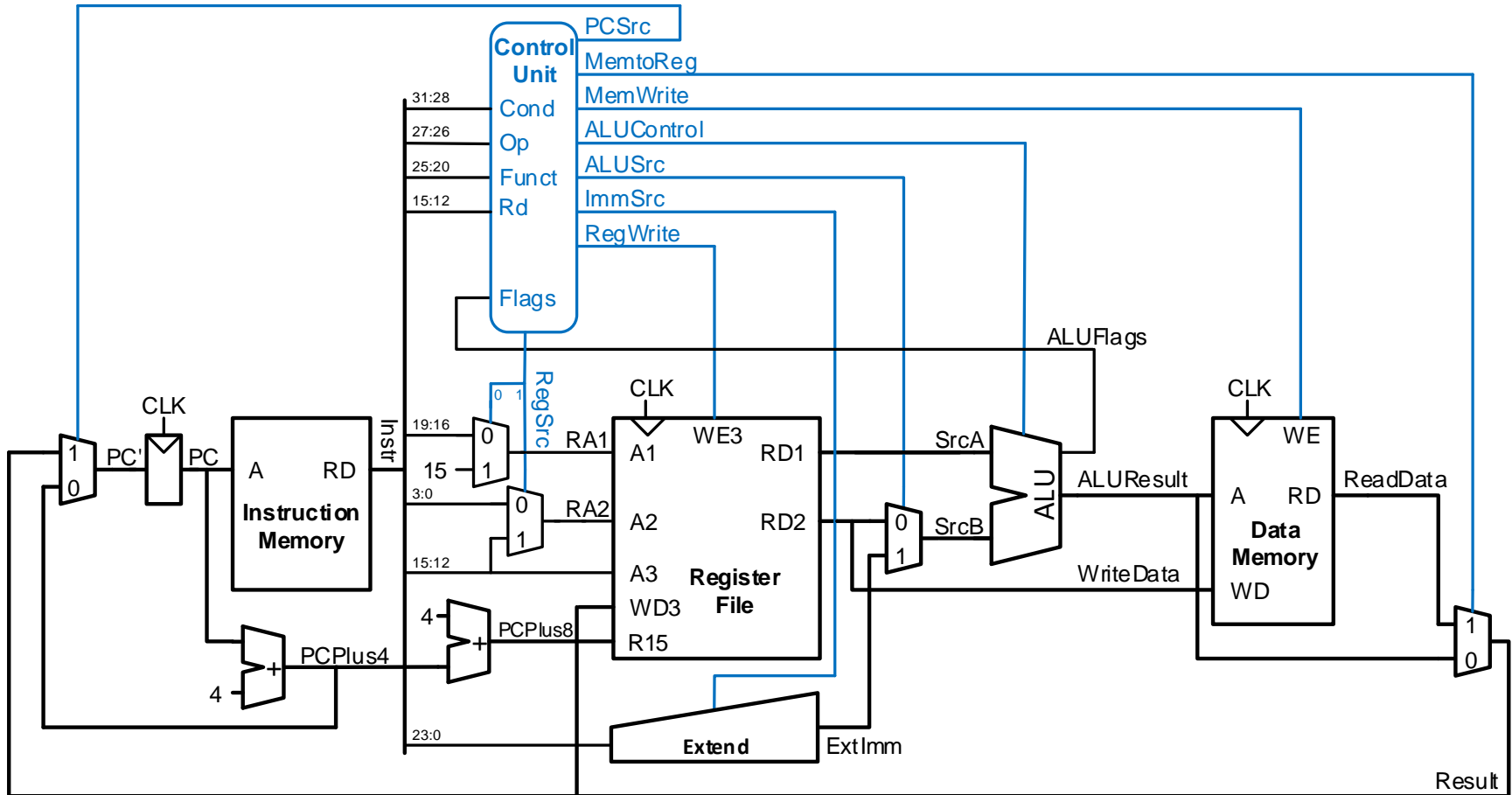

Review: Multicycle ARM Processor

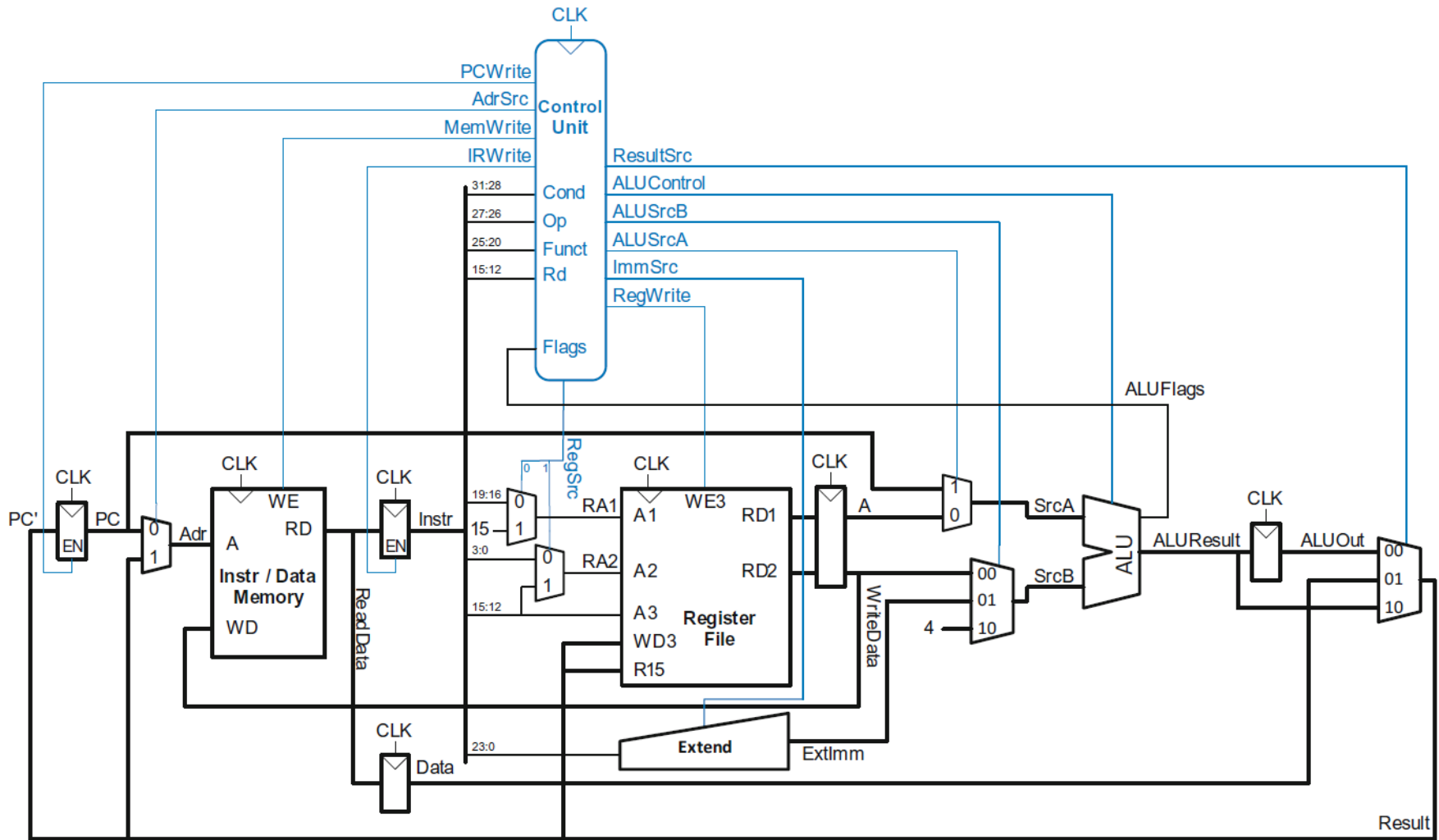


Pipelined ARM Processor

- Temporal parallelism
- Divide single-cycle processor into 5 stages:
 - Fetch
 - Decode
 - Execute
 - Memory
 - Writeback
- Add pipeline registers between stages




Single-Cycle vs. Pipelined

Single-Cycle

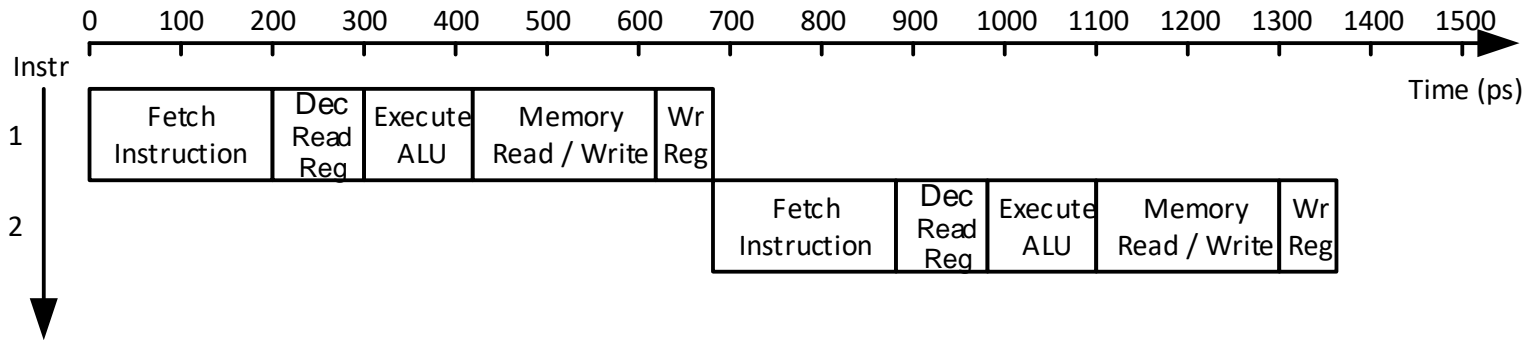


Pipelined

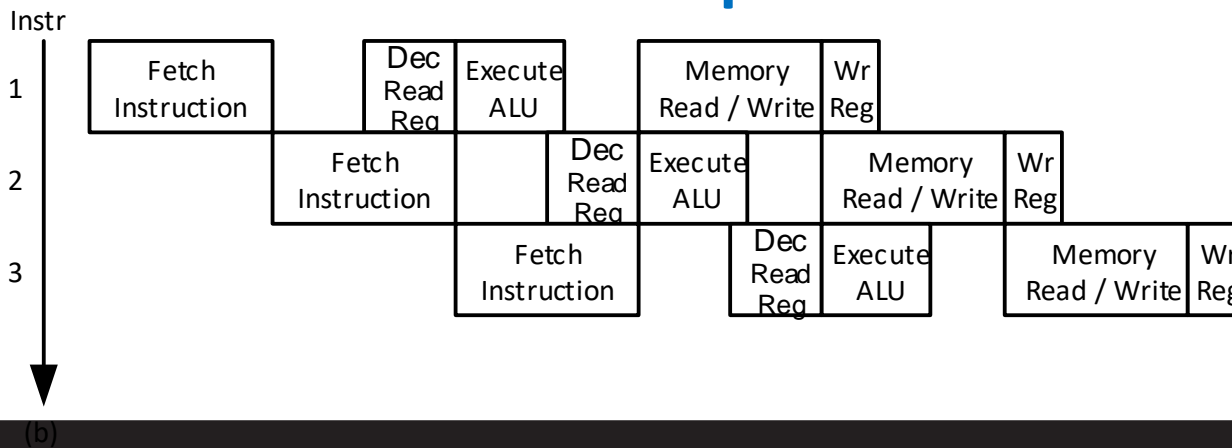

(b)




Pipelined Processor Abstraction

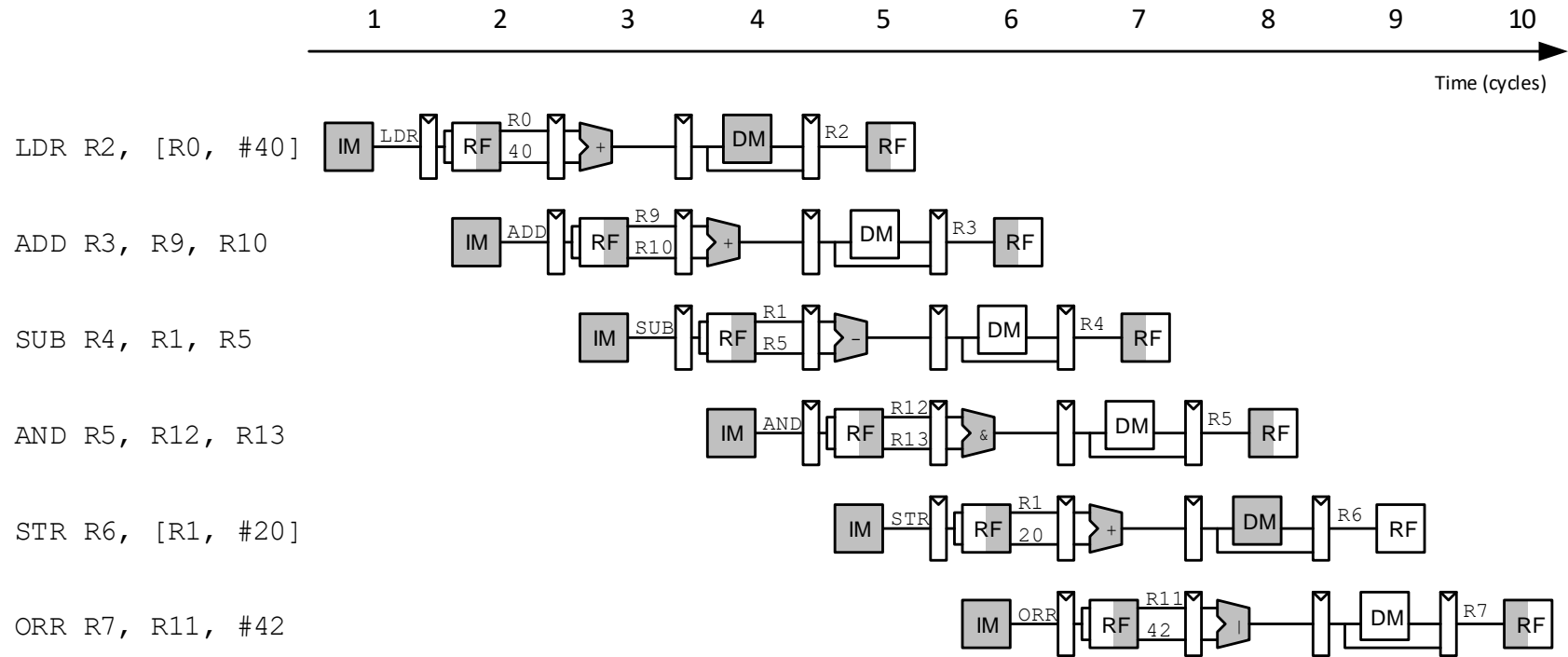


Single-Cycle & Pipelined Datapath


Single-Cycle

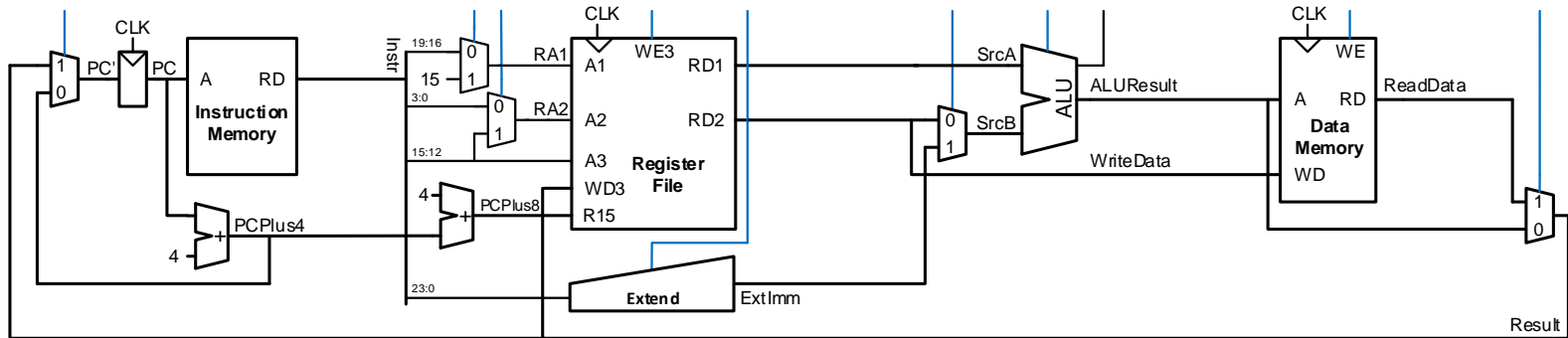

Pipelined

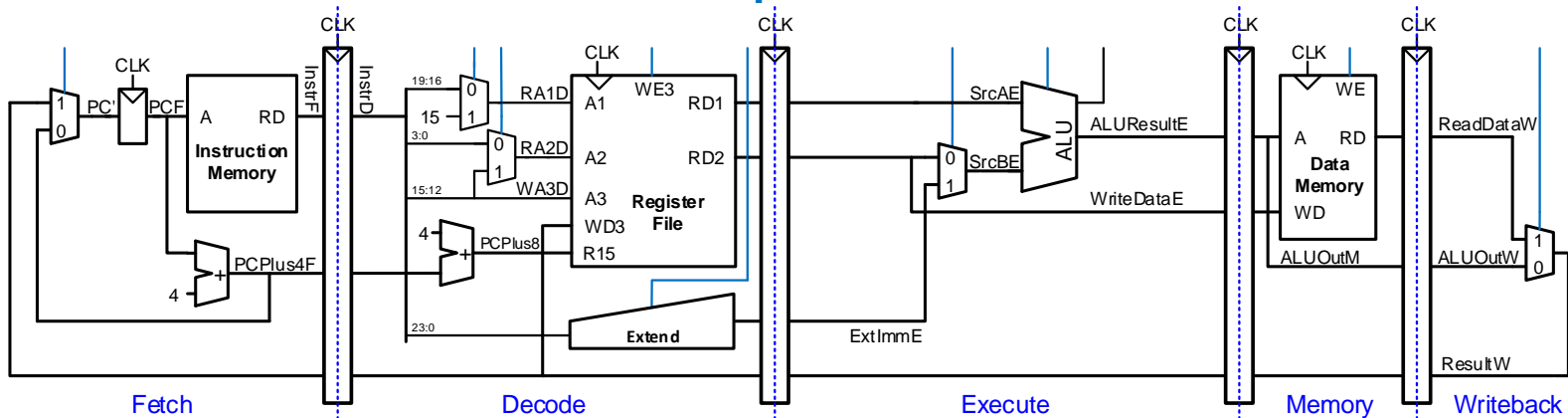



Corrected Pipelined Datapath

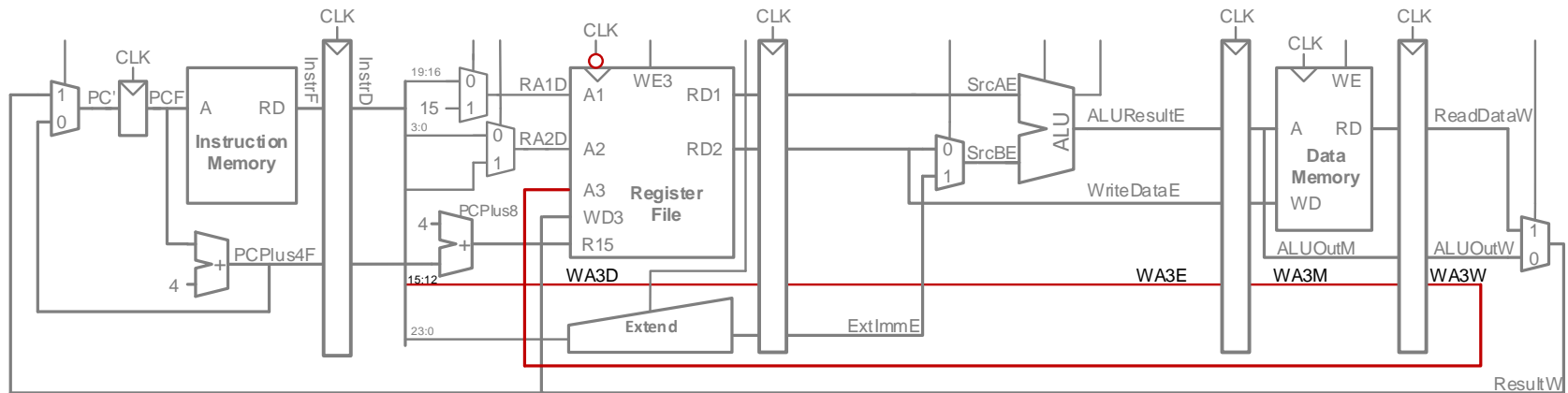

- ***WA3*** must arrive at same time as ***Result***
- Register file written on falling edge of ***CLK***




Optimized Pipelined Datapath

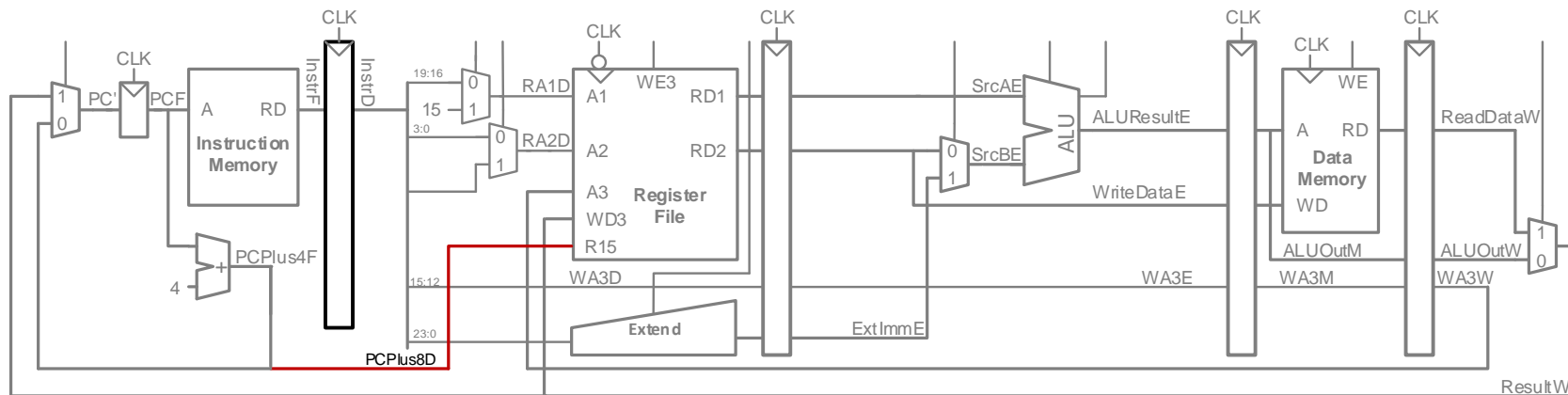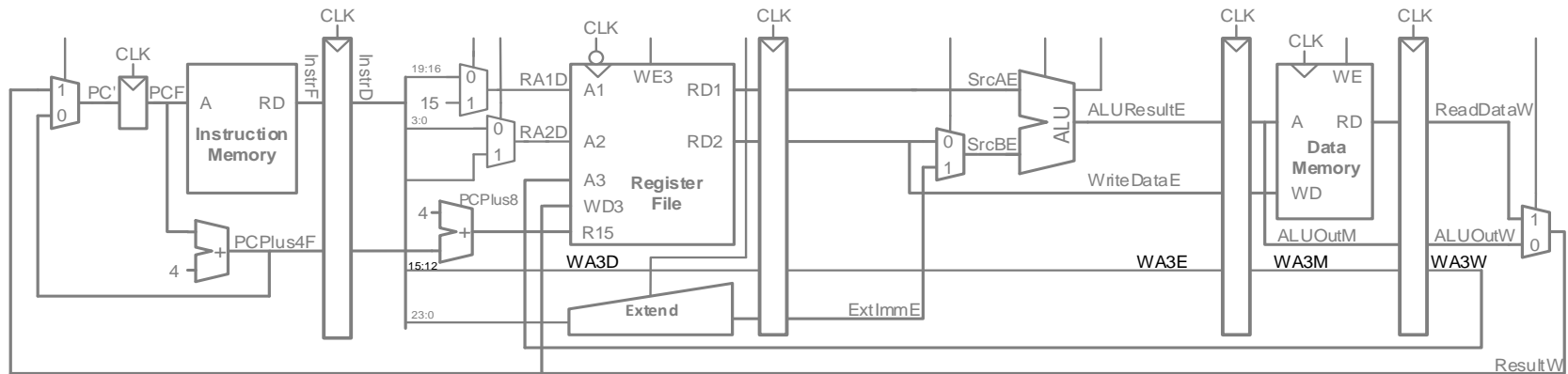

Remove adder by using $PCPlus4F$ after PC has been updated to $PC+4$



Pipelined Processor Control

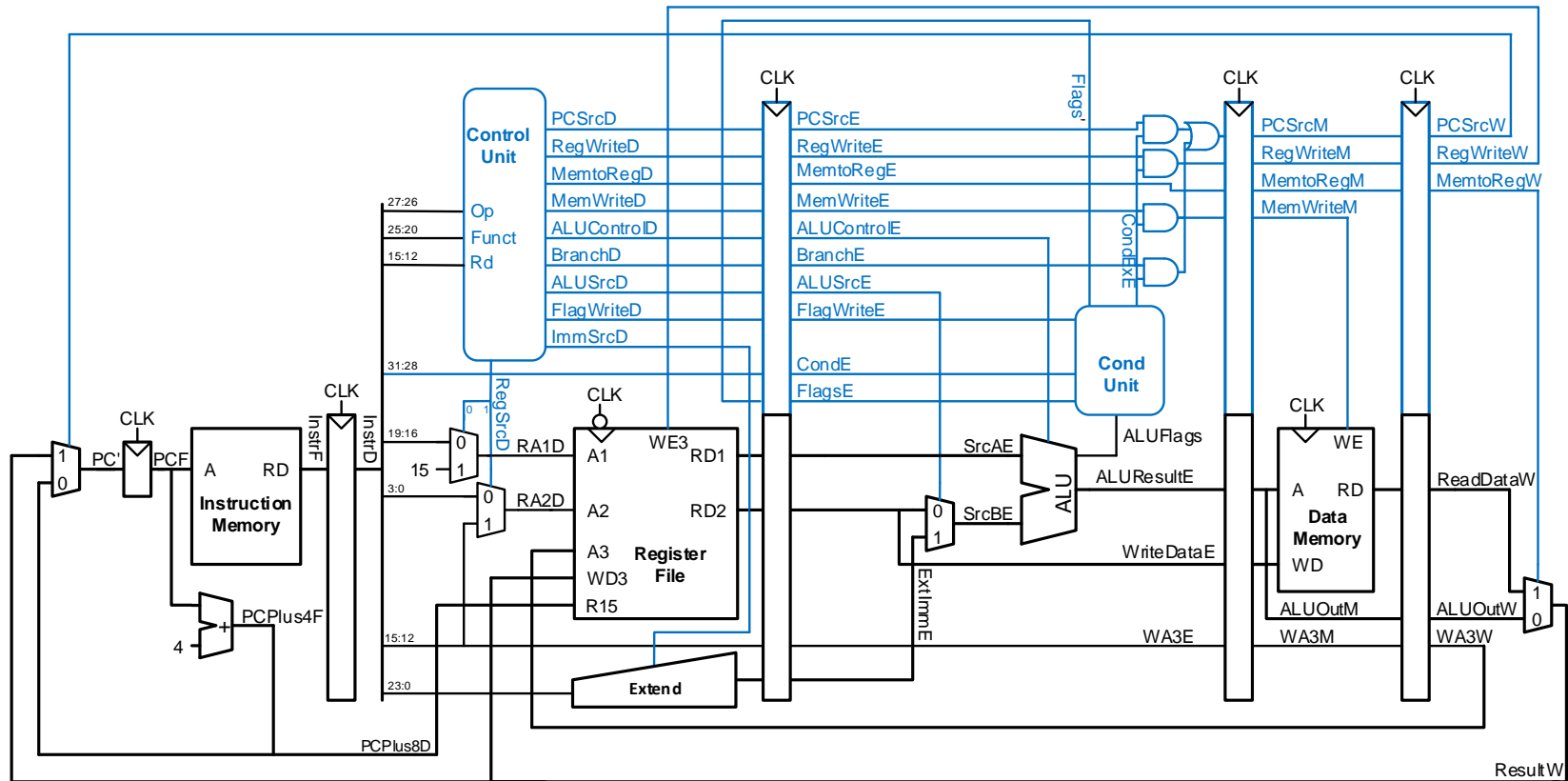

- Same control unit as single-cycle processor
- Control delayed to proper pipeline stage




Pipeline Hazards

- When an instruction depends on result from instruction that hasn't completed
- Types:
 - **Data hazard:** register value not yet written back to register file
 - **Control hazard:** next instruction not decided yet (caused by branch)



Data Hazard

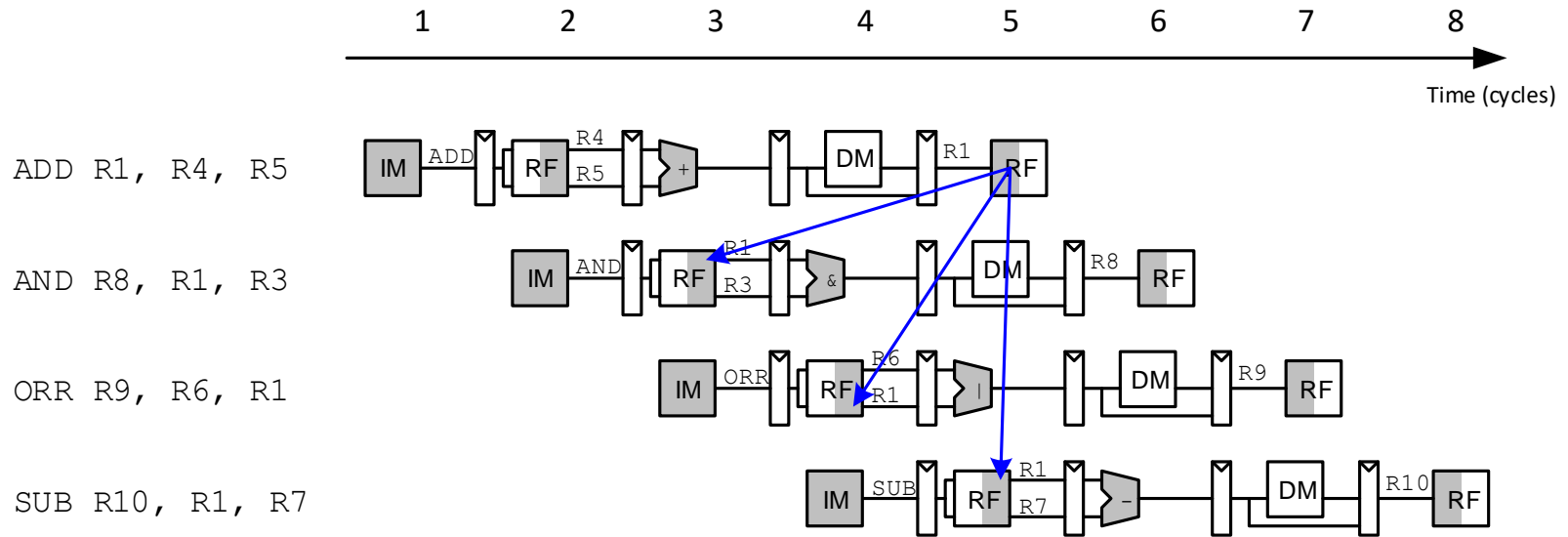


Handling Data Hazards

- Insert NOPs in code at compile time
- Rearrange code at compile time
- Forward data at run time
- Stall the processor at run time




Compile-Time Hazard Elimination

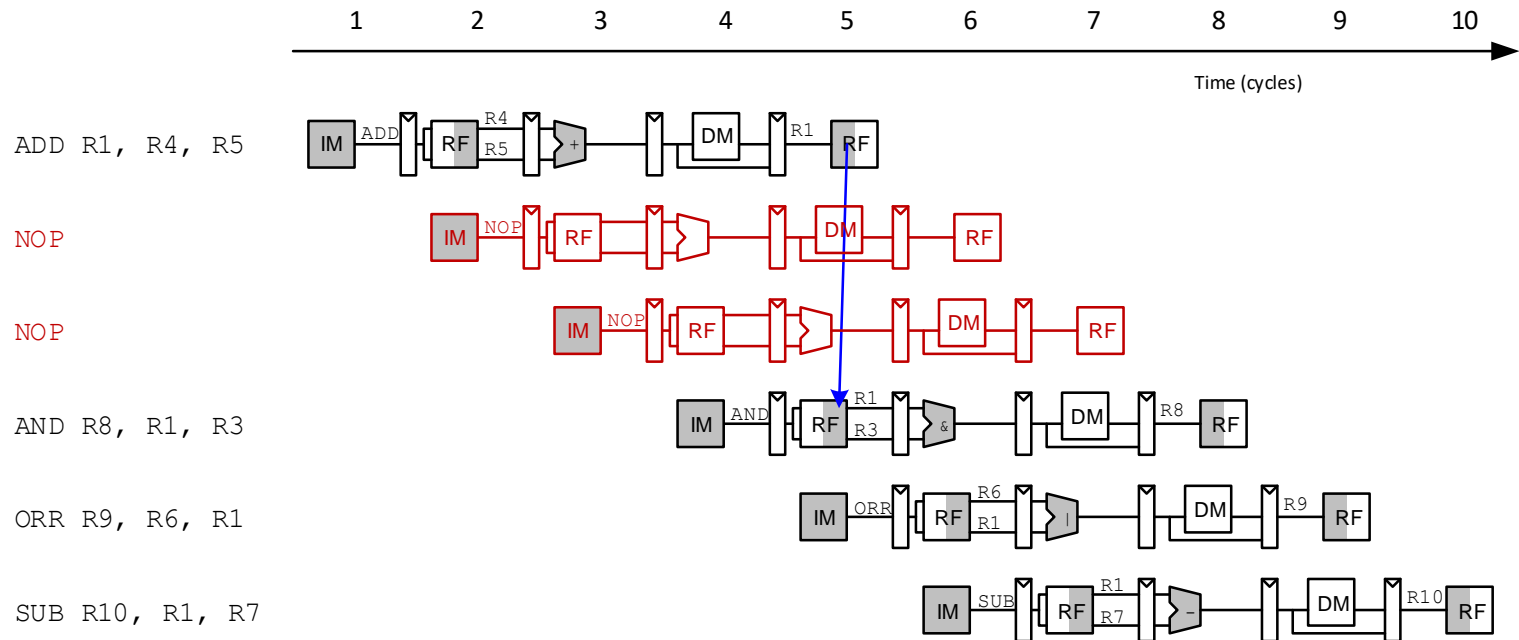
- Insert enough NOPs for result to be ready
- Or move independent useful instructions forward



Data Forwarding

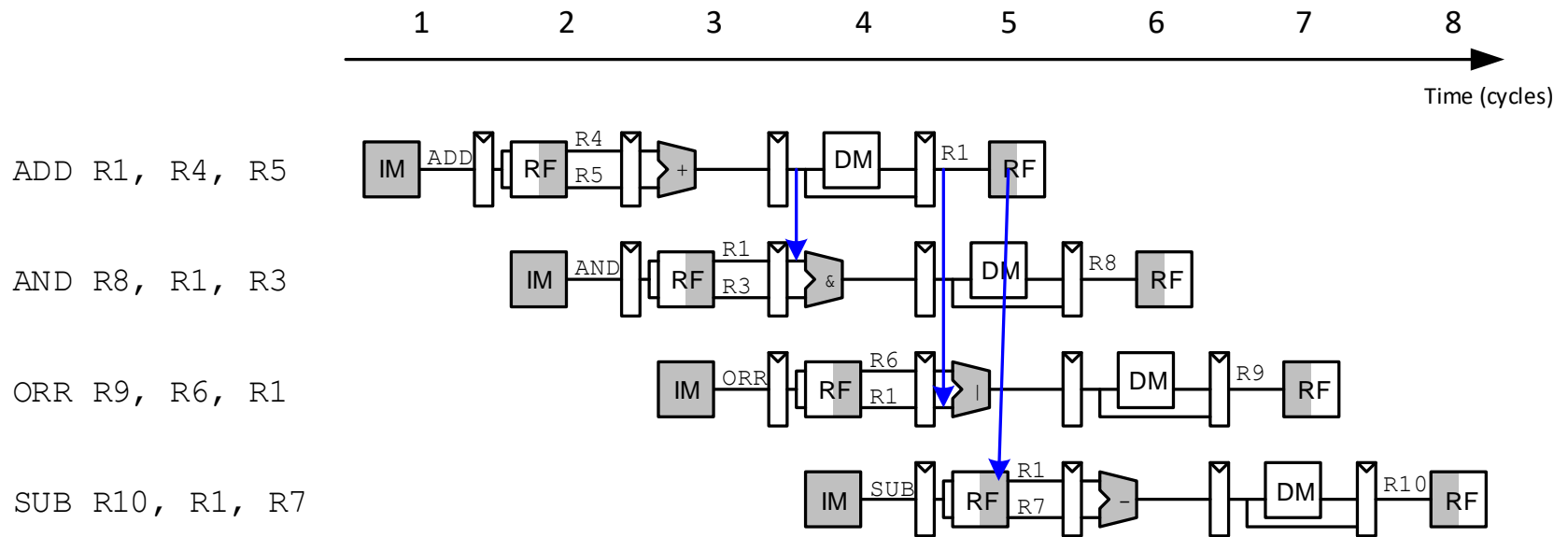


Data Forwarding

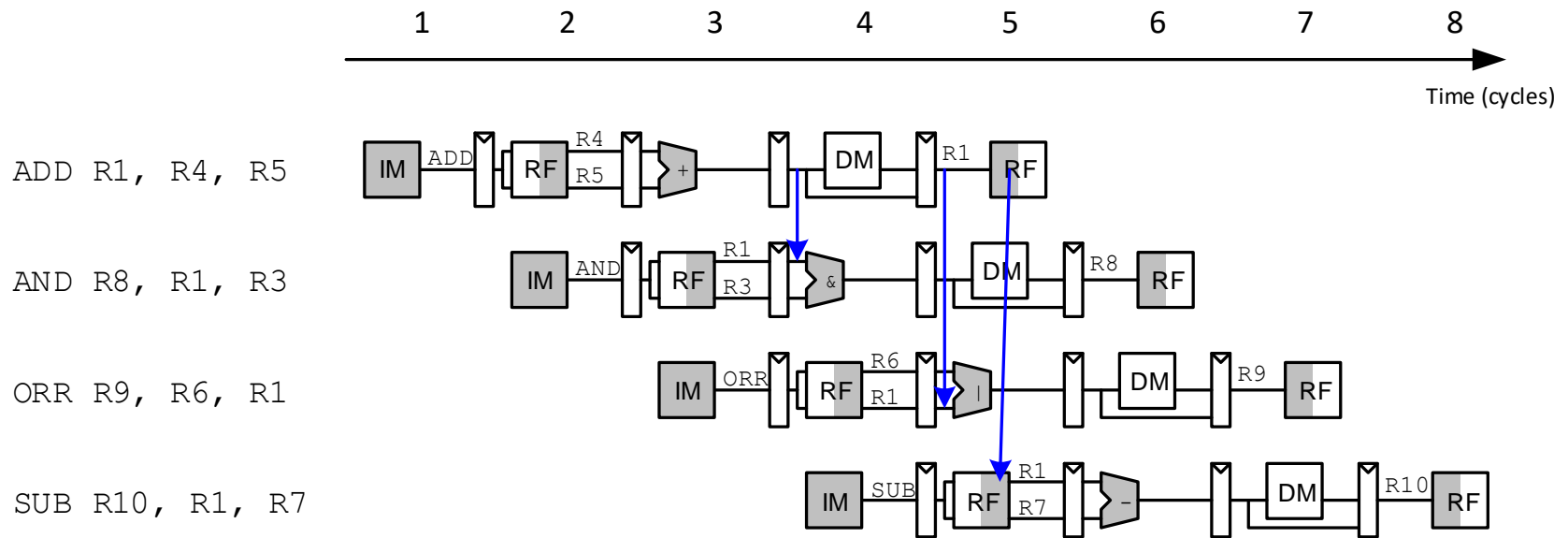

- Check if register read in Execute stage matches register written in Memory or Writeback stage
- If so, forward result



Data Forwarding

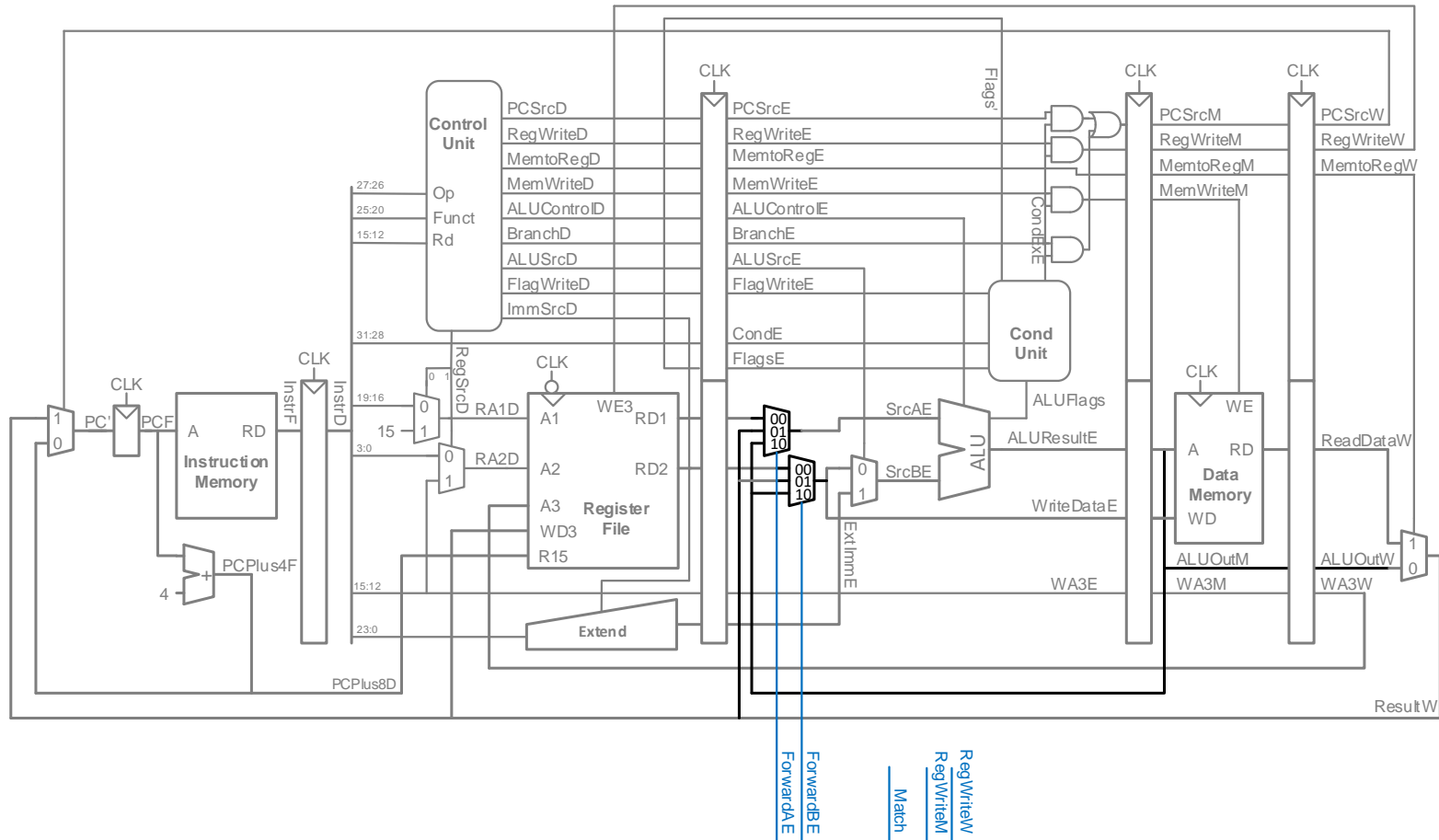

Hazard Unit



Data Forwarding

- **Execute** stage register matches **Memory** stage register?
Match_1E_M = (RA1E == WA3M)
Match_2E_M = (RA2E == WA3M)
- **Execute** stage register matches **Writeback** stage register?
Match_1E_W = (RA1E == WA3W)
Match_2E_W = (RA2E == WA3W)
- If it matches, forward result:

if	(Match_1E_M • RegWriteM)	ForwardAE = 10;
else if	(Match_1E_W • RegWriteW)	ForwardAE = 01;
else		ForwardAE = 00;



Data Forwarding


- **Execute** stage register matches **Memory** stage register?
Match_1E_M = (RA1E == WA3M)
Match_2E_M = (RA2E == WA3M)
- **Execute** stage register matches **Writeback** stage register?
Match_1E_W = (RA1E == WA3W)
Match_2E_W = (RA2E == WA3W)
- If it matches, forward result:

if	(Match_1E_M • RegWriteM)	ForwardAE = 10;
else if	(Match_1E_W • RegWriteW)	ForwardAE = 01;
else		ForwardAE = 00;


ForwardBE same but with Match2E




Stalling

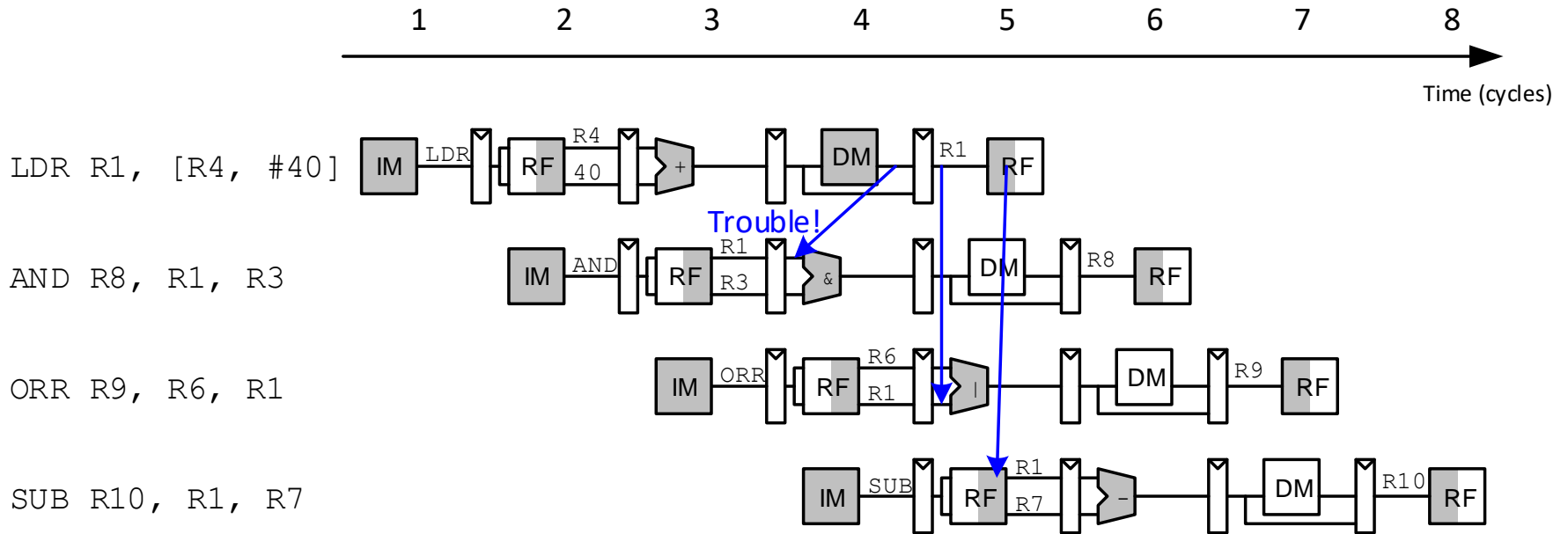

Stalling

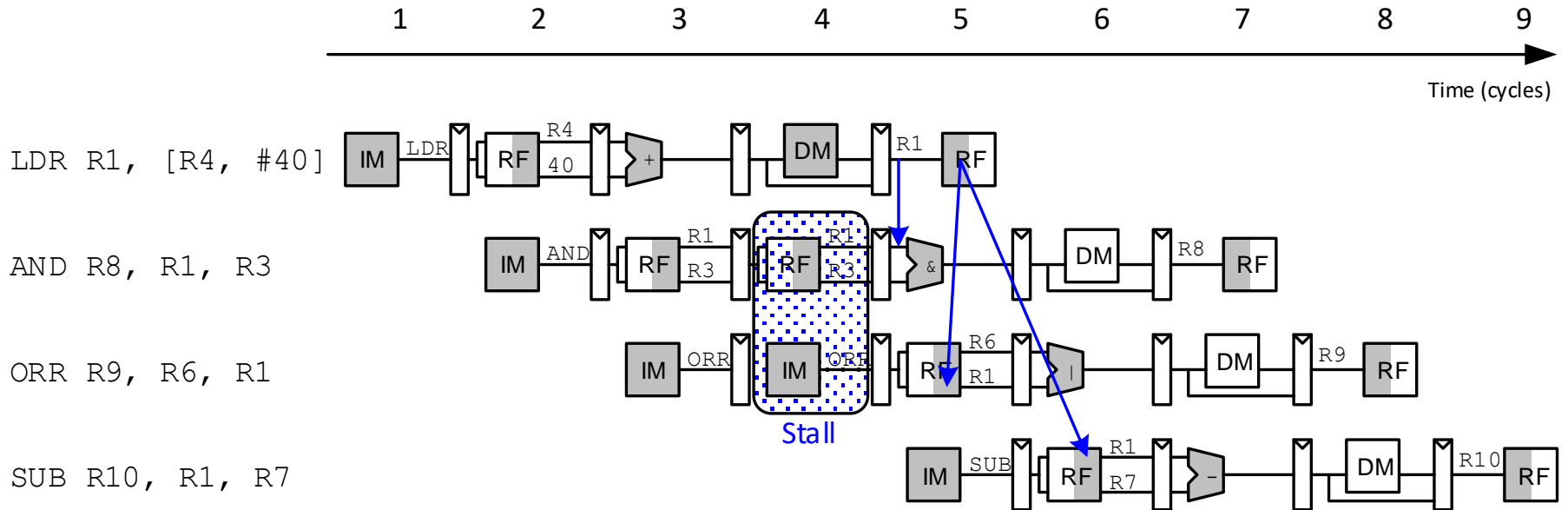

Stalling Hardware

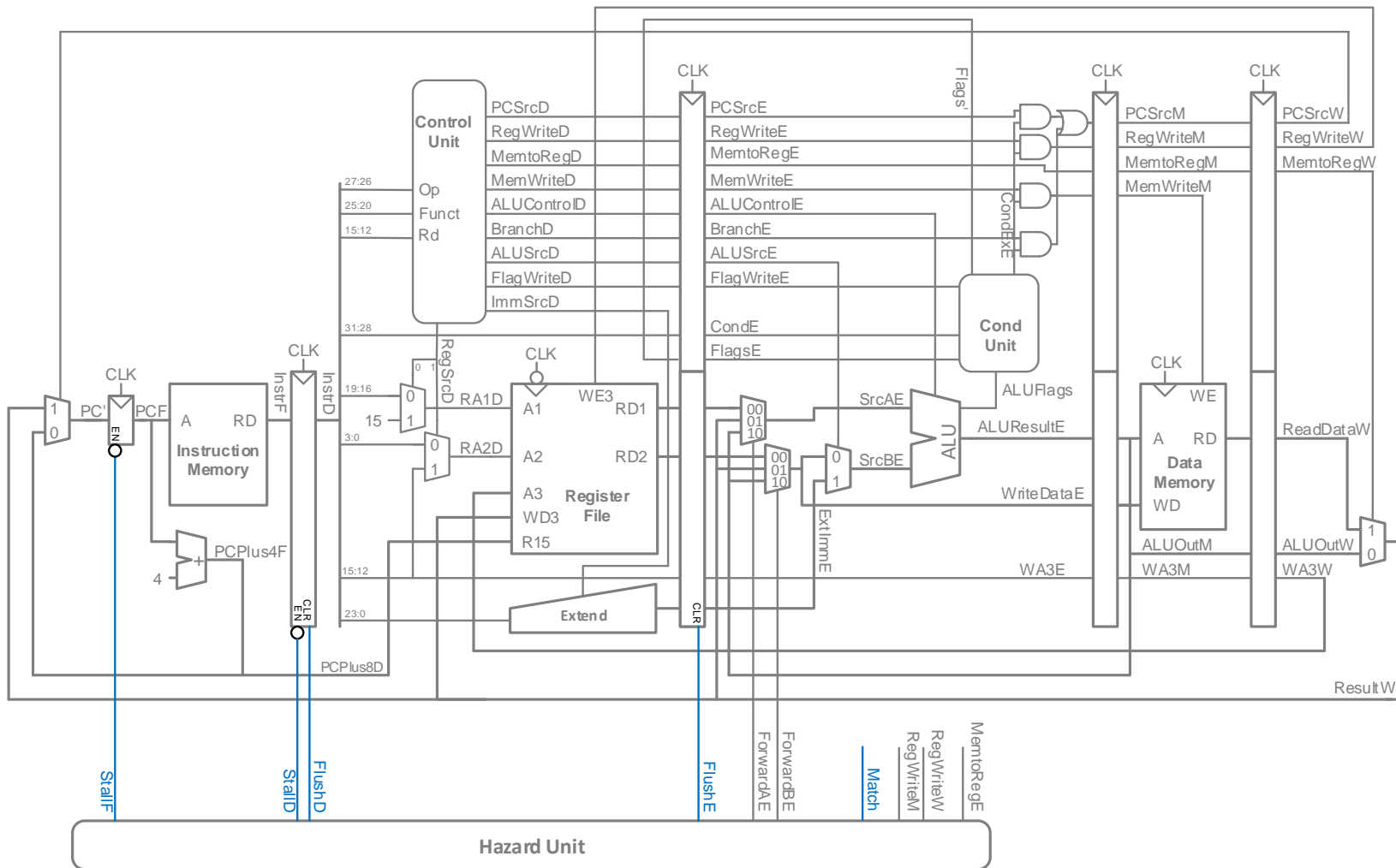

Stalling Logic

- Is either source register in the Decode stage the same as the one being written in the Execute stage?

$$Match_12D_E = (RA1D == WA3E) + (RA2D == WA3E)$$

- Is a LDR in the Execute stage AND $Match_12D_E$?

$$ldrstall = Match_12D_E \bullet MemtoRegE$$

$$StallF = StallD = FlushE = ldrstall$$




Control Hazards

- **B:**
 - branch not determined until the Writeback stage of pipeline
 - Instructions after branch fetched before branch occurs
 - These 4 instructions must be flushed if branch happens
- **Writes to PC (R15) similar**



Control Hazards

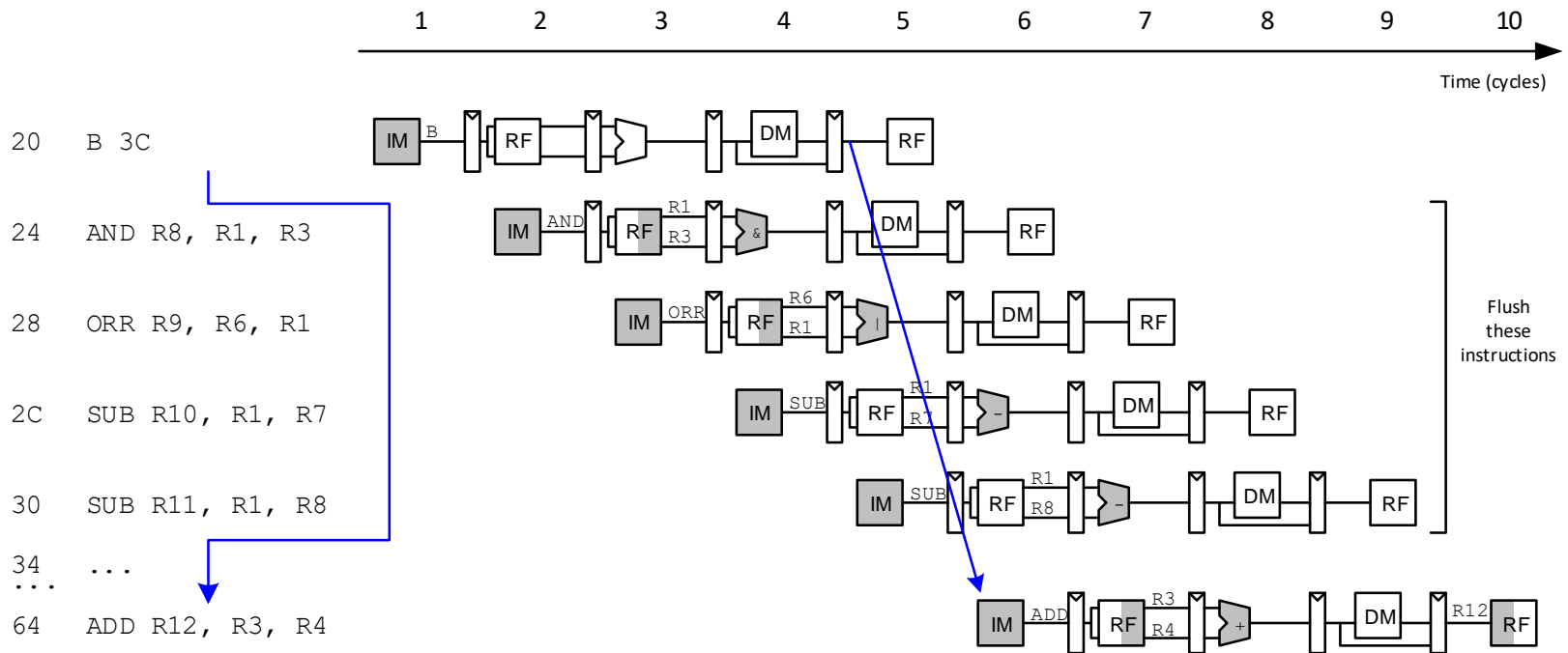

Branch misprediction penalty

- number of instruction flushed when branch is taken (4)
- May be reduced by determining BTA earlier




Early Branch Resolution


- **Determine BTA in Execute stage**
 - Branch misprediction penalty = 2 cycles
- **Hardware changes**
 - Add a branch multiplexer before *PC* register to select BTA from *ALUResultE*
 - Add *BranchTakenE* select signal for this multiplexer (only asserted if branch condition satisfied)
 - *PCSrcW* now only asserted for writes to *PC*



Pipelined processor with Early BTA

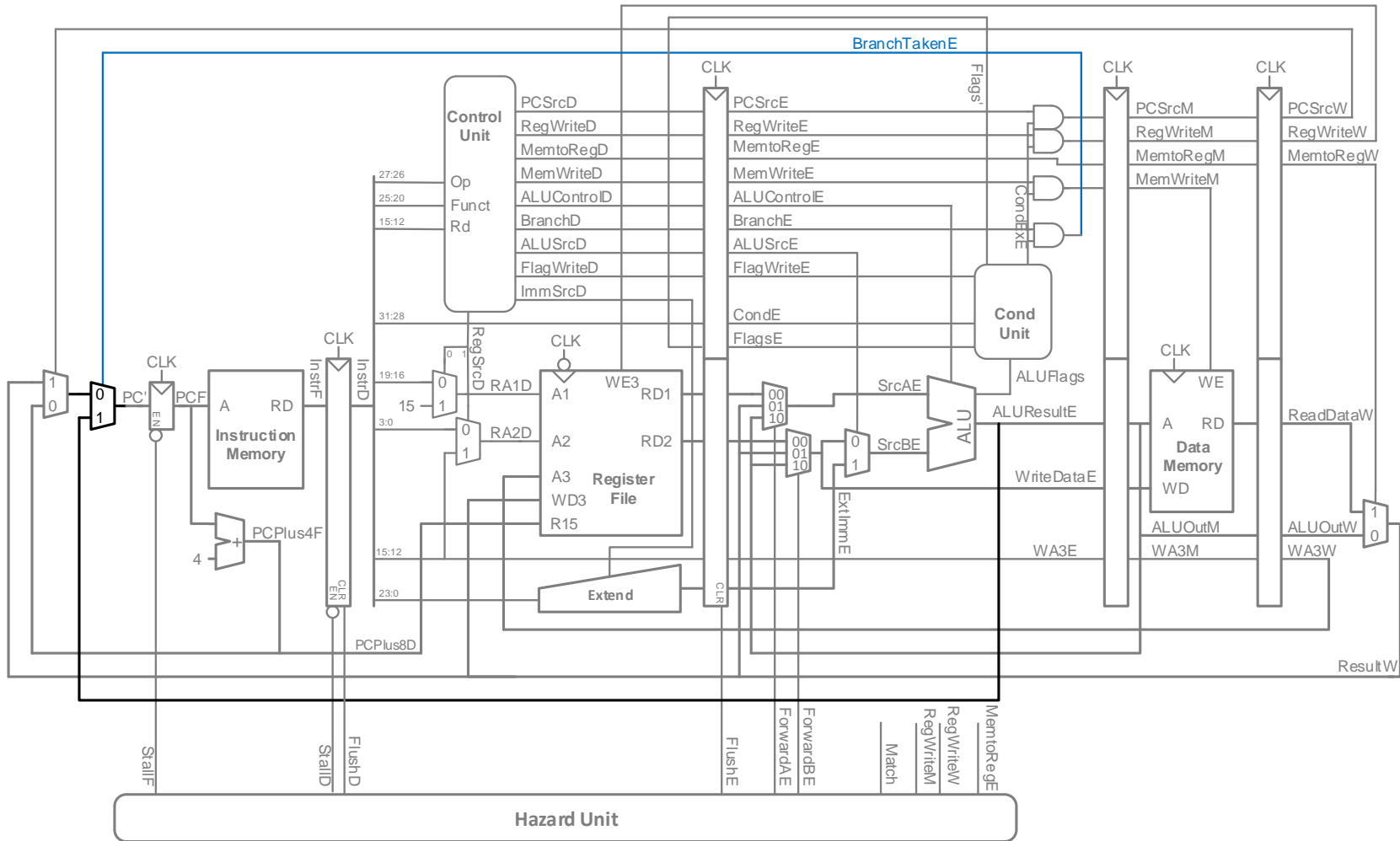

Control Hazards with Early BTA

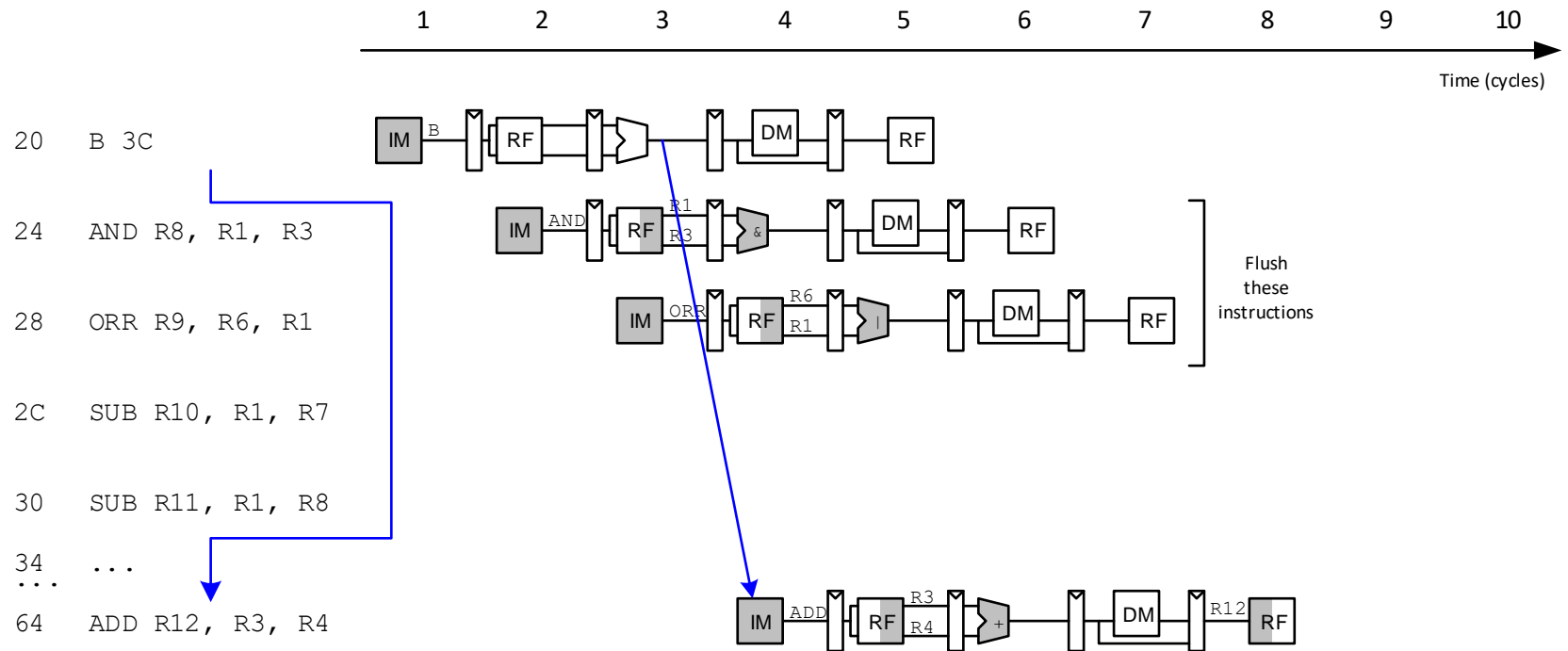

Control Stalling Logic

- ***PCWrPendingF* = 1** if write to *PC* in Decode, Execute or Memory

$$PCWrPendingF = PCSrcD + PCSrcE + PCSrcM$$

- **Stall Fetch** if *PCWrPendingF*

$$StallF = IdrStallD + PCWrPendingF$$

- **Flush Decode** if *PCWrPendingF* OR *PC* is written in Writeback OR branch is taken

$$FlushD = PCWrPendingF + PCSrcW + BranchTakenE$$

- **Flush Execute** if branch is taken


$$FlushE = IdrStallD + BranchTakenE$$

- **Stall Decode** if *IdrStallD* (as before)

$$StallD = IdrStallD$$



ARM Pipelined Processor with Hazard Unit

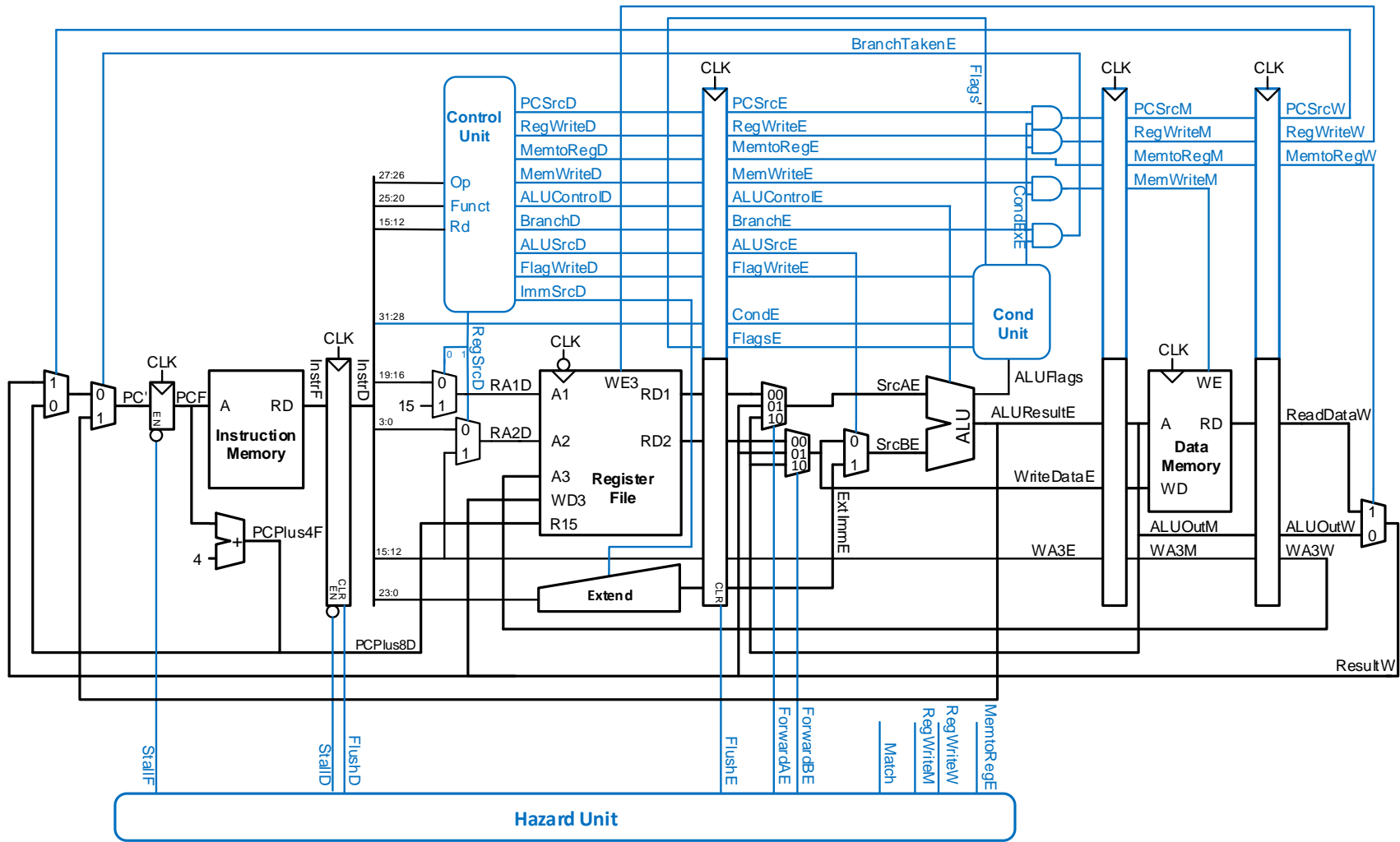

Pipelined Performance Example

- **SPECINT2000 benchmark:**
 - 25% loads
 - 10% stores
 - 13% branches
 - 52% R-type
- **Suppose:**
 - 40% of loads used by next instruction
 - 50% of branches mispredicted
- **What is the average CPI?**



Pipelined Performance Example

- **SPECINT2000 benchmark:**
 - 25% loads
 - 10% stores
 - 13% branches
 - 52% R-type
- **Suppose:**
 - 40% of loads used by next instruction
 - 50% of branches mispredicted
- **What is the average CPI?**
 - Load CPI = 1 when not stalling, 2 when stalling
So, $\text{CPI}_{lw} = 1(0.6) + 2(0.4) = 1.4$
 - Branch CPI = 1 when not stalling, 3 when stalling
So, $\text{CPI}_{beq} = 1(0.5) + 3(0.5) = 2$

$$\text{Average CPI} = (0.25)(1.4) + (0.1)(1) + (0.13)(2) + (0.52)(1) = 1.23$$



Pipelined Performance

- Pipelined processor critical path:

$$T_{c3} = \max [$$

$$t_{pcq} + t_{mem} + t_{setup}$$

$$2(t_{RFread} + t_{setup})$$

$$t_{pcq} + 2t_{mux} + t_{ALU} + t_{setup}$$

$$t_{pcq} + t_{mem} + t_{setup}$$

$$2(t_{pcq} + t_{mux} + t_{RFwrite})]$$

Fetch

Decode

Execute

Memory

Writeback



Pipelined Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	25
ALU	t_{ALU}	120
Memory read	t_{mem}	200
Register file read	t_{RFread}	100
Register file setup	$t_{RFsetup}$	60
Register file write	$t_{RFwrite}$	70

Cycle time: $T_{c3} = ?$



Pipelined Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	25
ALU	t_{ALU}	120
Memory read	t_{mem}	200
Register file read	t_{RFread}	100
Register file setup	$t_{RFsetup}$	60
Register file write	$t_{RFwrite}$	70

$$\begin{aligned}\text{Cycle time: } T_{c3} &= 2(t_{RFread} + t_{setup}) \\ &= 2[100 + 50] \text{ ps} = \mathbf{300 \text{ ps}}\end{aligned}$$



Pipelined Performance Example

Program with 100 billion instructions

$$\begin{aligned}\text{Execution Time} &= (\# \text{ instructions}) \times \text{CPI} \times T_c \\ &= (100 \times 10^9)(1.23)(300 \times 10^{-12}) \\ &= \mathbf{36.9 \text{ seconds}}\end{aligned}$$



Processor Performance Comparison

Processor	Execution Time (seconds)	Speedup (single-cycle as baseline)
Single-cycle	84	1
Multicycle	140	0.6
Pipelined	36.9	2.28



Advanced Microarchitecture

- Deep Pipelining
- Micro-operations
- Branch Prediction
- Superscalar Processors
- Out of Order Processors
- Register Renaming
- SIMD
- Multithreading
- Multiprocessors



Deep Pipelining

- 10-20 stages typical
- Number of stages limited by:
 - Pipeline hazards
 - Sequencing overhead
 - Power
 - Cost



Micro-operations

- Decompose more complex instructions into a series of simple instructions called *micro-operations* (*micro-ops* or μ -ops)
- At run-time, complex instructions are decoded into one or more micro-ops
- Used heavily in CISC (complex instruction set computer) architectures (e.g., x86)
- Used for some ARM instructions, for example:

Complex Op

```
LDR R1, [R2], #4
```

Micro-op Sequence

```
LDR R1, [R2]
```

```
ADD R2, R2, #4
```

Without u-ops, would need 2nd write port on the register file



Micro-operations

- Allow for dense code (fewer memory accesses)
- Yet preserve simplicity of RISC hardware
- ARM strikes balance by choosing instructions that:
 - Give better code density than pure RISC instruction sets (such as MIPS)
 - Enable more efficient decoding than CISC instruction sets (such as x86)



Branch Prediction

- Guess whether branch will be taken
 - Backward branches are usually taken (loops)
 - Consider history to improve guess
- Good prediction reduces fraction of branches requiring a flush



Branch Prediction

- Ideal pipelined processor: $CPI = 1$
- Branch misprediction increases CPI
- **Static branch prediction:**
 - Check direction of branch (forward or backward)
 - If backward, predict taken
 - Else, predict not taken
- **Dynamic branch prediction:**
 - Keep history of last several hundred (or thousand) branches in *branch target buffer*, record:
 - Branch destination
 - Whether branch was taken



Branch Prediction Example

```
MOV R1, #0           ; R1 = sum
MOV R0, #0           ; R0 = i

FOR                  ; for (i=0; i<10; i=i+1)
  CMP R0, #10
  BGE DONE
  ADD R1, R1, R0     ; sum = sum + i
  ADD R0, R0, #1
  B FOR

DONE
```




1-Bit Branch Predictor

- Remembers whether branch was taken the last time and does the same thing
- Mispredicts first and last branch of loop



2-Bit Branch Predictor

 


Only mispredicts last branch of loop



Superscalar

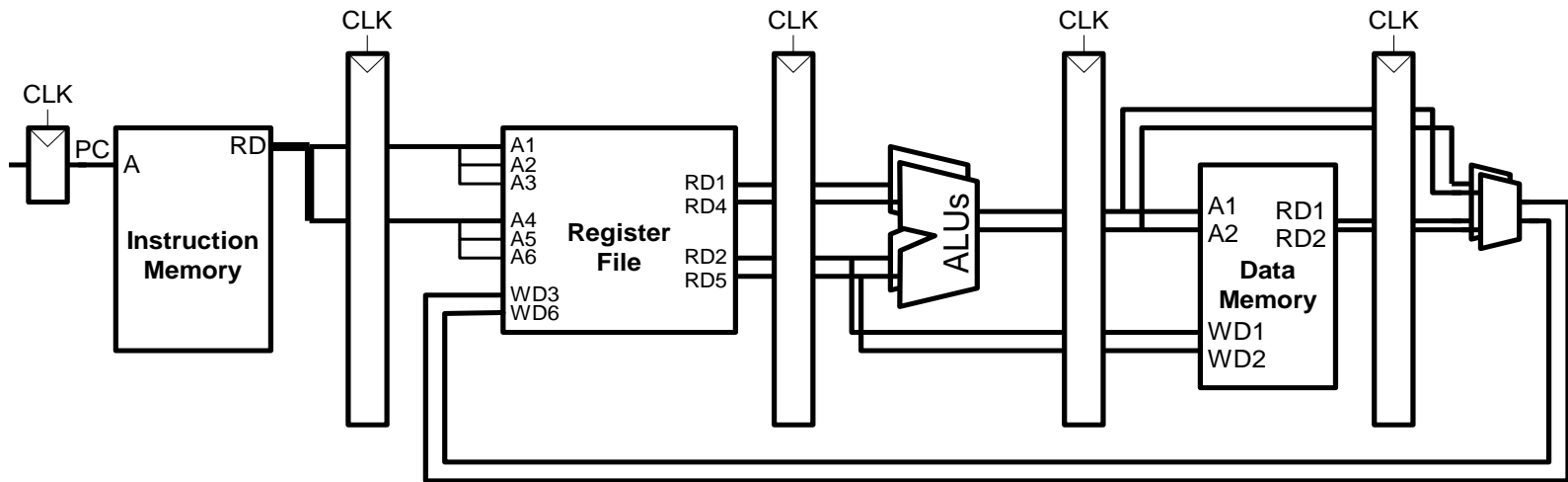
- Multiple copies of datapath execute multiple instructions at once
- Dependencies make it tricky to issue multiple instructions at once



Superscalar Example

Ideal IPC: 2


Actual IPC: 2

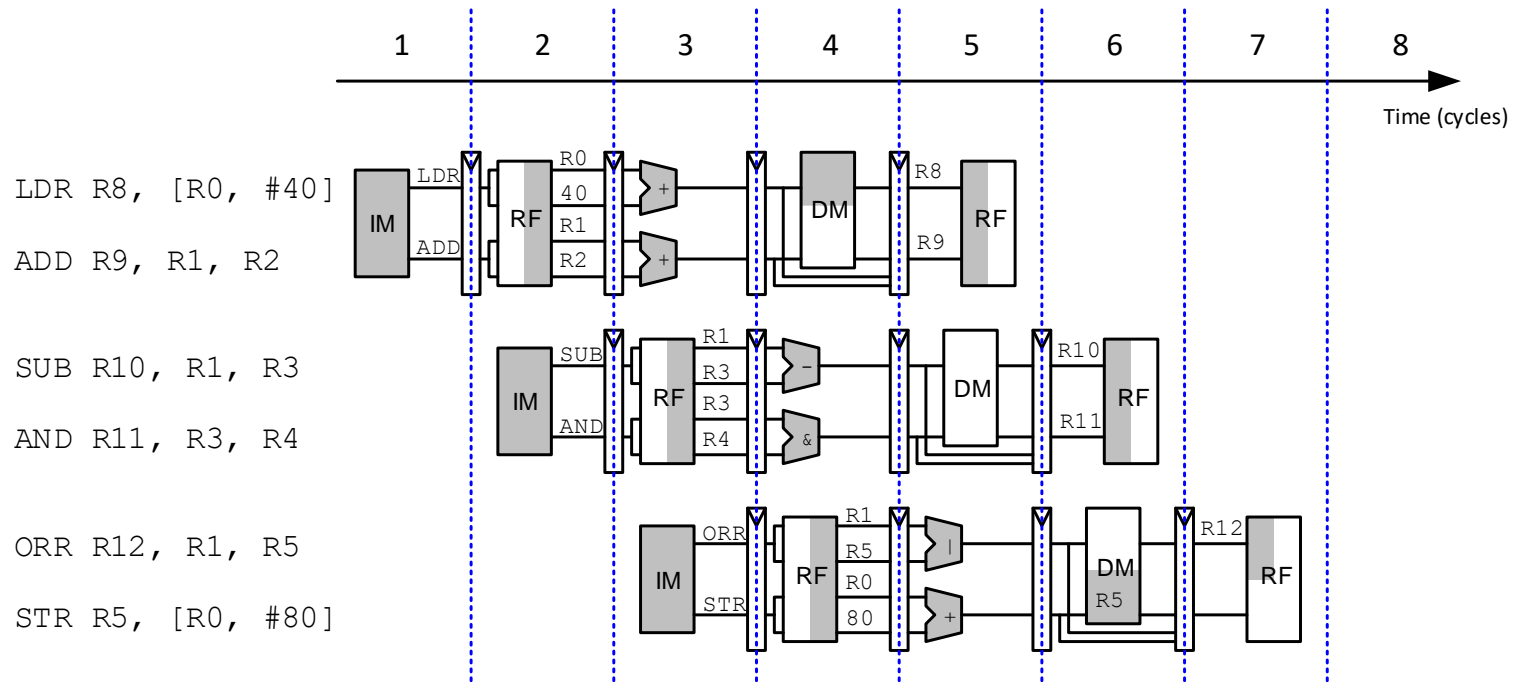

Superscalar with Dependencies

Ideal IPC: 2

Actual IPC: $6/5 = 1.2$

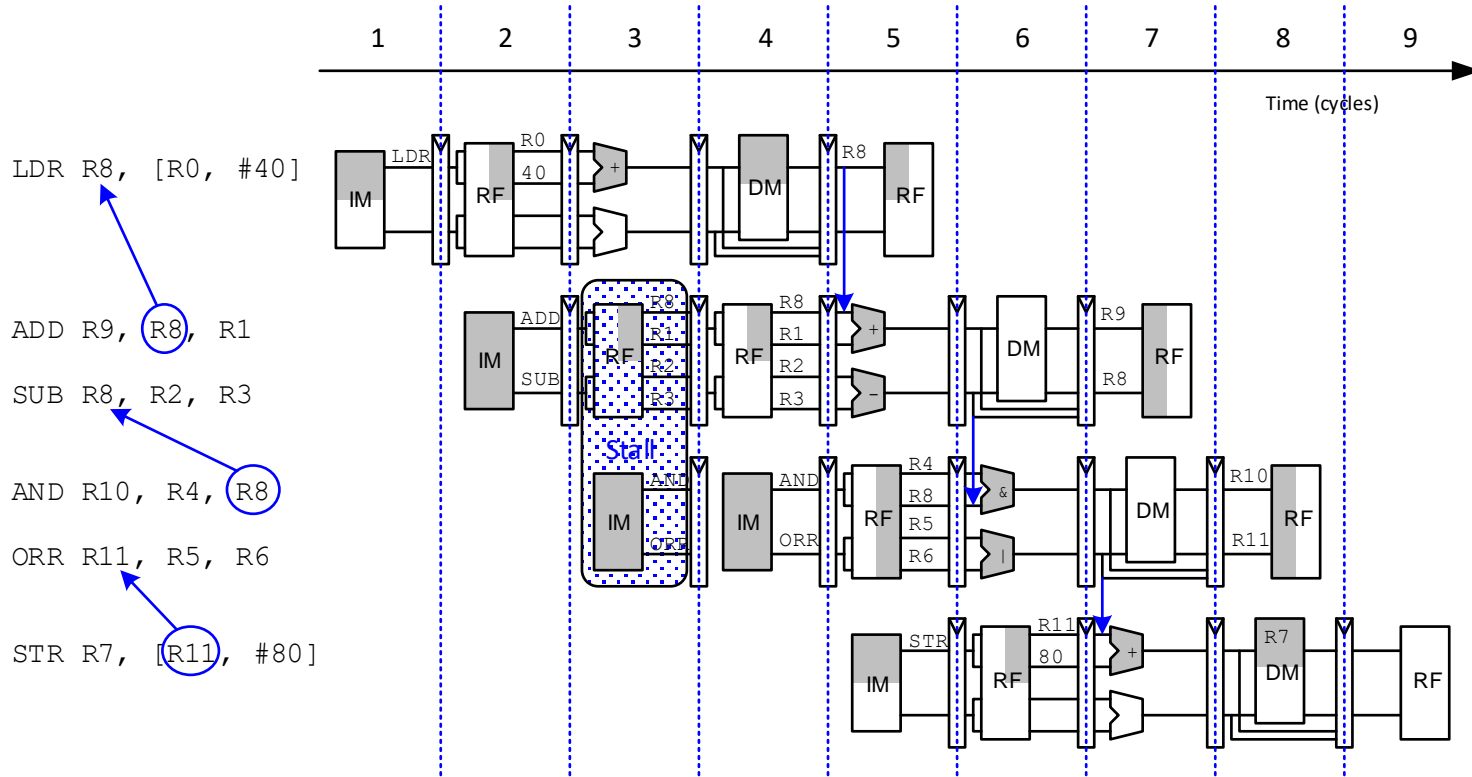

Out of Order Processor

- Looks ahead across multiple instructions
- Issues as many instructions as possible at once
- Issues instructions out of order (as long as no dependencies)
- **Dependencies:**
 - **RAW** (read after write): one instruction writes, later instruction reads a register
 - **WAR** (write after read): one instruction reads, later instruction writes a register
 - **WAW** (write after write): one instruction writes, later instruction writes a register



Out of Order Processor

- **Instruction level parallelism (ILP):** number of instruction that can be issued simultaneously (average < 3)
- **Scoreboard:** table that keeps track of:
 - Instructions waiting to issue
 - Available functional units
 - Dependencies




Out of Order Processor Example

```

LDR  R8, [R0, #40]
ADD  R9, R8, R1
SUB  R8, R2, R3
AND  R10, R4, R8
ORR  R11, R5, R6
STR  R7, [R11, #80]
    
```

Ideal IPC: 2
 Actual IPC: $6/4 = 1.5$

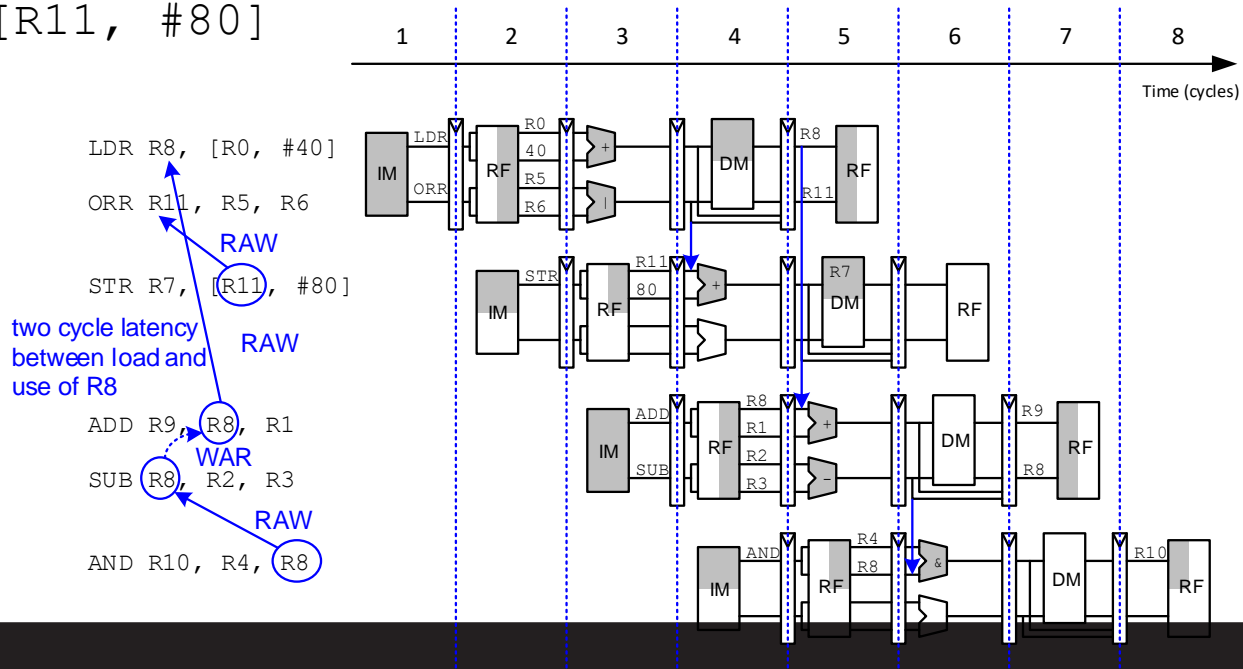


Register Renaming

```
LDR R8, [R0, #40]
ADD R9, R8, R1
SUB R8, R2, R3
AND R10, R4, R8
ORR R11, R5, R6
STR R7, [R11, #80]
```

Ideal IPC: 2
Actual IPC: $6/3 = 2$


```
LDR R8, [R0, #40]
SUB T0, R2, R3
AND R10, R4, T0
ORR R11, R5, R6
ADD R9, R8, R1
STR R7, [R11, #80]
```

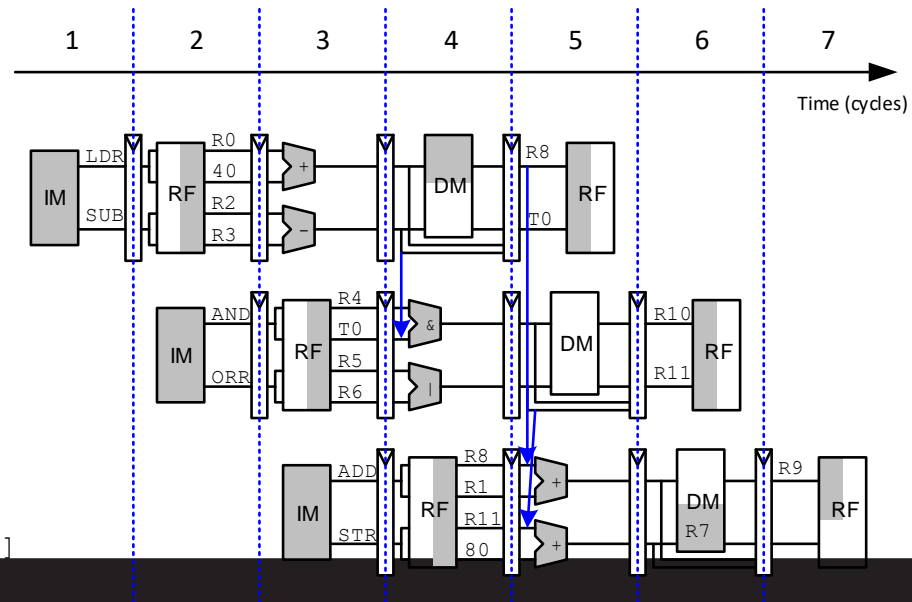2-cycle RAW (from LDR to AND)
 RAW (from LDR to ADD)
 RAW (from AND to ADD)



SIMD

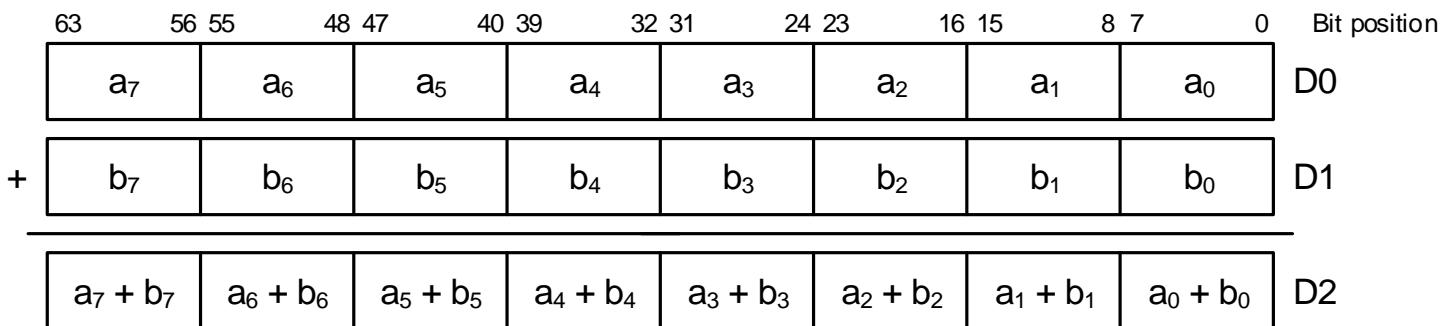- Single Instruction Multiple Data (SIMD)
 - Single instruction acts on multiple pieces of data at once
 - Common application: graphics
 - Perform short arithmetic operations (also called *packed arithmetic*)
- For example, add eight 8-bit elements



Advanced Architecture Techniques

- **Multithreading**
 - Wordprocessor: thread for typing, spell checking, printing
- **Multiprocessors**
 - Multiple processors (cores) on a single chip



Threading: Definitions

- **Process:** program running on a computer
 - Multiple processes can run at once: e.g., surfing Web, playing music, writing a paper
- **Thread:** part of a program
 - Each process has multiple threads: e.g., a word processor may have threads for typing, spell checking, printing



Threads in Conventional Processor

- One thread runs at once
- When one thread stalls (for example, waiting for memory):
 - Architectural state of that thread stored
 - Architectural state of waiting thread loaded into processor and it runs
 - Called **context switching**
- Appears to user like all threads running simultaneously



Multithreading

- Multiple copies of architectural state
- Multiple threads **active** at once:
 - When one thread stalls, another runs immediately
 - If one thread can't keep all execution units busy, another thread can use them
- Does not increase instruction-level parallelism (ILP) of single thread, but increases throughput

Intel calls this “hypertreading”



Multiprocessors

- Multiple processors (cores) with a method of communication between them
- Types:
 - **Homogeneous:** multiple cores with shared main memory
 - **Heterogeneous:** separate cores for different tasks (for example, DSP and CPU in cell phone)
 - **Clusters:** each core has own memory system



Other Resources

- Patterson & Hennessy's: *Computer Architecture: A Quantitative Approach*
- Conferences:
 - www.cs.wisc.edu/~arch/www/
 - ISCA (International Symposium on Computer Architecture)
 - HPCA (International Symposium on High Performance Computer Architecture)

